





**Chapter 9.** Sinusoidal signal  $\tilde{V}(t) = V_m \sin(\omega t + \phi)$  +  $\phi$  leads  $V_m$  and  $\omega$ . Phasor form  $\tilde{V} = V_m e^{j\phi} = V_m \angle \phi$ ,  $A_m$  magnitude  $\tilde{Y}(s) = Y = \frac{1}{Z}$  Impedance. Impedance  $\rightarrow Z = R + jX$  or  $|Z| < 0 \rightarrow$  if  $X > 0 \rightarrow$  Impedance lagging;  $X_C = \text{leading}$ . Also Admittance  $\rightarrow Y = G + jB$ ;  $G = \text{conductance}$ ,  $B = \text{susceptance}$ .

**Phasor Diagram:**

**Y-Delta:**  $Z_q = Z_1 + Z_2 + Z_3 + Z_4$ ,  $Z_1 = \frac{Z_c Z_1}{Z_1 + Z_2 + Z_3}$ ,  $Z_2 = \frac{Z_1 Z_2}{Z_1 + Z_2 + Z_3}$ ,  $Z_3 = \frac{Z_1 Z_3}{Z_1 + Z_2 + Z_3}$ ,  $Z_4 = \frac{Z_1 Z_4}{Z_1 + Z_3 + Z_4}$ .

**Delta-Y:**  $Z_1 = \frac{Z_1 Z_2}{Z_1 + Z_2 + Z_3}$ ,  $Z_2 = \frac{Z_1 Z_3}{Z_1 + Z_2 + Z_3}$ ,  $Z_3 = \frac{Z_1 Z_4}{Z_1 + Z_2 + Z_3}$ .

**Impedance triangle:**  $Z_1 = \frac{Z_1 Z_2}{Z_1 + Z_2 + Z_3}$ ,  $Z_2 = \frac{Z_1 Z_3}{Z_1 + Z_2 + Z_3}$ ,  $Z_3 = \frac{Z_1 Z_4}{Z_1 + Z_2 + Z_3}$ .

**Phase shift:** If the reactance and resistance are not the same value, then  $\theta$  will be  $45^\circ$ . Its  $\theta$  will be  $45^\circ$ .

**Chapter 10. Application / Sine Wave Oscillator** → for different frequency need to use superposition. If we got 2 source in a circuit like a cos and sin function in 1 circuit. We can convert sin to cos function for ex  $\cos \theta = \sin(\theta - \frac{\pi}{2})$  ex  $\Rightarrow 2 \sin st \rightarrow 2 \cos(st - \frac{\pi}{2}) \approx 2 \angle -90^\circ$ .

**Three phase circuit:**  $\rightarrow$  Voltage balance: same frequency with phase difference  $V_{AB} = V_p \angle +120^\circ$ ,  $V_{BC} = V_p \angle -120^\circ$ ,  $V_{CA} = V_p \angle -240^\circ$ . abc sequence (positive)  $\rightarrow V_{AB} = V_p \angle 0^\circ$ ,  $V_{BC} = V_p \angle -120^\circ$ ,  $V_{CA} = V_p \angle -240^\circ$ . acb sequence (negative)  $\rightarrow V_{AB} = V_p \angle 0^\circ$ ,  $V_{BC} = V_p \angle -120^\circ$ ,  $V_{CA} = V_p \angle -240^\circ$ . For impedance  $Z$  → Balance if same in magnitude / phasor sum  $\rightarrow Z_1 = Z_2 = Z_3 = Z$ . A wire-connected load / Delta  $\rightarrow Z_D = 3Z_y$ ;  $Z_y = \frac{1}{3}Z_D$ . Note that for  $Z_y$   $Z_y = Z_1 + Z_2 + Z_3$ . Instantaneous Power  $\rightarrow P = 3V_p I_p \cos \theta$ . Total instantaneous power is constant and does not change with time. Average Power per phase  $\rightarrow P_0 = V_p I_p \cos \theta$ ; Reactive Power per phase  $\rightarrow Q_0 = V_p I_p \sin \theta$ .  $P = 3V_p I_p \cos \theta = \sqrt{3} V_L I_L \cos \theta$ ;  $Q = 3V_p I_p \sin \theta = \sqrt{3} V_L I_L \sin \theta$ . Complex Power  $\rightarrow S = 3V_p I_p \angle \theta = 3I_p^2 Z_p = \frac{3V_p^2}{Z_p}$ . Power loss in the two wires  $\rightarrow P_{loss} = 2I_p^2 R = 2(\frac{P_0}{V_p})^2 R$ . Source voltage are not equal in magnitude or differ by phase angle that are reflected. Note that  $I_n = -(I_A + I_B + I_C)$ . Applications: Watt Meter directly by Mesh or nodal analysis. Instrument for measuring the average power  $\rightarrow$  for three meter. Two wattmeters  $\rightarrow P_T = P_1 + P_2$ ;  $P_1$  = reading (lower) from  $W_1$ ;  $P_2$  = reading (lower) from  $W_2$ . Consider a balance Y-load  $\rightarrow P_1 = V_L I_L \cos(\theta + 30^\circ)$ ;  $P_2 = V_L I_L \cos(\theta - 30^\circ)$ . Hence  $P_1 + P_2 = \sqrt{3} V_L I_L \cos \theta$ ;  $\theta = P_T$ ;  $P_2 - P_1 = V_L I_L \sin \theta = \frac{Q_T}{\sqrt{3}}$ ;  $\tan \theta = \frac{Q_T}{\sqrt{3}} / (P_T - P_1)$ .

**Chapter 11 AC Power Analysis:** The average power (Average of instantaneous Power)

**Average Power in phasor**  $\rightarrow P = \frac{1}{T} \int_{0}^{T} (P(t)) dt \Rightarrow \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$

**When  $\theta_v = \theta_i \rightarrow$  Purely resistive load**  $\rightarrow P = \frac{1}{2} V_m I_m = \frac{1}{2} I_m^2 R = \frac{1}{2} \frac{V_m^2}{R}$

**When  $\theta_v - \theta_i = \pm 90^\circ \rightarrow$  Purely reactive load**  $\rightarrow P = \frac{1}{2} V_m I_m \cos(\pm 90^\circ) = 0$

**Average Power Absorb by Impedance**  $\rightarrow P = \frac{1}{2} I^2 R \rightarrow$  Only resistance will contribute to average power

**Maximum Average Power**  $\rightarrow P = \frac{1}{2} I^2 R_L = \frac{1}{2} \frac{V_{TH}^2 R_L}{(R_{TH} + R_L)^2 + (X_{TH} + X_L)^2} \rightarrow R_L = R_{TH}$

**Note**  $\rightarrow Z_{TH} = R_{TH} + jX_{TH}$  for purely resistive  $\rightarrow Z_L = R_L + jX_L$  give  $P_{max} = \frac{V_{TH}^2}{8R_{TH}}$  only real part used.

**Pmax for  $R_L = \sqrt{R_{TH}^2 + X_{TH}^2} \rightarrow Z_L = Z_{TH}$**  use same eq.  $\rightarrow$  Max Power Open circuit ( $Z_{TH}$ )

**For the sinusoid  $i(t) = I_m \cos \omega t \rightarrow I_{rms} = \frac{I_m}{\sqrt{2}}$**   $\rightarrow$   $V_{rms} = \frac{V_m}{\sqrt{2}}$   $\rightarrow$  The average power  $\rightarrow P = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$

**We also define**  $\rightarrow \tilde{V}_{rms} = V_{rms} \angle \theta_v = V_m \angle \frac{\theta_v}{\sqrt{2}}$ ;  $\tilde{I}_{rms} = I_{rms} \angle \theta_i = \frac{I_m}{\sqrt{2}} \angle \theta_i$

**Load Impedance**  $\rightarrow Z = \frac{\tilde{V}}{\tilde{I}} = \frac{\tilde{V}_{rms}}{\tilde{I}_{rms}}$  Apparent power / Power factor  $\rightarrow$  from  $P = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$

**Chapter 11 Continued** for purely resistive load  $\rightarrow \theta_v - \theta_i = 0 \rightarrow \text{VAR} = 0$  for purely reactive load  $\rightarrow \theta_v - \theta_i = \pm 90^\circ \rightarrow P_f = 1 \rightarrow P = |S|$  Also Apparent power  $|S| = V_{rms} I_{rms} \rightarrow \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \rightarrow P = 0$   $\rightarrow S = L Z = P \angle \theta_v - \theta_i$

**Complex power**  $\rightarrow S = \frac{1}{2} \tilde{V} \tilde{I}^* = \tilde{V}_{rms} \tilde{I}_{rms}^* = V_{rms} I_{rms} \angle \theta_v - \theta_i \rightarrow S = V_{rms} I_{rms} \angle \theta_v - \theta_i$

The average power (real power)  $\rightarrow P = I_{rms}^2 R = V_{rms} I_{rms} \cos(\theta_v - \theta_i) = |S| \cos(\theta_v - \theta_i)$

reactive power  $\rightarrow Q = I_{rms}^2 X = V_{rms} I_{rms} \sin(\theta_v - \theta_i) = |S| \sin(\theta_v - \theta_i)$

**Q < 0  $\Leftrightarrow$  X < 0  $\Leftrightarrow$  Negative pf angle ( $\theta < 0$ )  $\Leftrightarrow \theta_v > \theta_i \Leftrightarrow$  leading**

**Q > 0  $\Leftrightarrow$  X > 0  $\Leftrightarrow$  Positive pf angle ( $\theta > 0$ )  $\Leftrightarrow \theta_v < \theta_i \Leftrightarrow$  lagging**

**Power triangle**  $\rightarrow$   $\begin{array}{c} \text{Impedance triangle} \\ \text{Complex Power} \\ \text{Unit} \Rightarrow V_A; P = \text{Real} \end{array}$

**Relationships**  $S = \frac{V_{rms}^2}{Z}$ ;  $S = I_{rms}^2 Z$ ;  $S = I_{rms}^2 R + j I_{rms}^2 X$

**Conservation of AC Power**  $\rightarrow$  The complex, real and reactive power of the source equal the respective sums of the complex, real and reactive powers of the individual loads. **Power factor correction**  $\rightarrow$  Add capacitors to find shunt capacitance. **Phase angle reduce**  $\rightarrow$  Power factor instrument  $(C = \frac{P(\tan \theta_1 - \tan \theta_2)}{W V^2}) \rightarrow Q_0 \text{ or kVAR rating} = P(\tan \theta_1 - \tan \theta_2)$

**Chapter 12** from Chapter 11  $\rightarrow$  given voltage or current in phasor form; then it's a peak value  $I_m$  and  $V_m$  To find  $V_{rms}$  and  $I_{rms}$  just divide by  $\sqrt{2}$

**Chapter 13**  $\rightarrow V = L \frac{di}{dt} \rightarrow$  self-inductance  $\rightarrow L = N \frac{\Phi}{dt}$ ; For two coil where  $i$  only carry the current. Energy in a coupled circuit  $\rightarrow$  energy stored in the circuit is  $\frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2$ .  $W_1 = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2$ ;  $W_2 = \frac{1}{2} L_2 i_2^2 + \frac{1}{2} L_1 i_1^2$ . Total energy when  $i_1, i_2$  reach constant  $\rightarrow W = W_1 + W_2$ . Total energy  $\rightarrow W = W_1 + W_2 = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + \frac{1}{2} L_1 i_2^2 + \frac{1}{2} L_2 i_1^2$ .  $\rightarrow M_{12} = M_{21} = M$   $\rightarrow$  Mutual inductance of coil 1 respect to coil 2.  $\rightarrow$  If one current leave and one current enter then  $\rightarrow W = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 - M I_1 I_2$ . Coefficient of coupling  $\rightarrow K = \frac{M}{\sqrt{L_1 L_2}}$ .  $\rightarrow$  If  $K < 0.5$ , Trant if  $K > 0.5$ .

**Linear Transformer**  $\rightarrow Z_{in} = R_L + j \omega L_L + \frac{W^2 M^2}{R_L + j \omega L_L + j \omega C_L}$   $\rightarrow$   $Z_{in}$  reflected impedance due to the coupling.

**II Circuit**  $\rightarrow$   $\begin{array}{c} \frac{1}{j \omega L_1} + \frac{1}{j \omega L_2} \\ \frac{1}{j \omega L_2} + \frac{1}{j \omega L_1} \end{array}$

**Power by Resistor**  $\rightarrow P = Re(U_i^2)$

**Power Formulae**  $P = I^2 R$ ;  $P = V^2 / R$ ;  $P = V_{rms}^2 / R$

**Apparent power**  $P_f = (\cos(\theta_v - \theta_i))^2$   $\rightarrow \theta_v - \theta_i = P_f \text{ angle}$ .

**Note that**  $P_f$  angle is equal to the angle of load impedance  $P_f = \angle Z = \theta_v - \theta_i$

**Phase voltages/cu**

$V_{an} = V_p/0^\circ$	<b>Line voltages/currents</b>	<b>Positive Sequence Chapter 13 Continued</b>	<b>Pic for II Circuit</b>
$V_{bn} = V_p/-120^\circ$	$V_{ab} = \sqrt{3}V_p/30^\circ$	<b>Ideal transformer</b> $\rightarrow K=1; R_1=R_2=0; L_1, L_2, M \rightarrow \infty \rightarrow n=\text{turn ratio}$	
$V_{cn} = V_p/+120^\circ$	$V_{bc} = V_{ab}/-120^\circ$	$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$ Apply the same as $\frac{V_2}{V_1}$ for current $\frac{i_1}{i_2} = \frac{V_2}{V_1} = n$	$\frac{I_1}{I_2} = \frac{V_2}{V_1} = n$ If $n=1 \Rightarrow$ isolation transformer.
Same as line curr	$V_{ca} = V_{ab}/+120^\circ$	<b>Step-down</b> $\rightarrow n > 1 : V_2 > V_1 ; V_2 < V_1 ; n < 1$	<b>Rules</b> $\Rightarrow$ If $V_1/V_2$ are both positive or negative at the dotted terminal then $n = \frac{V_2}{V_1}$ else $\frac{V_2}{V_1} = -n$ .
$V_{an} = V_p/0^\circ$	$V_{ab} = V_{AB} = \sqrt{3}V_p/30^\circ$	<b>Step-up transformer</b> $\rightarrow n > 1 : V_2 > V_1$	$\Leftarrow$ If $i_1/i_2$ both enter into or both leave the dotted terminal then $\frac{I_1}{I_2} = -n$ else $\frac{I_1}{I_2} = n$
$V_{bn} = V_p/-120^\circ$	$V_{bc} = V_{BC} = V_{ab}/-120^\circ$	<b>Ideal Transformer absorb no power</b> $\rightarrow S_1 = S_2$ <b>same apparent Power</b>	<b>Thevenin equivalent</b> reflecting the secondary side to primary side
$V_{cn} = V_p/+120^\circ$	$V_{ca} = V_{CA} = V_{ab}/+120^\circ$	<b>Input Impedance</b> $\rightarrow Z_{in} = \frac{V_1}{I_1}$ <b>Complex Power</b>	$Z_1 = \frac{Z_2}{n^2}$ divide second $Z$ by $n^2$ and multiply second $V$ by $n$ and second $I$ by $n$ .
$I_{AB} = \sqrt{3}V_p/30^\circ$	$I_a = I_{AB}\sqrt{3}/-30^\circ$	<b>KVA rating</b> $\rightarrow  S  = V_1 I_1$	$V_1 = \frac{V_{2d}}{n}$ multiply the primary $V$ by $n$ and divide the primary $I$ by $n$ .
$I_{BC} = \sqrt{3}V_p/30^\circ$	$I_b = I_{AB}/-120^\circ$	<b>Power delivered to load</b> $\rightarrow P =  I_1 ^2 Z_L$	$I_1 = \frac{I_{2d}}{n}$ multiply the primary $I$ by $n$ and divide the primary $V$ by $n$ .
$I_{CA} = \sqrt{3}V_p/30^\circ$	$I_c = I_{AB}/+120^\circ$	<b>Autotransformer</b> $\rightarrow$ transfer large apparent Power for Step-down. $\rightarrow \frac{V_1}{V_2} = \frac{N_1+N_2}{N_2} = \frac{I_2}{I_1}$ also apply for phasor	
$V_{an} = V_p/0^\circ$	$V_{bc} = V_p/-120^\circ$	<b>Step-up</b>	<b>Application</b> $\rightarrow$ Transformer as an Isolation device $\Rightarrow$ To provide Isolation $\rightarrow$ Turn ratio $f_s = 1$ . Cuts prevent any DC Voltage in one stage from effecting the DC bias of the next stage.) <b>Impedance Matching</b> $\rightarrow$ Max Power transfer
$V_{bn} = V_p/+120^\circ$	$I_a = I_{AB}\sqrt{3}/-30^\circ$	$\frac{V_1}{V_2} = \frac{N_1}{N_1+N_2} = \frac{I_2}{I_1}$	
$V_{ca} = V_p/0^\circ$	$I_b = I_{AB}/-120^\circ$		
Same as phase voltages			
<b>Chapter 14</b>			
<b>Frequency Response</b> $\Rightarrow$ Amplitude / Phase angle remain constant and vary the frequency.			
$H(j\omega) = \frac{Y(j\omega)}{X(j\omega)}$	<b>Four type of frequency Responce</b> $\rightarrow H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$ <b>Voltage gain.</b>		
	$H(j\omega) = \frac{I_o(j\omega)}{I_i(j\omega)}$ <b>Current gain</b> , $H(j\omega) = \frac{V_o(j\omega)}{I_i(j\omega)}$ <b>transistor Impedance.</b>		
<b>The Gain G</b>	<b>Bode Plot +</b>		
$G_{BB} = 10 \log_{10} \frac{P_2}{P_1} = 10 \log_{10} \left( \frac{\frac{V_L}{R_L}}{\frac{V_T}{R_T}} \right)$	<b>1st factor</b> $\rightarrow$ Constant B. $\rightarrow (j\omega)$ . For the gain K as shown $\phi = 0, K > 0$ as shown $\phi = 180, K < 0$		
$\text{If } R_1 = R_2 \text{ then } G_{BB} = 20 \log_{10} \frac{V_L}{V_1} = 20 \log_{10} \frac{I_2}{I_1}$			
<b>4. <math>z_m = c.c.; p_n = c.c.</math></b>	<b>Type 1</b> $\rightarrow$ $H(j\omega) = \frac{1}{1 + j\omega/\omega_n}$ <b>Exact</b>		
	<b>Type 2</b> $\rightarrow$ $H(j\omega) = \frac{1}{1 + j\omega/\omega_n} + \frac{1}{1 + j\omega/\omega_d}$ <b>Approximate</b>		
	<b>Type 3</b> $\rightarrow$ $H(j\omega) = \frac{1}{1 + j\omega/\omega_1} \cdot \frac{1}{1 + j\omega/\omega_2}$ <b>Pole</b>		
	<b>Type 4</b> $\rightarrow$ $H(j\omega) = \frac{1}{1 + j\omega/\omega_1} \cdot \frac{1}{1 + j\omega/\omega_2} \cdot \frac{1}{1 + j\omega/\omega_3}$ <b>Approximate</b>		
<b>Series Resonance</b> $\rightarrow$ Resonance Occur when $\text{Im}(Z) = 0 \Rightarrow$ Resonance frequency $\omega_0$			
The reactive and capacitive Reactance are equal.	$\omega_0 L = \frac{1}{\omega_0 C}$	<b>Passive filter</b> $\rightarrow$ Contain only passive elements $R, L$ and $C$ pass signal with desire frequency.	
In resonance $\rightarrow$ It's purely resistive $\rightarrow Z = R$ , The Voltage $V_b$ and $I$ are in phase		<b>Lowpass filter</b> $\rightarrow$ Pass low frequencies and reject high frequencies	
Highest Power dissipated at Resonance $\rightarrow P_{CW_0} = \frac{1}{2} I_{max}^2 R = \frac{1}{2} \frac{V_m^2}{R}$		$H(j\omega) = \frac{1}{1+j\omega RC}$ ; Let off frequency $\omega_0 = \frac{1}{RC}$ or set $H(j\omega) = \frac{1}{\sqrt{2}}$	
Half Power frequency $\rightarrow I(W_1) = I(W_2) = \frac{I_{max}}{\sqrt{2}}$		<b>Highpass filter</b> $\rightarrow$ Passes high frequencies and rejected low frequencies	
$W_1 = \frac{R}{2L} \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$ ; $W_2 = \frac{R}{2L} \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$		$H(j\omega) = \frac{j\omega RC}{1+j\omega RC}; W_C = \frac{1}{\omega C}$	
Half Power Bandwidth $\rightarrow BW = W_2 - W_1 = \frac{R}{L}$	<b>Bandstop filter</b> $\rightarrow$ Passes frequency outside a frequency band and block frequency within the band.	$H(j\omega) = \frac{R}{R + j(\omega - \frac{1}{\omega_C})}$	
Relation Between $\beta/Q$ $\rightarrow BW = \frac{R}{L} = \frac{\omega_0}{Q} \Rightarrow Q = \frac{\omega_0}{BW}$	<b>high Q circuit</b> when $Q \geq 10$	$H(j\omega) = \frac{j(\omega L - 1/C\omega)}{R + j(\omega L - 1/C\omega)}$	
$V_L = \frac{V_m}{R} \omega_0 L = \frac{V_m}{R} \frac{1}{\omega_0 C} = V_C$	for Resonance $\rightarrow$ The inductor / capacitance can be much more than the source voltage.	$H(j\omega) = \frac{1}{R + j(\omega L - 1/C\omega)}$	
<b>Parallel Resonance</b> $\rightarrow$ Resonance Occur when $\text{Im}(Y) = 0; \omega_0 = \frac{1}{\sqrt{LC}}$		<b>Bandpass filter</b> $\rightarrow$ Cascading low pass filter and high pass filter and an inverter gain $-R_f/R_i$	
Current instead of Voltage	<b>Energy In Inductor</b> $\rightarrow \frac{1}{2} L I^2$	<b>First Order</b> $\rightarrow H(j\omega) = -\frac{R_f}{R_i} \left( \frac{j\omega/w_0}{1+j\omega/w_0} \right); w_0 = \frac{1}{R_i C_j}$	
$\omega_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$	<b>Band Reject Filter</b> $\rightarrow$ Parallell combination of a low pass filter and a high pass filter.	<b>First Order high pass</b> $\rightarrow H(j\omega) = -\frac{R_f}{R_i} \left( \frac{j\omega/w_0}{1+j\omega/w_0} \right); w_0 = \frac{1}{R_i C_j}$	
$\omega_2 = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$	<b>Note</b> $\rightarrow W_1 = 2\pi f_1; W_2 = 2\pi f_2$	<b>Center frequency</b> $\rightarrow w_0 = \sqrt{w_1 w_2}$	
$BW = \omega_2 - \omega_1 = \frac{1}{RC}$	for Band Reject $W_1 = \frac{1}{(R C_1)}$ corner cut-off frequency	$BW = W_2 - W_1 \rightarrow R_f \left( \frac{W_2}{W_1 + w_0} \right)$	
$Q = \frac{\omega_0}{BW} = \omega_0 RC = \frac{R}{\omega_0 L}$	$W_2 = \frac{1}{(R C_2)}$ upper cut-off frequency	<b>Pass sum gain</b> $K = \frac{R_f}{R_i} \left( \frac{W_2}{W_1 + w_0} \right)$	



