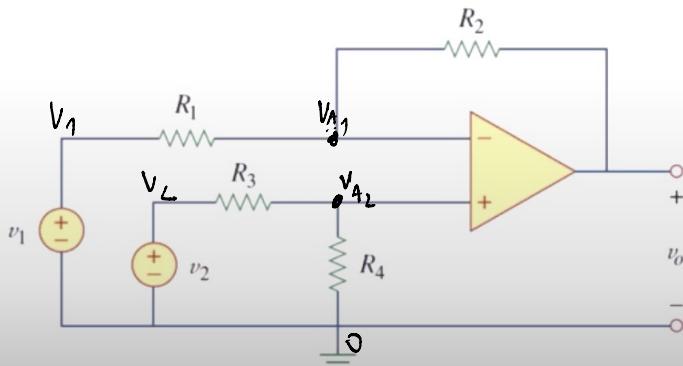




Q1. For the difference amplifier circuit, please derive the equation below. (8 points)

$$v_o = \left( \frac{R_2}{R_1} + 1 \right) \frac{R_4}{R_3 + R_4} v_2 - \frac{R_2}{R_1} v_1$$



At node  $V_{A_1}$   $\frac{V_{A_1} - V_1}{R_1} + \frac{V_{A_1} - V_o}{R_2} = 0$

$V_{A_1} = V_{A_2}$

At node  $V_{A_2}$   $\frac{V_{A_2} - V_2}{R_3} + \frac{V_{A_2}}{R_4} = 0$

$$\frac{V_A - V_2}{R_3} + \frac{V_A}{R_4} = 0$$

$$V_A \left( \frac{R_4 V_2 + R_3 V_A}{R_3 R_4} \right) = \frac{V_2}{R_3}$$

$$V_A = \frac{R_3 R_4}{R_4 + R_3} \left( \frac{V_2}{R_3} \right)$$

$$V_A = \frac{+V_2 R_4}{R_4 + R_3}$$

$$\frac{\left(\frac{V_2 R_4}{R_4 + R_3}\right) - V_1}{R_1} + \frac{\left(\frac{V_0 R_4}{R_4 + R_3}\right) - V_0}{R_2} = 0$$

$$= \frac{V_2 R_4}{R_1 (R_4 + R_3)} - \frac{V_1}{R_1} + \frac{V_0 R_4}{R_2 (R_4 + R_3)} - \frac{V_0}{R_2} = 0$$

$$\frac{V_0}{R_2} = \left( \frac{R_2 R_4 V_2 + R_1 R_4 V_2}{R_1 R_2 (R_4 + R_3)} \right) - \frac{V_1}{R_1}$$

$$V_0 = \left( \frac{R_2}{R_1} + 1 \right) \frac{R_4 V_2}{R_3 + R_4} - \frac{V_1}{R_1} R_2$$


~~X~~

Q3. The circuit model of a dc voltage source is shown below. The following voltage measurements are made at the terminals of the source: (1) With the terminals of the source open, the voltage is measured at 50 mV, and (2) with a  $15\text{ M}\Omega$  resistor connected to the terminals, the voltage is measured at 48.75 mV. All measurements are made with a digital voltmeter that has a meter resistance of  $10\text{ M}\Omega$ . (10 points)

$$V_L$$

- (a) What is the internal voltage of the source  $v_s$  in millivolts?  
 (b) What is the internal resistance of the source  $R_s$  in kilo-ohms?


$$V_s = 50\text{ mV}$$

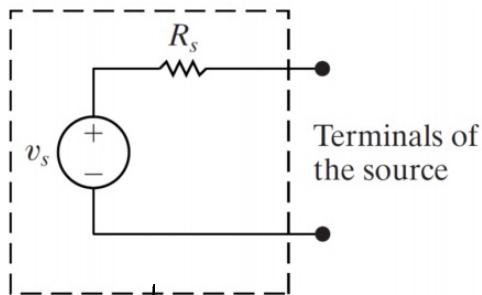

Q3  
 when a practical voltage source is connected to  
 the load then


$$V_L = \left( \frac{R_L}{R_s + R_L} \right) V_s$$

1st Case

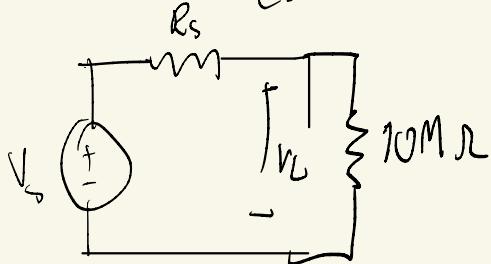

$$50\text{ mV} = \frac{10V_s}{R_s + 10} \rightarrow (2)$$

2nd Case

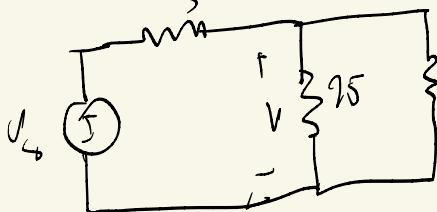


$$10\text{ mV} = 48.75 = \frac{6V_s}{R_s + 6}$$

Q4. The rheostat  $R_o$  in the circuit below has been adjusted so that the maximum power is delivered to  $R_o$ . (18 points)

(a) Find the value of  $R_o$ .

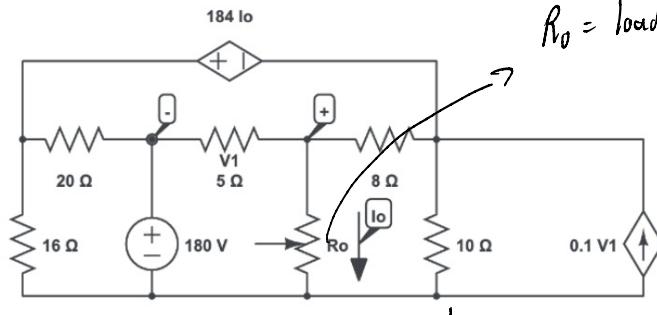
(b) Find the maximum power delivered to  $R_o$ .



$R_o = \text{load resistance } j \text{ as if consume power output from the circuit}$

Max power delivered to the load when  $R_o = R_{TH}$

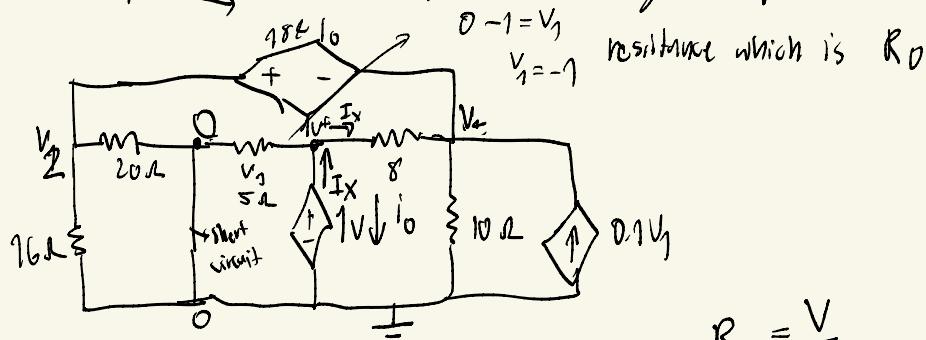(a) Find  $R_{TH}$  → Close all independent sources, and open circuit load



$$\text{Node Analysis at Supermesh } V_2 / V_4 \rightarrow R_{TH} = \frac{V}{I_x}$$

$$\frac{V_2}{16} + \frac{V_2 - 0}{20} + \frac{V_4 - 1}{8} + \frac{V_4}{10} - 0.1V_1 = 0 \rightarrow (1)$$

$$\text{Also } V_2 - V_4 = 184 - I_o \rightarrow (2); \text{ also } V_1 = 9 - 0$$

$$\text{Node Analysis at 1} \rightarrow \frac{9 - 0}{5} - I_x + \frac{1 - V_4}{8} = 0 \rightarrow (3)$$

$$I_x = \frac{1}{5} + \frac{1 - V_4}{8} \rightarrow (4)$$

$$\text{also } I_x = -I_o \rightarrow I_o = -\frac{I}{x}$$

Solve for  $I_x \rightarrow \text{get } R_{TH}$


$$R_{TH} \Rightarrow 27.45 \Omega$$

~~if~~


Q4. The rheostat  $R_o$  in the circuit below has been adjusted so that the maximum power is delivered to  $R_o$ . (18 points)

(a) Find the value of  $R_o$ .

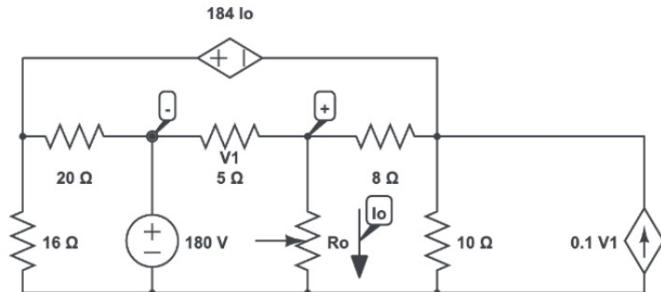(b) Find the maximum power delivered to  $R_o$ .



Find  $V_{TH}$  or  $V_{OC}$

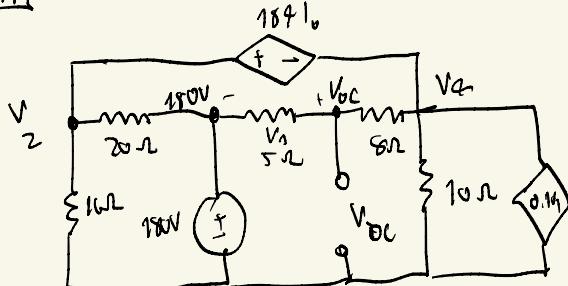

Make sure to  
write down equation

$$\frac{V_2}{16} + \frac{V_2 - 180}{20} + \frac{V_4 - V_{OC}}{8} + \frac{V_4}{10} - 0.1V_1 =$$

$$V_1 = V_{OC} - 180$$


Q5. Inductors are initially charged and are connected to the black box at  $t = 0$ . If  $i_1(0) = 6 \text{ A}$ ,  $i_2(0) = -3 \text{ A}$ , and  $v(t) = 50e^{-100t} \text{ mV}$  when  $t \geq 0$ , please answer (a)-(d). (16 points)

(a) The energy initially stored in each inductor.

(b) The total energy delivered to the black box from  $t = 0$  to  $t = \infty$ .

(c)  $i_1(t)$  and  $i_2(t)$  when  $t \geq 0$ .

(d)  $i(t)$ ,  $t \geq 0$ .

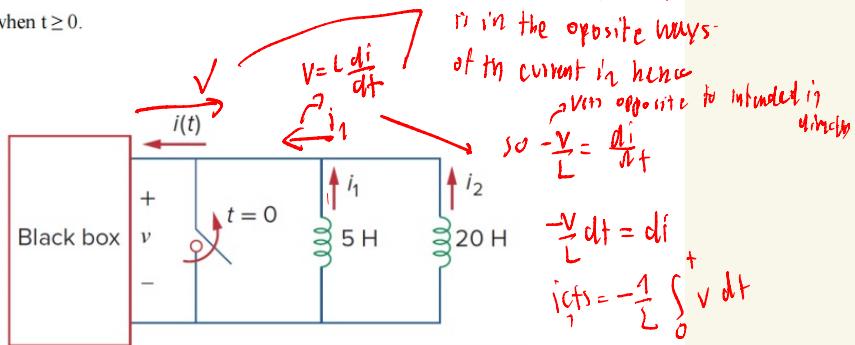

$$\begin{aligned}
 \text{(a)} \quad \text{for each inductor} \rightarrow W_{\text{inductor at } 5 \text{ H}} &\rightarrow \frac{1}{2} L i^2 = \frac{1}{2} 5 (6)^2 \\
 &= \frac{1}{2} \times 5 \times 36 \\
 &= 90 \text{ J}
 \end{aligned}$$

$$W_{\text{inductor at } 20 \text{ H}} \rightarrow \frac{1}{2} L i^2 = \frac{1}{2} (20) (-3)^2$$

$$\frac{5 \times 20}{5 + 20} = \frac{100}{25} = 4$$

$$\begin{aligned}
 \text{(b.)} \quad W &= W_1 + W_2 \rightarrow \text{All energy will be transfer to the black box} \\
 &\checkmark
 \end{aligned}$$

$$\Rightarrow W = W_1 + W_2 = 90 + 90$$

$$= 180 \text{ J}$$

(c.)  $V = L \frac{di_1}{dt} = V dt + L di$   $\rightarrow V(t) = \text{negative Q}$



for inductor = 5 or init

 $\frac{V}{L} dt = di$ 
 $i(t) = \int_0^t V dt$ 
 $i(0) = 0 \quad \rightarrow \quad = \frac{1}{5} \int_0^t 50 e^{-100t} dt + i(0)$ 
 $= \frac{1}{5} \left( -\frac{1}{100} \right) \left[ e^{-100t} - e^{-100(0)} \right]$ 
 $= \frac{1}{10} \left[ e^{-100t} - 1 \right]$ 
 $\therefore v(t) = MV$

$i_1(t) = 1 \times 10^{-t} (e^{-100t} - 1) + b$ 

$i(t) = i_1(t) + i_2(t) \Rightarrow i_2(t) \text{ solve the same way as } i_1(t)$

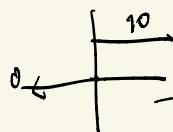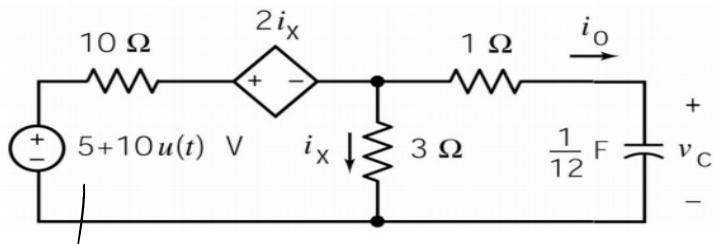Q6. Please determine a capacitor current  $i_0$  when  $t > 0$ . (18 points)




$$\text{when } t > 0 = 5 + 10 = 15$$

$$\text{when } t < 0 = 5$$

Rc circuit with step input

find  $i_C$
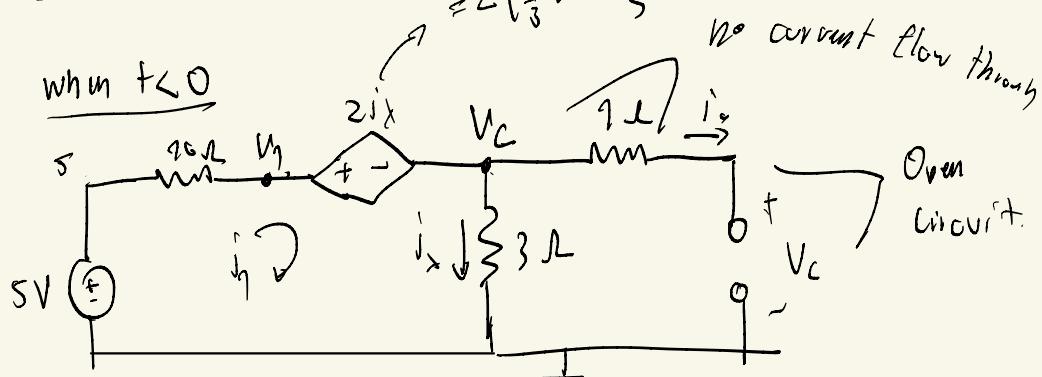
$$= 2 \left( \frac{1}{3} \right) = \frac{2}{3}$$



$$i_{C(0^+)} = i_{C(0^-)} = 0$$

$$\text{also } i_X = i_1$$

$$\text{KVL at } i_1 \quad 10i_1 + 2i_X + 3i_1 - 5 = 0$$

$$10i_X + 2i_X + 3i_X - 5 = 0$$

$$15i_X = 5$$

$$i_x = \frac{1}{3} A \rightarrow (1)$$

level at  $V_2$  supernode  $V_2$  and  $V_1$


$$\frac{V_1 - 5}{10} + \frac{V_C}{3} = 0 \rightarrow (2)$$

$$\text{also } V_1 - V_C = 2i_x = V_1 - V_C = \frac{2}{3} \rightarrow (3)$$

$$\text{also } i_x = \frac{V_C - 0}{3} = \frac{1}{3}(3) = V_C$$

$$V_C = 1$$
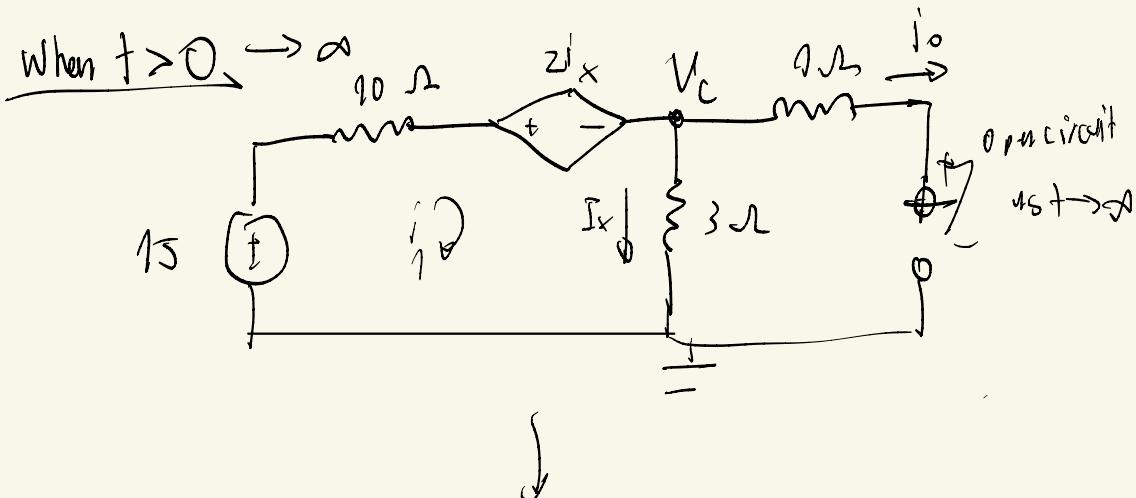
$$V_C(0^+) = V_C(0^-) = V_o = 1 \text{ V}$$



same KVL  $i_1$  also  $i_1 = I_x$

$$10i_1 + 2i_x + 3i_1 - 15 = 0$$

$$10i_x + 2i_x + 3i_x - 15 = 0$$

$$15i_x = 15$$

$$i_x = 1 \text{ A}$$


also  $I_x = \frac{V_C - 0}{3}$

$$1 \times 3 = V_C$$

$$3 = V_C(\infty)$$

Response for  $R_C$  circuit with step input  $\rightarrow V(\infty) + [V(0+) - V(\infty)] e^{-\frac{t}{RC}}$

$T \Rightarrow RC \rightarrow$

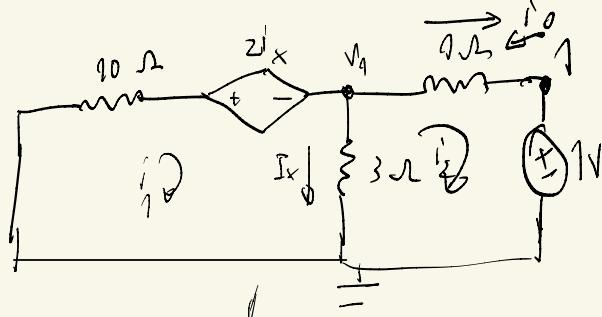

Mesh analysis

$$10i_1 + 2i_x + 3(i_1 - i_2) = 0$$

$$\dot{i}_x = i_1$$

$$10I_x + 2I_x + 3I_x - 3i_2 = 0$$

$$13I_x - 3i_2 = 0 \rightarrow (1)$$

From mesh 2  $\rightarrow i_2 + 1V + 3(i_2 - I_x) = 0$

$$\therefore i_2 = -i_0$$

$$4i_2 - 3I_x = -1V \rightarrow (2)$$

$$i_x = i_0 = \frac{13}{43}$$

$$T = RC \Rightarrow \frac{13}{43} \left( \frac{1}{12} \right) = \frac{13}{516},$$

$$= 0.025$$


$$V(t) = \beta + (1-\beta)e^{-\frac{t}{P}}$$

$$= 3 - 2e^{-4+}$$


$$i(t) = C \frac{dV}{dt} = \frac{1}{R} \left[ 8e^{-4t} \right]$$

$$= \frac{2}{3} e^{-4t}$$
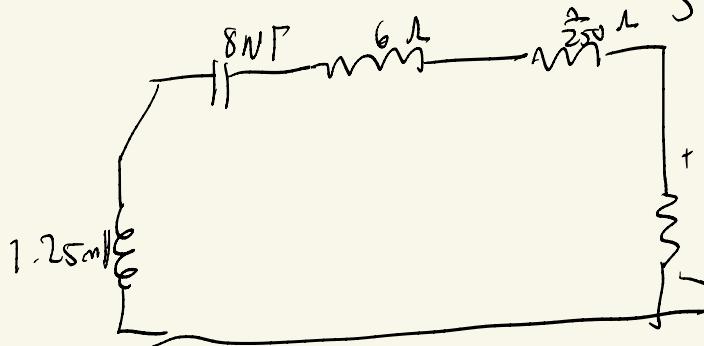
$$\text{when } t < 0 \Rightarrow V(O^+) = V(O^-) = \frac{2}{3}$$



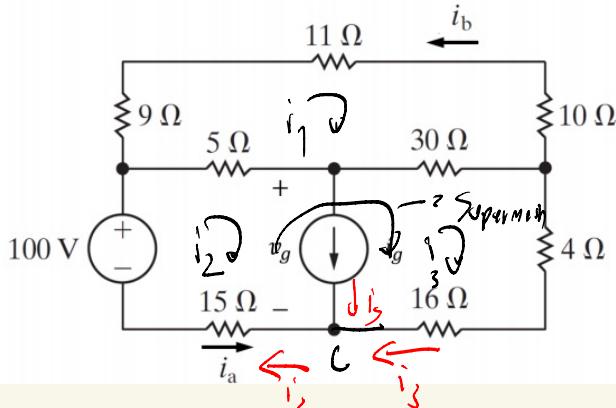1. The currents  $i_a$  and  $i_b$  in the circuit are 4 A and -2 A respectively. Find  $i_g$  and  $v_g$ . [8 points]



Supermesh between  $i_2$ ,  $i_3$ .

From KCL at C

$$-i_g - i_3 + i_2 =$$

$$i_g = i_2 - i_3 \quad \dots \rightarrow (1)$$

Supermesh  $\rightarrow$

$$i_2 = i_g ; \quad i_g = 4 ; \quad i_b = -2$$

$$5(i_2 - i_1) + 30(i_3 - i_1) + 4i_3 + 16i_3 + 15i_2 - 100 = 0$$

~~$$5i_2 - 5i_1 + 30i_3 - 30i_1 + 4i_3 + 16i_3 + 15i_2 = 100$$~~

$$-35i_1 + 20i_2 + 50i_3 = 100 \rightarrow (2)$$

Mesh 1

$$11i_1 + 10i_g + 30(i_1 - i_3) + 5(i_1 - i_2) + 9i_1 = 0$$

$$i_1 = -i_b = -(-2) = 2 \rightarrow (3)$$

Sub  $i_1$  to (3)

$$22 + 20 + 60 - 30i_3 + 10 - 5i_2 + 18 = 0$$

$$-30i_3 - 5i_2 = -130 \rightarrow (4)$$

$$-35i_1 + 20i_2 + 50i_3 = 100 \rightarrow (2)$$



$$i_1 = 2 \rightarrow 20i_2 + 50i_3 = 170 \rightarrow (5)$$

Want to solve (4) (5)

$$\Rightarrow i_2 = -4 ; i_3 = 5$$

$$i_2 = i_2 = -4$$

$$i_9 = i_2 - i_3 = -4 - 5 = -9 \text{ A}$$

From mesh j<sub>2</sub>

$$5(i_2 - i_1) + V_g + 15i_2 - 100 = 0$$


$$5i_2 - 5i_1 + V_g + 15i_2 - 100 = 0$$

$$-20 - 10 + V_g - 60 - 100 = 0$$

$$V_g = 140 \text{ V}$$

2. (a) Use the mesh-current method to find the branch currents in  $i_a \sim i_e$  in the circuit below. [8 points]

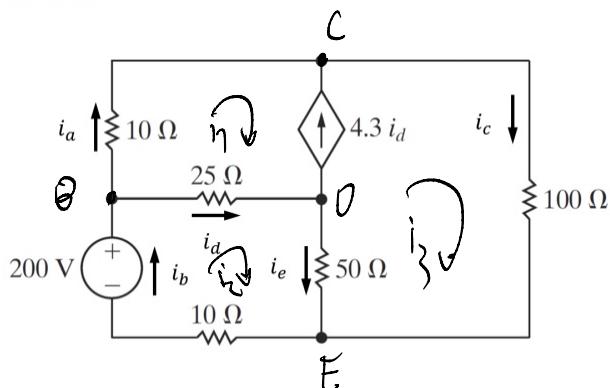(b) Check your solution by showing that the total power generated in the circuit equals the total power consumed. [8 points]



Mesh  $i_1/i_3$   $\rightarrow$  Super mesh

$$\text{also } i_1 = i_a \quad i_c = i_3$$

KCL at C  
 $-i_1 - 4.3i_d + i_c = 0$   
 $-i_a - 4.3i_d + i_c = 0$

$$i_c = i_a + 4.3i_d \quad \rightarrow (1)$$

for supermesh  $i_1/i_3$       or       $i_3 = i_1 + 4.3i_d$

$$100i_3 + 50(i_3 - i_2) + 25(i_1 - i_2) + 10i_1 = 0$$

$$100i_3 + 50i_3 - 50i_2 + 25i_1 - 25i_2 + 10i_1 = 0$$

$$35i_1 - 75i_2 + 150i_3 = 0 \rightarrow (2)$$

Y

$$\underline{\text{Mesh } i_2} \quad 25(i_2 - i_1) + 50(i_2 - i_3) + 10i_2 - 200 = 0$$

$$25i_2 - 25i_1 + 50i_2 - 50i_3 + 10i_2 - 200 = 0$$

$$-25i_1 + 85i_2 - 50i_3 = 200 \rightarrow (3)$$

$$\underline{\text{also KCL at } \beta} \quad i_6 = i_a + i_d \Leftrightarrow i_6 = i_1 + i_d \rightarrow (4)$$

$$\underline{\text{KCL at } \delta} \quad -i_d + 4,3i_d + i_e = 0 \rightarrow$$

$$3,3i_d = -i_e$$

$$i_d = \frac{-10}{33}i_e \rightarrow (5)$$

$$\underline{\text{KCL at } A} \quad -i_e - i_3 + i_2 = 0$$

$$i_2 = i_e + i_3$$

$$\Rightarrow i_e = -3,3i_d$$

$$i_2 = -3,3i_d + i_3$$

$$i_d = \frac{i_3 - i_2}{3,3} \rightarrow (6)$$

$$\text{Sub (6) to (1)} \quad i_3 = i_1 + 4.3 \left( \frac{i_3 - i_2}{3.3} \right)$$

$$= i_3 = i_1 + \frac{43}{33} i_3 - \frac{43}{33} i_2$$

$$0 = i_1 - \frac{43}{33} i_2 + \frac{10}{33} i_3 \rightarrow (7)$$

Solve (2) (3) (7) give

$$i_1 = 5.7 \text{ A}; i_2 = 4.6 \text{ A}; i_3 = 0.97 \text{ A}$$

Hence

$$i_d = 5.7 \text{ A}; i_c = 0.97 \text{ A}$$

$$\text{also } i_c = i_1 + 4.3 i_d$$

$$\frac{i_c - i_1}{4.3} = i_d \rightarrow i_d = -1.1 \text{ A} \rightarrow i_d$$

$$\text{also } i_e = -3.3 i_d \Rightarrow 3.63 \text{ A}$$

$$i_B \Rightarrow i_a + i_d = 5.7 - 1.1$$

$$j_b \Rightarrow 4.6 \text{ A}$$

## 6) kirchhoff power law.

Power dissipated

$$\checkmark \quad \text{total power generated} = \text{total power consumed}$$

by the independent source

by All resistors

Voltage Source / Current Source

check Power dissipated

$$\underline{\text{Power dissipated}} \rightarrow \sum P_{\text{dis}} \Rightarrow \sum I^2 R_L$$

= Come all current with their connected

Resistance  $R_L$  - from independent source

$$\underline{\text{Power generated}} \rightarrow \text{Supply} = \sum = P_{\text{voltage}} + P_{\text{current}}$$

$$P_{\text{voltage}} = V j_b = -(200) A \cdot b$$

$$= -920 \text{ W}$$

Negative as its supply

$$P_{\text{current}} = V_{\text{current}} \times (4.3 I_d)$$

$$V_{\text{current from loop } i_7} = 84.5 (4.3 [-1, 1])$$
$$\approx -399.685 \text{ V}$$

$$P_{\text{total}} \Rightarrow -399.685 \leftarrow P_{\text{loss}}$$


negative as its man

supply power

3. The variable resistor ( $R_o$ ) in the circuit is adjusted until it absorbs maximum power from the circuit.


(a) Find the value of  $R_o$ . [12 points]

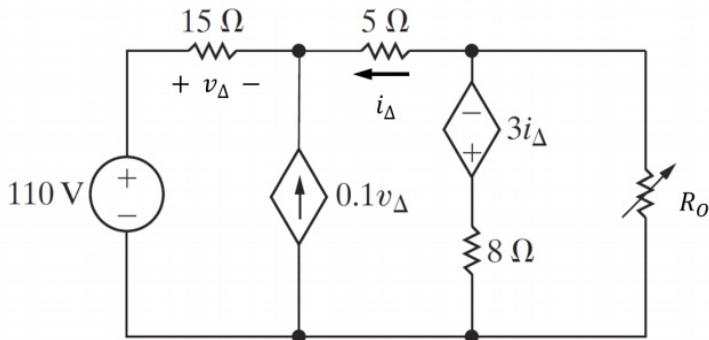(b) Find the maximum power delivered to  $R_o$ . [4 points]




Max power transfer to the load when  $R_{TH} = R_o$

(q.) Hence  $R_o = R_{TH}$

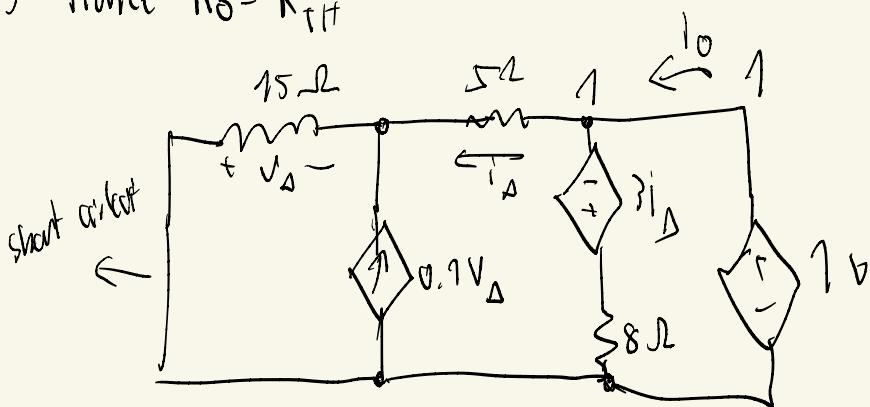

$$R_{TH} = \frac{V}{I_0} \rightarrow \text{Apply } 1V = \frac{1}{I_0}$$

↓

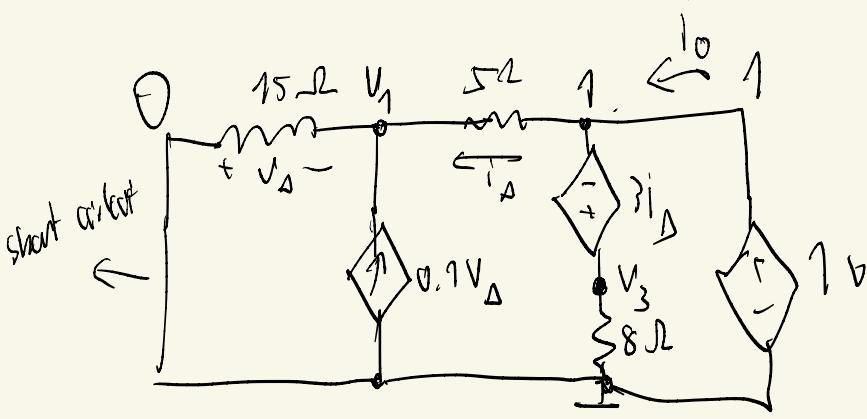

$$R_{TH} = \frac{V}{i_0} \rightarrow \text{Apply } 1V = \frac{1}{i_0}$$

find  $i_0$   
At node  $V_1$

$$15 \left( \frac{V_1 - 0}{15} - 0.1V_\Delta + \frac{V_1 - 1}{5} = 0 \right)$$

$$V_1 - 1.5V_\Delta + 3V_1 - 3 = 0$$

$$4V_1 - 3 - 1.5V_\Delta = 0 \rightarrow (1)$$

$$\text{at } V_1 \quad 0 - V_1 = V_\Delta$$

$$4V_1 - 3 + 1.5V_1 = 0$$

$$5.5V_1 - 3 = 0 \rightarrow (2)$$

$$V_1 = \frac{3}{5.5} \quad \checkmark$$

$$\text{also } i_A = \frac{1 - V_1}{5} = \frac{1 - \frac{3}{5.5}}{5} = \frac{1}{11}$$

Super node  $V_2/V_3$

$$\frac{1 - V_1}{5} + \underbrace{\frac{V_3 - 0}{8}}_{\rightarrow (2)} - i_o = 0 \rightarrow (2)$$

$$\text{also } V_3 - 1 = 3i_A$$

$$V_3 = 3\left(\frac{1}{11}\right) + 1 = \frac{14}{11} V$$

solve (2)


$$\frac{1}{11} + \frac{\frac{14}{11}}{8} = i_o$$

$$i_o = \frac{1}{8}$$


Hence  $R_{TH} = \frac{1}{i_o} = \frac{1}{\frac{1}{8}} = \underline{\underline{8}}$   $\Rightarrow = R_o$

(b) Find the maximum power delivered to  $R_o$ . [4 points]

6.)

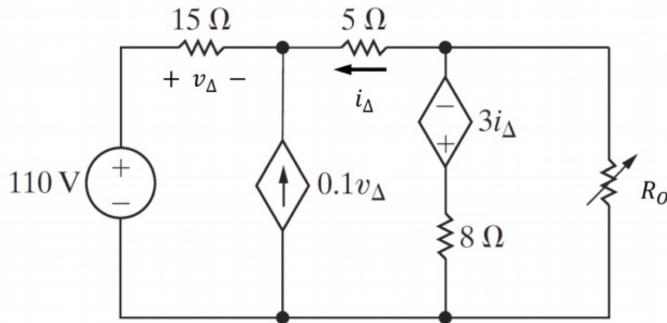
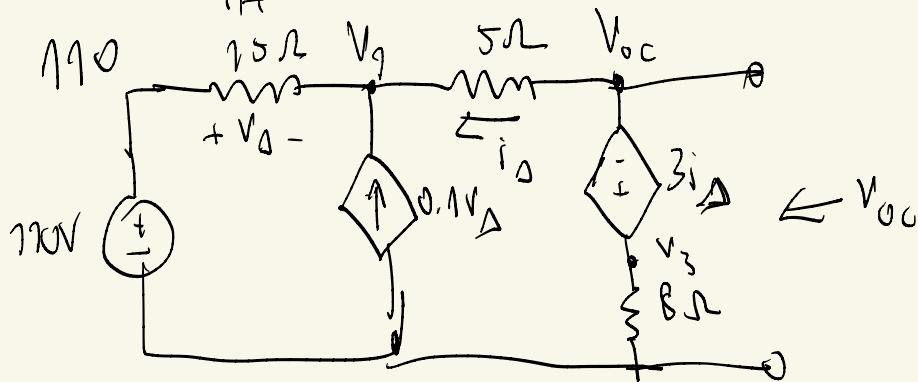
$$P_{\max} = \frac{V_{TH}^2}{4R_{TH}} \Rightarrow \text{Need } V_{TH} = V_o,$$



Supernode  $V_{oC}$  and  $V_3$

$$40 \left( \frac{V_{oC} - V_1}{5} + \frac{V_3 - 0}{8} = 0 \right)$$

$$8V_{oC} - 8V_1 + 5V_3 = 0 \rightarrow (1)$$

$$\text{also } \rightarrow i_D = \frac{V_{OC} - V_1}{5\Omega} \quad i_D = \frac{V_{OC} - 110 + V_\Delta}{5\Omega}$$

$$\text{so } \rightarrow V_3 - V_{OC} = 3i_D$$

solve at Node  $V_1$   $\left( \frac{V_1 - 110}{15} + \frac{V_1 - V_{OC}}{5} - 0.1V_\Delta = 0 \right) 15$

$$V_1 - 110 + 3V_1 - 3V_{OC} - 1.5V_\Delta = 0$$

$$4V_1 - 3V_{OC} - 1.5V_\Delta = 110 \rightarrow (2)$$

$$\text{also } 110 - V_1 = V_\Delta$$

$$V_1 = 110 - V_\Delta$$

Sub to (1)/2

$$8V_{OC} - 8(110 - V_\Delta) + 5V_3 = 0 \rightarrow (3)$$

$$4(110 - V_\Delta) - 3V_{OC} - 1.5V_\Delta = 110 \rightarrow (4)$$

$$8V_{OC} - 880 + 8V_D + 5V_3 = 0 \quad V_3 = V_{OC} + 3V_D$$

$$(5) \quad 8V_{OC} + 8V_D + 5V_3 = 880 \quad = V_{OC} + 3\left(\frac{V_{OC} - 120 + V_D}{5}\right)$$

$$-3V_{OC} - 5.5V_D = -330 \quad \downarrow$$

$$(6) \quad = V_{OC} + \frac{3}{5}V_{OC} - \frac{330}{5} + \frac{3V_D}{5}$$

from (5)  $\rightarrow 8V_{OC} + 8V_D + 5\left(V_{OC} + \frac{3}{5}V_{OC} - \frac{330}{5} + \frac{3V_D}{5}\right) = 880$

$$\cancel{8V_{OC} + 8V_D + 5V_{OC}} + \cancel{3V_{OC}} - 330 + 3V_D = 880$$

$$16V_{OC} + 11V_D = 1210 \rightarrow (7)$$


$$V_{OC} = 55 \text{ V} \quad V_D = 30$$

$$P_{MAX} = \frac{(V_{TH})^2}{4R_{TH}} \Rightarrow \frac{(55)^2}{4(4)} = 189.0625 \text{ W}$$

4. Show that if  $\Delta R \ll R$ , the output voltage of the op amp is approximately

$$v_o \approx \frac{R_f(R + R_f)}{R^2(R + 2R_f)}(-\Delta R)v_{in}$$

for the circuit below. [20 points]

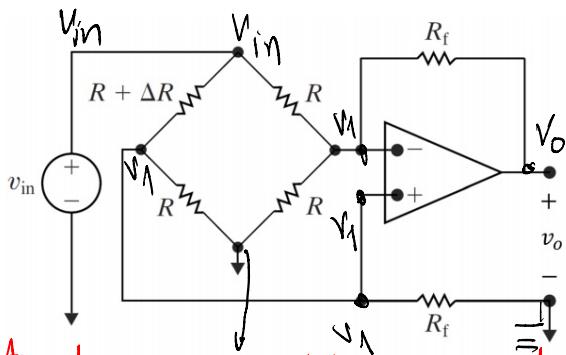

Arrow down mean ; Connected to the ground.

At node  $V_1$  for inverting amplifier.

$$\frac{V_1 - V_{in}}{R} + \frac{V_1}{R} + \frac{V_1 - V_o}{R_f} = 0$$

$$\frac{V_1}{R} + \frac{V_1}{R} + \frac{V_1}{R_f} = \frac{V_{in}}{R} + \frac{V_o}{R_f}$$

$$V_1 \left( \frac{2R_f + R}{RR_f} \right) = \frac{V_{in}}{R} + \frac{V_o}{R_f} \rightarrow (1)$$

KCL at node  $V_1$  for non inverting amplifier.

$$\frac{V_1 - 0}{R_t} + \frac{V_1}{R} + \frac{V_1 - V_{in}}{R + \Delta R} = 0 \rightarrow (2)$$

q/su

From (2)  $\rightarrow \left( \frac{V_1}{R_t} + \frac{V_1}{R} + \frac{V_1}{R + \Delta R} - \frac{V_{in}}{R + \Delta R} = 0 \right) (R_f)(R)(R_t + R)$

$$V_1(R)(R + \Delta R) + V_1(R_f)(R_f + \Delta R) + V_1(R_f)(R) - V_{in}(R_f)(R) = 0$$

$$V_1(R^2 + R\Delta R) + V_1(R_f R + R_f \Delta R) + V_1 R_f R = V_{in}(R_f)(R)$$

$$= V_1 (R^2 + R\Delta R + 2R_f R + R_f \Delta R) = V_{in}(R_f)R$$

$$V_1 = \frac{V_{in}(R_f)R}{R^2 + R\Delta R + 2R_f R + R_f \Delta R}$$

↓  
Plug to (1)

$$\frac{V_{in}(R_f)(R)}{R^2 + R\Delta R + 2R_f R + R_f \Delta R} \left( \frac{2R_f + R}{R_f} \right) \Rightarrow \frac{V_{in}}{R} + \frac{V_o}{R_f}$$

$$\frac{V_{in} (2R_f + R)}{R^2 + R\Delta R + 2R_f R + R_f \Delta R} \Rightarrow \frac{V_{in}}{R} + \frac{V_o}{R_f}$$

$$\frac{V_o}{R_f} = \frac{V_{in}(2R_f + R)}{R^2 + R\Delta R + 2R_f R + R_f \Delta R} - \frac{V_{in}}{R}$$

↓

$$\frac{V_o}{R_f} \Rightarrow \frac{V_{in} (2R_f R) - V_{in} (R^2 + R \Delta R + 2R_f R + R_f \Delta R)}{R (R^2 + R \Delta R + 2R_f R + R_f \Delta R)}$$

~~$2R_f R V_{in} + R^2 V_{in} - V_{in} R^2 - V_{in} R \Delta R - V_{in} 2R_f R - V_{in} R_f \Delta R$~~

$$R (R^2 + R \Delta R + 2R_f R + R_f \Delta R)$$

$$V_o \Rightarrow \frac{- (\Delta R) (R + R_f) R_f V_{in}}{R C R^2 + 2R R_f + R \Delta R + R_f \Delta R}$$


$R + R_f \gg \Delta R$  so fast such that two terminal are eliminated,

Hence  $V_o \Rightarrow \frac{(-\Delta R) R_f (R + R_f) V_{in}}{R^2 (R + 2R_f)}$


X

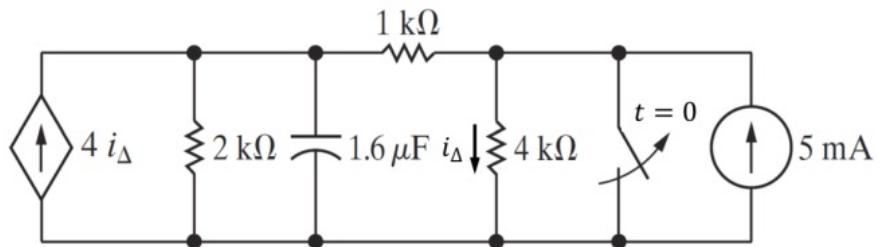5. The switch in the circuit below has been closed for a long time. The maximum voltage rating of the  $1.6 \mu\text{F}$  capacitor is 14.4 kV. How long after the switch is opened does the voltage across the capacitor reach the maximum voltage rating? Please follow steps below.

- Find Thevenin equivalent circuit seen from the capacitor. [10 points]
- Derive a capacitor voltage in the Thevenin circuit, i.e.  $RC$  circuit. [6 points]
- Find time for the capacitor to reach the maximum voltage rating. [4 points]



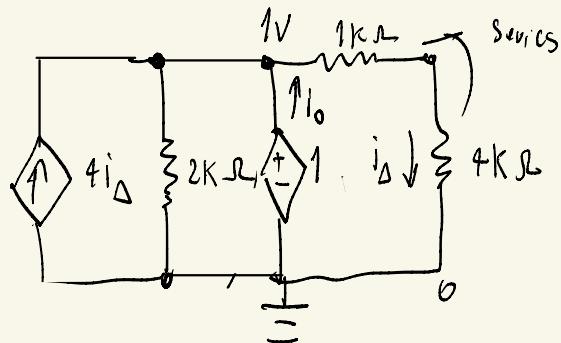(a.) Find  $R_{TH}$  Close all independent + source



$$k\text{CL at } 1V \rightarrow \left( -4i_\Delta + \frac{1-0}{2k\Omega} - i_0 + \frac{1-0}{4k\Omega} = 0 \right) 70k$$

$$-40i_1 + 5 - 10k i_0 + 2 = 0$$

$$+10k i_1 + 10k i_0 = 7 \rightarrow (1)$$

$$\text{Also } i_D = \frac{1-0}{5} = \frac{1}{5k} -$$


$$\text{Plug } i_D \text{ to (1)} \rightarrow \cancel{40\left(\frac{1}{5k}\right)} + 10i_0 = 7$$

$$\frac{1}{10} \left( 10i_0 = 7 - 8 \right)$$

$$i_0 = \frac{-1}{10k} = -1 \times 10^{-9}$$

Hence  $R_{TH} = \frac{1}{i_0} = \frac{1}{\frac{-1}{10}} = -10k\Omega$

Find  $V_{TH}$

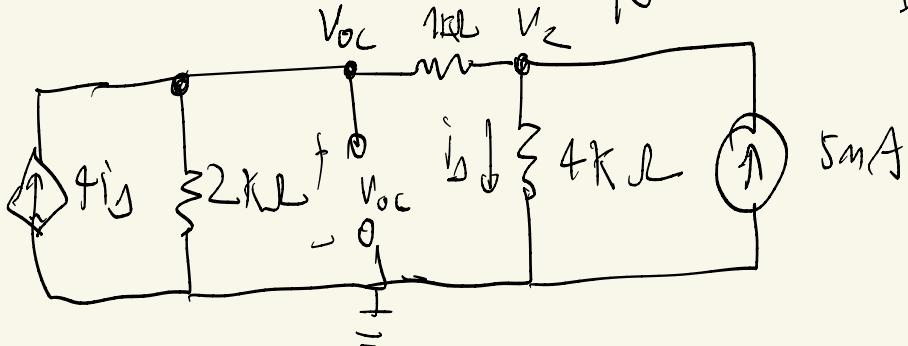

$$\left( -4i_D + \frac{V_{OC}}{2k} + \frac{V_{OC} - V_2}{1k} = 0 \right) 10k$$

$$-40k i_D + 5V_{OC} + 10V_{OC} - 10V_2 = 0$$

$$15V_{OC} - 10V_2 = 40k i_D \rightarrow CD$$

$$\text{KCL at } V_2 \rightarrow \left( \frac{V_2 - V_{OC}}{1K} + \frac{V_2}{4K} - SMA = 0 \right) 4K$$

$$4V_2 - 4V_{OC} + V_2 = 20$$

$$-4V_{OC} + 5V_2 = 20 \rightarrow (2)$$

$$4I_{SO} \rightarrow \frac{V_2 - 0}{4K} \rightarrow \text{Sub } f_{OC}$$

$$15V_{OC} - 10V_2 = 40K \left( \frac{V_2}{4K} \right)$$

$$15V_{OC} = 20V_2$$


$$V_2 = \frac{3}{7}V_{OC}$$

$$-4V_{OC} + 5 \left( \frac{3}{7}V_{OC} \right) = 20$$

$$-4V_{OC} + \frac{15}{7}V_{OC} = 20 \rightarrow \frac{1}{6}V_{OC} = 20$$

$$V_{OC} = V_{TH} = \sim 80V$$

\* Thevenin equivalent Circuit.

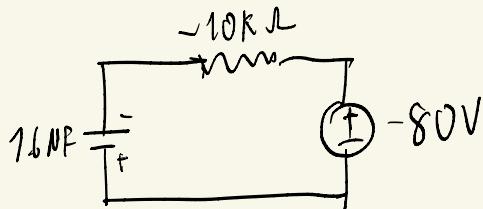


6.) Capacitor Voltage  $\rightarrow$

when  $t < 0$  or when  $t = 0$   $V_C(0^+) = V_C(0^-)$




Capacitor behave like a short

Circuit.

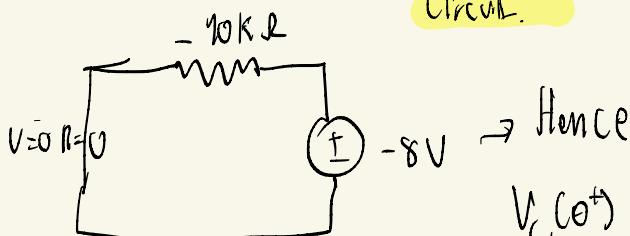

$$V_C(0^+) = V_C(0^-)$$

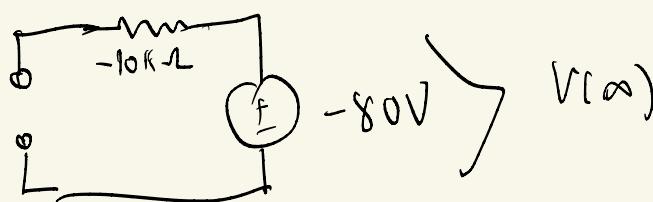when  $t \rightarrow \infty$  : Capacitor act as a open circuit.



$$T = R C = -10000 \times (1.6 \times 10^{-6}) = -16 \text{ ms}$$

$$V(t) = V_c(\infty) + [V_c(0^+) - V_c(\infty)] e^{-\frac{t}{T}}$$
$$= 14400 e^{62.5 t}$$

(ii) Max Voltage rating = 14.4 KV

$$= 14400$$


$$\text{Hence } 14400 + 80 = 80e^{62.5 t}$$

$$187 = e^{62.5 t}$$

$$62.5 t = \ln(187)$$

$$t = 83.02 \text{ ms}$$

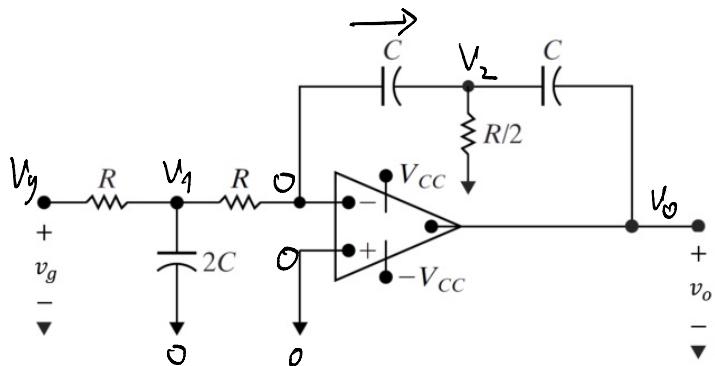6. Derive the differential equation that relates the output voltage to the input voltage for the circuit shown below. [20 points]



$$\text{KCL at } V_1 \rightarrow \frac{V_1 - V_g}{R} + 2C \frac{dV_1}{dt} + \frac{V_1}{R} = 0$$

$v_{in} = C \frac{dV}{dt}$  is the voltage across the capacitor from positive terminal to negative terminal.

KCL at 0

$$\frac{0 - V_1}{R} + C \frac{d(0 - V_2)}{dt} = 0$$

Positive terminal

Voltage across the capacitor from positive terminal to negative terminal  
has the same as node analysis

KCL at  $V_2$

$$-C \frac{d(0 - V_2)}{dt} + \frac{V_2}{R/2} + C \frac{d(V_2 - V_o)}{dt} = 0$$

from  $\rightarrow (1)$

$$V_g = 2RC \frac{dV_1}{dt} + 2V_1 \rightarrow (1)$$

from  $(2) \rightarrow$

$$V_1 = -R \frac{C \frac{dV_o}{dt}}{R/2} \rightarrow (2)$$

$$\text{from (3)} \rightarrow C \frac{dV_2}{dt} + 2 \frac{V_2}{R} + C \frac{dV_2}{dt} - C \frac{dV_0}{dt}$$

$$\frac{dV_0}{dt} = \frac{aV_2}{dt} + \frac{2}{RC} V_2 + \frac{dV_2}{dt}$$

$$\frac{dV_0}{dt} = 2 \frac{dV_2}{dt} + \frac{2V_2}{RC} \rightarrow (3)$$

$$\frac{a^2 V_0}{dt^2} = 2 \frac{d^2 V_2}{dt^2} + 2 \frac{dV_2}{dt} \frac{1}{RC}$$

from (2)

$$-\frac{V_1}{RC} = \frac{dV_2}{dt}$$

$$\text{so } \frac{d^2 V_2}{dt^2} = -\frac{1}{RC} \frac{dV_1}{dt}$$

$$\frac{d^2 V_0}{dt^2} = -\frac{2}{RC} \frac{dV_1}{dt} - \frac{2V_1}{RC^2}$$


$$= \frac{-1}{(RC)^2} \left( 2RC \frac{dV_1}{dt} + 2V_1 \right)$$

$$Z_{RC} = \frac{V_o}{V_1} = 2RC \frac{dV_1}{dt} + 2V_1$$


$$\boxed{\frac{d^2V_o}{dt^2} = -\frac{V_o}{R^2C^2}}$$
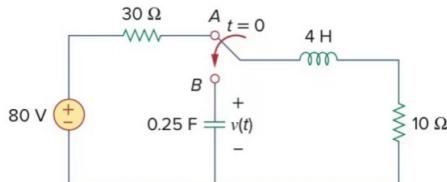
### Exercise 4.3 (20%)

The switch in the following figure moves from position A to position B at  $t = 0$  (please note that the switch must connect to point B before it breaks the connection at A, a make-before-break switch). Let  $v(0) = 0V$ , find  $v(t)$  for  $t > 0$ .




When  $t < 0$ .  $v(0) = 0V$

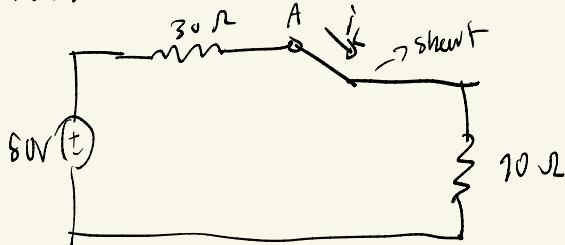

$$i(0^+) = i(0^-) = \frac{V}{R} = \frac{80V}{40\Omega} = 2A$$

When  $t > 0$

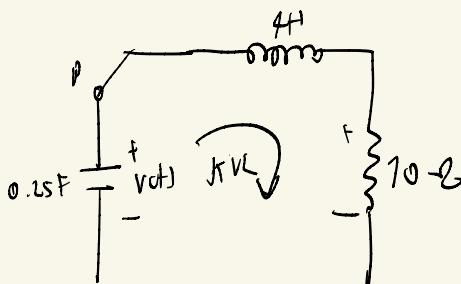

RLC series circuit

do KVL

$$V = L \frac{di}{dt}$$

$$\frac{V}{L} dt = di \rightarrow i = \int_{-\infty}^{\infty} \frac{V}{L} dt$$

$$i_C = C \frac{dv}{dt}$$

$$L \frac{di_L}{dt} + 10i_2 + V_C(t) = 0$$

$$\frac{i_C}{C} dt = dv$$

$$v_C = \int_{-\infty}^{\infty} \frac{i_C}{C} dt$$

$$= L \frac{d^2 i_L}{dt^2} + \frac{10}{L} \frac{di_L}{dt} + \frac{i_L}{C} = 0$$

$$\frac{d^2 i_L}{dt^2} + \frac{10}{L} \frac{di_L}{dt} + \frac{1}{LC} i_L = 0$$

V

Since response due to RLC series input

$$\rightarrow \frac{d^2 i_L}{dt^2} + \frac{5}{2} \frac{di_L}{dt} + i_L = 0$$

$$= s^2 + \frac{5}{2}s + 1 = 0 \rightarrow (1)$$

$$b^2 - 4ac = \left(\frac{5}{2}\right)^2 - 4(1)(1) = \frac{9}{4}$$

$$9 > \frac{9}{4} > 0 \rightarrow \text{Overdamped}$$

$$d = \frac{R}{ZL} \Rightarrow \frac{10}{2(4)} = \frac{10}{8} = \frac{5}{4}$$

$$W_r = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{4\left(\frac{1}{4}\right)}} = 1$$

$$\text{Response} = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\text{From (1)} \quad -\frac{\frac{5}{2} \pm \sqrt{\left(\frac{5}{2}\right)^2 - 4(1)(1)}}{2(1)} \Rightarrow -\frac{5}{4} \pm \frac{3}{4}$$

$$S_1 = -\frac{1}{2}; S_2 = -2$$

$$i(t) = A_1 e^{-\frac{1}{2}t} + A_2 e^{-2t}$$

from  $\frac{di_L}{dt} \rightarrow L \frac{di_L}{dt} + 10i_2 + V_C(t) = 0$

↓                    ↓  
 (2)                 $V_C(0^+) = V_C(0^-) = 0$

$$L \frac{di_L}{dt} = -20$$

$$\frac{di_L}{dt} = -\frac{20}{4} = -5 \frac{A}{s}$$

$$i'(t) = -5$$

↓  
0

$$i'(t) \Rightarrow -\frac{1}{2} A_1 e^{-\frac{1}{2}t} - 2A_2 e^{-2t} =$$

$$i'(0) = -\frac{1}{2} A_1 - 2A_2 = -5$$

$$i'(0) = 2 \rightarrow A_1 + A_2 = 2$$

$$A_1 = -\frac{2}{3} ; A_2 = \frac{8}{3}$$

$$i(t) \Rightarrow -\frac{2}{3} e^{-\frac{1}{2}t} + \frac{8}{3} e^{-2t}$$

$$i_L(t) \Rightarrow C \frac{dV}{dt}$$

$$\frac{i_L(t)}{C} dt \Rightarrow dV$$


$$V = \frac{1}{C} \int_0^t i_L(t) dt$$

$$= \frac{1}{0.25} \left[ \frac{t+4}{3} e^{-\frac{1}{2}t} - \frac{4}{3} e^{-2t} \right]_0^t$$

$$= \frac{16}{3} e^{-\frac{1}{2}t} - \frac{16}{3} e^{-2t}$$

**7.10** For the circuit in Fig. 7.90, find  $v_o(t)$  for  $t > 0$ .


Determine the time necessary for the capacitor voltage to decay to one-third of its value at  $t = 0$ .

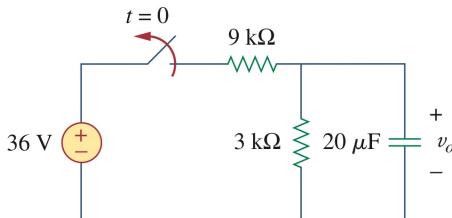

**Figure 7.90**

For Prob. 7.10.


RC Source free circuit

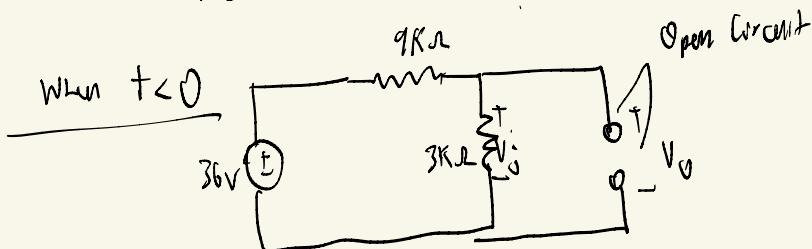

$$V_o(0^+) = V_o(0^-) \Rightarrow \left(\frac{3k}{3+9}\right)36 = \frac{3}{12} \times 36 = 9 \text{ V}$$

When  $t > 0$

$$i_c = C \frac{dv}{dt}$$

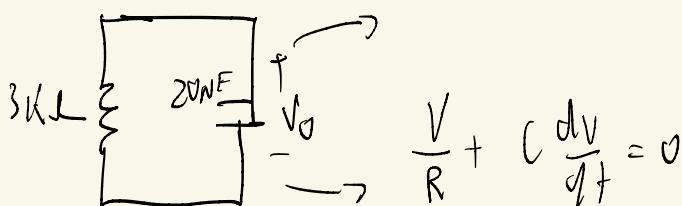

Response  $\rightarrow$  Series RC circuit  $\rightarrow$

$$T = 3k(20 \times 10^{-6}) \quad v = V_o e^{-\frac{t}{T}} = 9 e^{-\frac{t}{\frac{3}{50}}} = 9 e^{-\frac{t}{\frac{3}{50}}}$$

$$= 3000 \times (20 \times 10^{-6}) = \frac{3}{50}$$

$$= 9 e^{-\frac{50}{2} t}$$

$$as \quad V(\omega) = 4$$

$$3 = 9 e^{-\frac{50}{3} +}$$

$$\frac{1}{3} = e^{-\frac{50}{3} +}$$

$$\ln \left| \frac{1}{3} \right| = -\frac{50}{3} +$$

$$+ = 65,92 \text{ m/s}$$

6.62 Consider the circuit in Fig. 6.84. Given that

$v(t) = 12e^{-3t}$  mV for  $t > 0$  and  $i_1(0) = -10$  mA,  
find: (a)  $i_2(0)$ , (b)  $i_1(t)$  and  $i_2(t)$ .

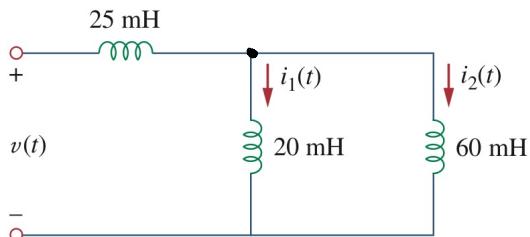


Figure 6.84

For Prob. 6.62.

$$\begin{aligned} \text{find } i_1(t) \rightarrow i_1(t) &= \frac{1}{L_1} \left( V_{at} + i(t_0) \right) \\ &= \frac{1}{\frac{1}{4} \cdot 10} \left( 12 e^{-3t} + i(0) \right) \\ &= \frac{1}{\frac{1}{4} \cdot 10} \left[ -4 e^{-3t} \left| \int_0^t + i(0) \right. \right] \end{aligned}$$

for current division

$$i_1(t) \Rightarrow i(t) \left( \frac{60}{20+60} \right)$$

$$i_1(t) \Rightarrow \frac{3}{4} i(t)$$

$$i_1(0) = \frac{3}{4} i(0)$$

$$\begin{aligned} L_{eq} &\Rightarrow 20/60 + 25 \\ &= \frac{20 \times 10}{20+60} + 25 \\ &= \frac{12.0 \text{ mH}}{8 \text{ mH}} + 25 \text{ mH} \\ &= 40 \text{ mH} \end{aligned}$$

$$i(t) = \frac{1}{40} \left( -4 e^{-3t} + t \right) + i(0)$$

$$i(t) \Rightarrow \left[ \frac{1}{10} \text{ mH} e^{-3t} + \frac{1}{10} \text{ mH} t + i(0) \right]$$

$$-10 \text{ mA} = \frac{3}{4} (i(0))$$

$$-\frac{40}{3} \text{ mA} = i(0)$$

$$i(0) = -0.0133 \text{ A}$$

X

$$(a) i_2(0) \Rightarrow i(t) \left( \frac{20}{20+60} \right) = \frac{1}{4} i(0)$$

$$= \frac{1}{4} (-0.0133)$$

$$= -3.33 \times 10^{-3} \text{ A}$$



$$(6) / (c) \rightarrow \text{as } i_1(0) = \frac{3}{4}i(0)$$



$$\Rightarrow i_1(t) = \frac{3}{4}i(t)$$

$$\Rightarrow \frac{3}{4} \left[ \left( -\frac{1}{10 \text{ mH}} e^{-3t} + \frac{1}{10 \text{ mH}} \right) + i_1(0) \right]$$

$$= -0.075 e^{-3t} + 0.075 + \frac{3}{4}i(0)$$

$$= -0.075 e^{-3t} + 0.065$$

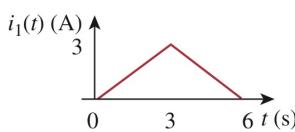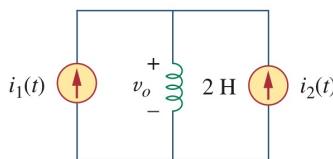**6.63** In the circuit of Fig. 6.85, sketch  $v_o$ .

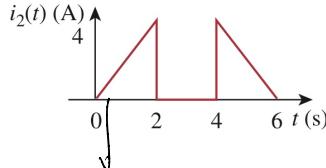


**Figure 6.85**

For Prob. 6.63.

$$i_1(t)(0-3)$$

$$\Rightarrow i_1(t) = t$$



$$i_2(t) \text{ for } 0 < t < 2 \\ = 2t$$

$$i_2(t) \text{ for } 4 < t < 6 \\ \Rightarrow -2$$

$$V_{o, \text{superposition}} \quad V_o = V_1 + V_2$$

$$V_1 = L \frac{di_1(t)}{dt} \rightarrow (0 < t < 3)$$




$$V_1 = L(1) = 2 \quad (0 < t < 3)$$

$$V_1 = L(-1) = -2 \quad (3 < t < 6)$$


$$V_2 = L(2) = 4 \quad (0 < t < 2)$$

$$V_2 = L(0) = 0 \quad (2 < t < 4)$$


$$= L(-2) = -4 \quad (4 < t < 6)$$

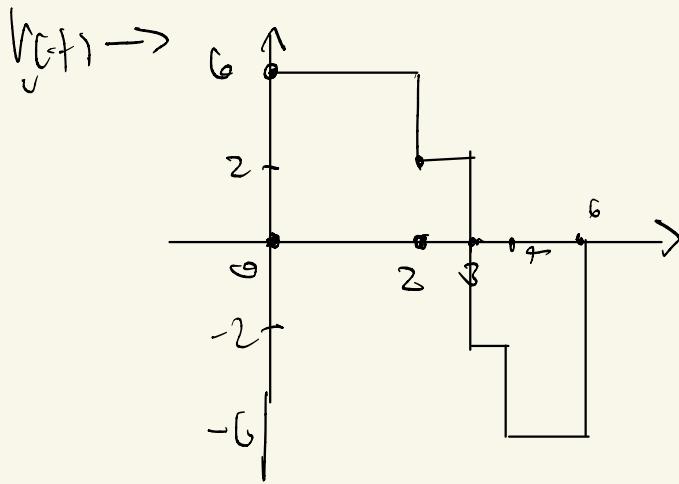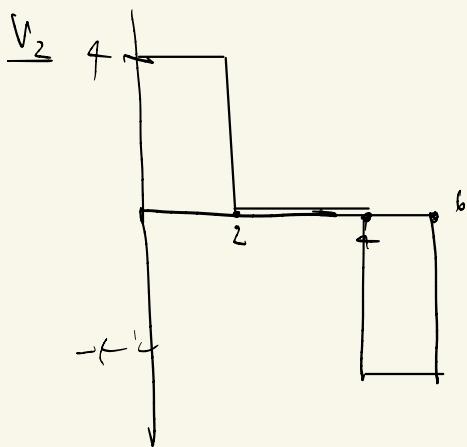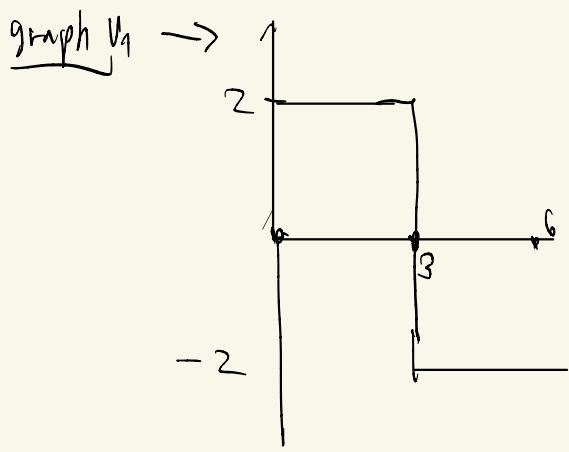

- \*6.57 Determine  $L_{eq}$  that may be used to represent the inductive network of Fig. 6.79 at the terminals.

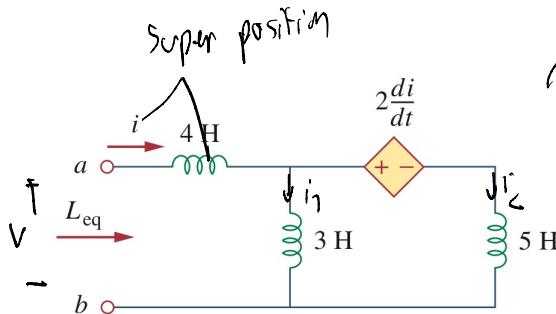

**Figure 6.79**  
For Prob. 6.57.

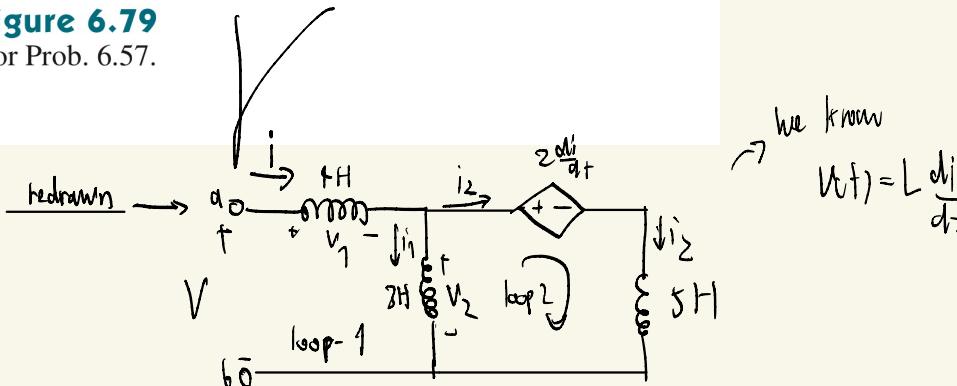

The total current  $i \rightarrow$  is  $i = i_1 + i_2 \rightarrow (2)$

apply KVL at loop 1  $\rightarrow i_2 = i - i_1$

$$V = V_1 + V_2 \rightarrow (1)$$

$$\text{also } V_1 = 4 \frac{di}{dt} \quad ; \quad V_2 = 3 \frac{di_2}{dt}$$

$$\frac{di_2}{dt} = \frac{V_2}{3}$$

$$\text{from (1)} \rightarrow V = 4 \frac{di}{dt} + V_2 \rightarrow (3)$$

$$\text{KVL Loop 2} \quad 2 \frac{di}{dt} + 5 \frac{di_2}{dt} - V_2 = 0$$

$$V_2 = 2 \frac{di}{dt} + 5 \frac{di_2}{dt} \rightarrow \text{from } Z \rightarrow i - i_2 = i_2$$

$$= 2 \frac{di}{dt} + 5 \frac{di}{dt} - 5 \frac{di_2}{dt}$$

$$V_2 = 7 \frac{di}{dt} - 5 \frac{di_2}{dt} \quad \text{also } \frac{di_2}{dt} = \frac{V_2}{3}$$

$$V_2 = 7 \frac{di}{dt} - 5 \frac{V_2}{3}$$

$$V_2 = \frac{21}{8} \frac{di}{dt}$$


Sub to (3) →  $V = 4 \frac{di}{dt} + \frac{21}{8} \frac{di}{dt}$

$$V = \frac{53}{8} \frac{di}{dt}$$

Hence from  $V(t) = \log \frac{di}{dt} = \frac{53}{8} \frac{di}{dt} = \log \frac{di}{dt}$

$$L_{eq} = \frac{53}{8} \cancel{\text{mH}}$$

- 6.61** Consider the circuit in Fig. 6.83. Find: (a)  $L_{eq}$ ,  $i_1(t)$ , and  $i_2(t)$  if  $i_s = 3e^{-t}$  mA, (b)  $v_o(t)$ , (c) energy stored in the 20-mH inductor at  $t = 1$  s.

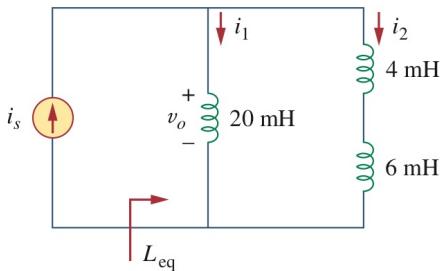

**Figure 6.83**

For Prob. 6.61.

$$L_{eq} \Rightarrow 10//20 = \frac{200}{30} = \frac{20}{3} \text{ mH}$$

$$i_1(t) = \frac{10}{(20+10)} (3e^{-t}) = e^{-t}$$

$$i_2(t) \Rightarrow \frac{20}{(30)} (3e^{-t}) = 2e^{-t}$$


$$\text{b.) } v_o = L_{eq} \frac{di_s}{dt} = \frac{20}{3} \times (-3e^{-t} \text{ mA})$$

$$= \frac{C}{3} \times 10^{-3} (-3e^{-t} \times 10^3)$$


$$W = \frac{1}{2} (20 \times 10^{-3}) (e^{-t})^2 = -20 e^{-t} \text{ Nm}$$

- 6.64** The switch in Fig. 6.86 has been in position A for a long time. At  $t = 0$ , the switch moves from position A to B. The switch is a make-before-break type so that there is no interruption in the inductor current. Find:

- (a)  $i(t)$  for  $t > 0$ ,
- (b)  $v$  just after the switch has been moved to position B,
- (c)  $v(t)$  long after the switch is in position B.

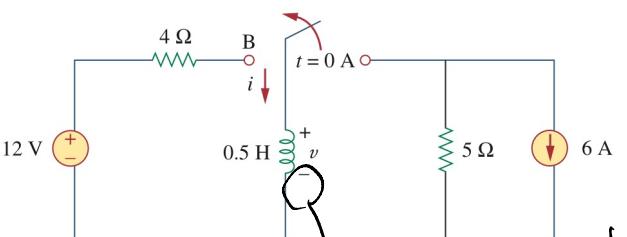


**Figure 6.86**  
For Prob. 6.64.

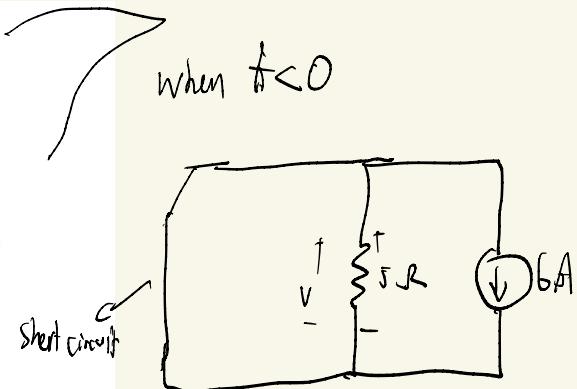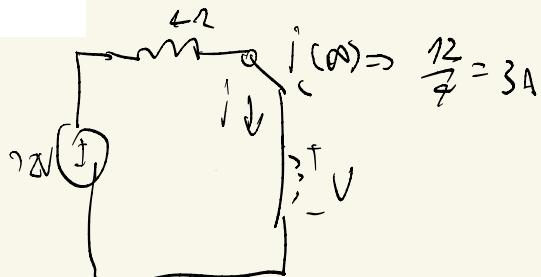

$$i(0+) = i(0-) = -6 \text{ A}$$

When  $t > 0 \rightarrow i \rightarrow \infty$



Step response

$$i(t) \Rightarrow i(0) + (i(\infty) - i(0)) e^{-\frac{t}{T}}$$

$$T = \frac{L}{R} = \frac{0.5}{4} = \frac{1}{8}$$

$$i(t) \Rightarrow 3 + (-6 - 3) e^{-8t}$$

$$= \frac{1}{8}$$

$$i_{CS} = 3 - 9e^{-8t}$$

for when  $t \rightarrow 0$   $V = L \frac{di_{CS}}{dt}$

$$V_{CS} = 0.5 \left( 72 e^{-8(0)} \right) = \frac{1}{2} (72) \\ \approx 36 V$$

$i_C = 0$  when  $V \rightarrow 0$   $\Rightarrow$  inductor become short circuit

hence  $V = 0$

7.46 For the circuit in Fig. 7.113,  $i_s(t) = 5u(t)$ . Find  $v(t)$ .


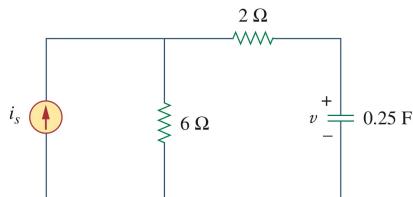


Figure 7.113

For Prob. 7.46.


$$i_{CS} = 5u(t) \rightarrow$$

when  $t < 0$

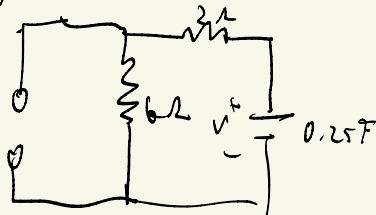

$$V(0^+) = V(0^-) = 0$$


When  $f > 0$

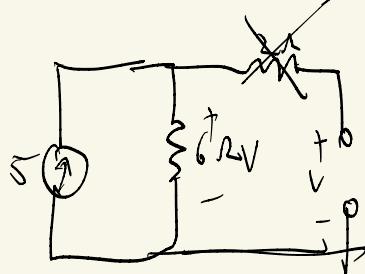

$$V \rightarrow \infty \Rightarrow V = jR \Rightarrow S(b) = 30$$

$$V(t) = 30 + (0 - 30)e^{-\frac{t}{T}}$$

$$T = RC \Rightarrow$$

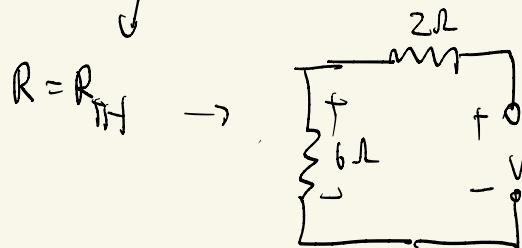


$R_{TH} \rightarrow$  (base independent) source  $\rightarrow$  Current becomes open circuit

Voltage becomes short circuit

$$R_{TH} = 8 \Rightarrow T = RC = 8 \times 0.25 = 2$$

$$V(t) = 30 - 30 e^{-\frac{t}{2}}$$

- 7.47 Determine  $v(t)$  for  $t > 0$  in the circuit of Fig. 7.114  
if  $v(0) = 0$ .

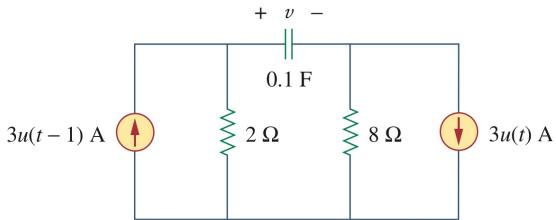

**Figure 7.114**

For Prob. 7.47.

Given  $V(0) \rightarrow 3v(t-1) \rightarrow$  when  $t < 1 = 0$

when  $t > 1 = 3$


when  $t < 0 \rightarrow V(0) = 0$

when  $0 < t < 1$

as  $V(0) \rightarrow$

Capacitor  $\Rightarrow$  Open

$$V = IR$$

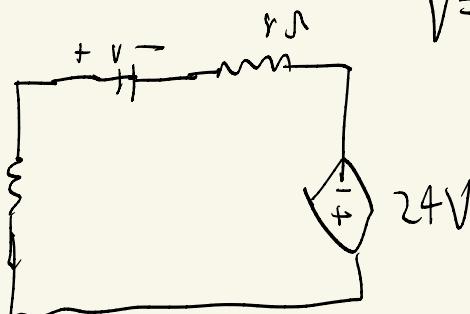

Circuit and  $V(\infty) = 24V$

$$\therefore V(t) = 24 + (0 - 24)e^{-\frac{t}{T}}$$


$$T = R C \Rightarrow R_{T/H} = 10 \rightarrow R = 10(\Omega A) \\ = 1$$

$$V(t) = 24 - 24e^{+\frac{t}{T}} V \text{ for } 0 < t < 1$$


$$\downarrow \quad V(1) = 24 - 24e^{-1} \Rightarrow 15.17 V$$

Now when  $t > 1$


$$V(0) = 15.97 \text{ V}$$

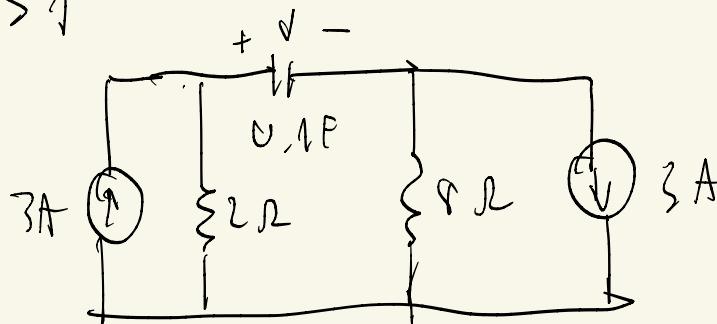

$$V(\infty) =$$

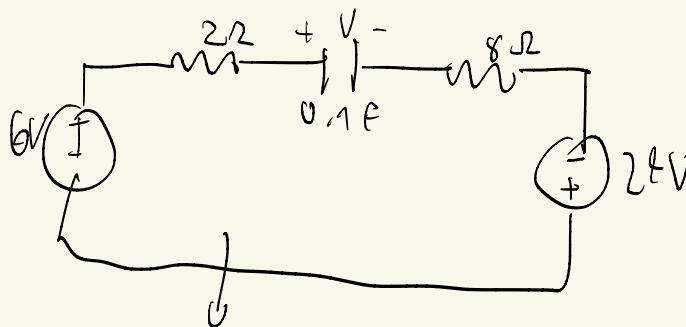

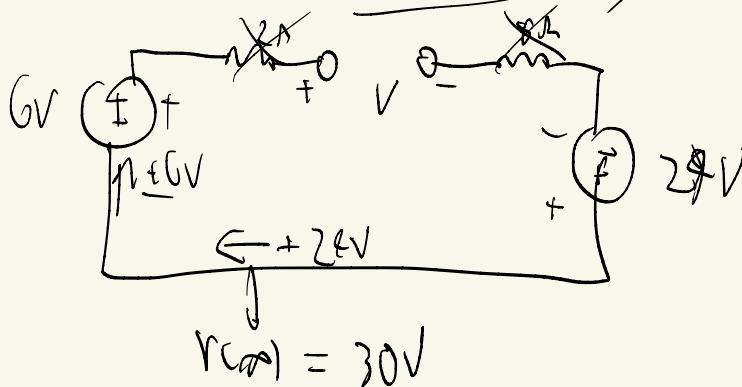Capacitor becomes open circuit, no current through



$$V(\infty) = 30 \text{ V}$$


$$T = RC = 10(0.1) = 1$$

$$\therefore V(t) \Rightarrow 30 + (15.97 - 30)e^{-t}$$

$$30 - 14.83 e^{-C(t-1)} \xrightarrow{\text{when } t > 1}$$

~~X~~

**7.48** Find  $v(t)$  and  $i(t)$  in the circuit of Fig. 7.115.

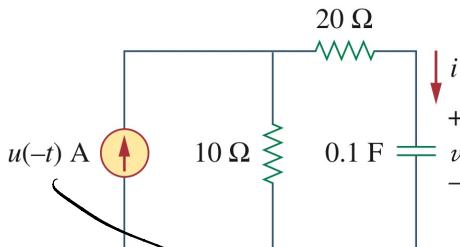


**Figure 7.115**  
For Prob. 7.48.

$1 \rightarrow t < 0$


$0 \rightarrow t > 0$

Open circuit; No current  
flow in

When  $t < 0$

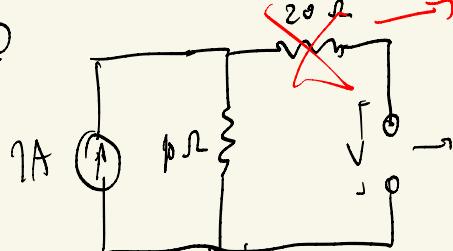


No current open circuit

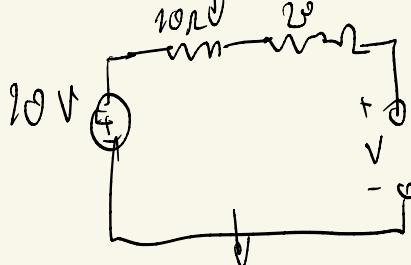

$$V(0) = 10V$$

$\approx V_0$

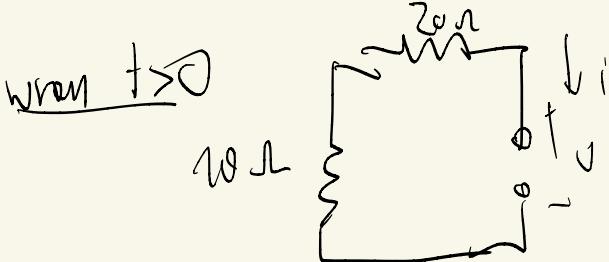

$$V(\infty) = 0 \quad T = RC \rightarrow \Rightarrow 0(0, 1)$$

$$= 3 \text{ s}$$


$$V(t) = 0 + (10 - 0) e^{-\frac{t}{3}}$$

$$V(t) = 10 e^{-\frac{t}{3}} //$$

$$i(t) = \left( \frac{dV}{dt} \right) = 0, 1 \left( -\frac{10}{3} e^{-\frac{t}{3}} \right)$$

$$i(t) = -\frac{1}{3} e^{-\frac{t}{3}}$$


- \*7.50 In the circuit of Fig. 7.117, find  $i_x$  for  $t > 0$ . Let  $R_1 = R_2 = 1 \text{ k}\Omega$ ,  $R_3 = 2 \text{ k}\Omega$ , and  $C = 0.25 \text{ mF}$ .

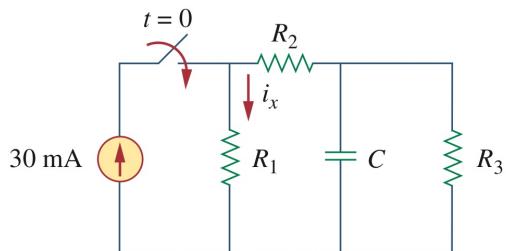

**Figure 7.117**


For Prob. 7.50.

When  $t < 0$

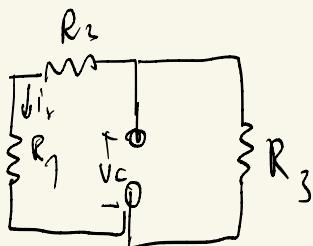


$$V(0^+) = V(0^-) = V_g = 0$$

When  $t > 0$

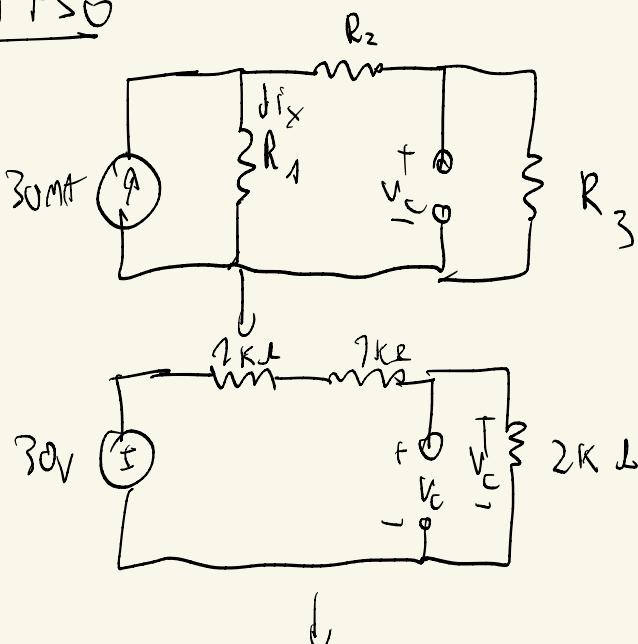

$$V_C(\infty) = \left(\frac{2}{2+2}\right) 30 = \frac{60}{4} = 15 \text{ V}$$

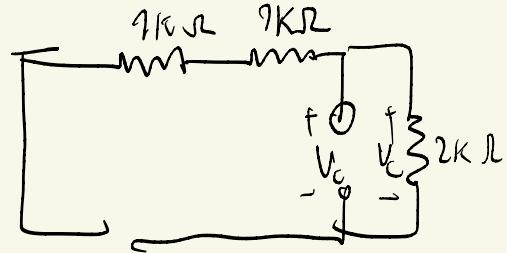$R = R_{TH} C \rightarrow R_{TH} \rightarrow$  Close all independent source



$$= 9 \times 1 // 2$$

$$= \frac{2 \times 2}{2+2} = 1 \text{ k}\Omega$$


$$R = 1 \text{ k}\Omega \times 0.25 \text{ mF} \Rightarrow 0.25 \text{ S}$$

$$V_C(t) = 15e^{-t} (0 - 15) e^{-4t}$$

$I_{CX} \rightarrow$  When  $t > 0$

↓

Parallel branches have the same Voltage.

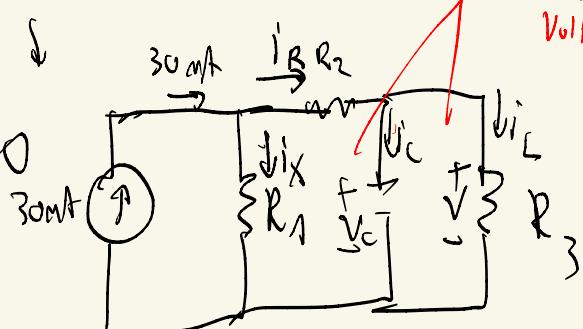

V

$$30 = i_x + i_R$$


$$i_R = 30 - i_x$$

$$i_R = i_C + i_L$$

$$i_C = C \frac{dV}{dt} + \frac{V}{R_3}$$

20, 25x  
solve then  $I_x = 30 - i_R$

- \*7.57 Find  $i_1(t)$  and  $i_2(t)$  for  $t > 0$  in the circuit of Fig. 7.123.

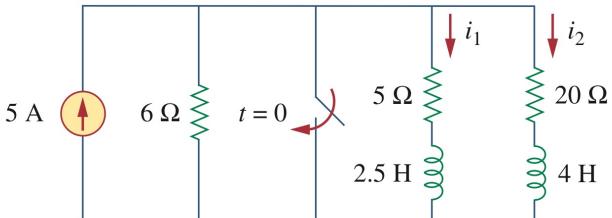


**Figure 7.123**

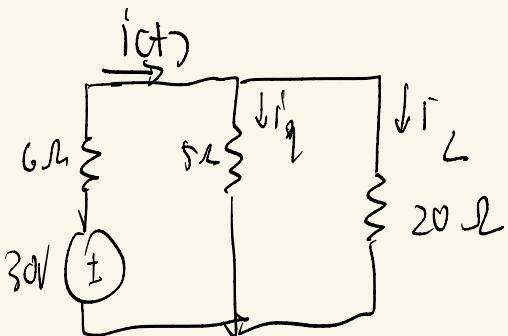For Prob. 7.57.

first step is to find  
the whole V(t), over  
ict, first

When  $t < 0 \rightarrow$  inductor  $b_{unl}$  short circuit




$$i_{\text{total}} \Rightarrow \frac{V}{R_{\text{eq}}} = \frac{30}{10} = 3$$

$$i(t) = 3$$

$$i(0) = 3$$

current division find  $i_1(0)$  /  $i_2(0)$
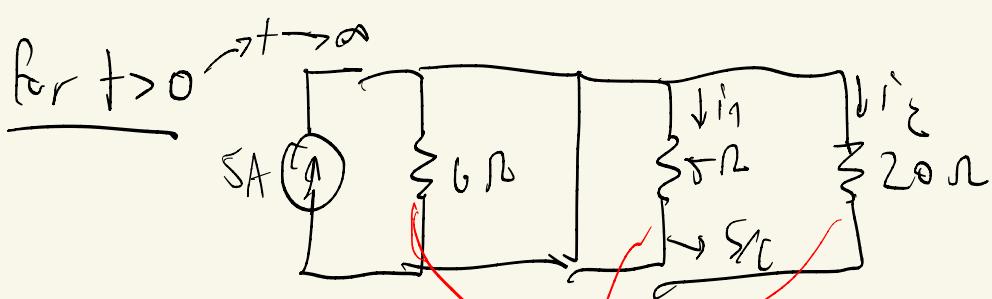
$$i_1(0) = \left(\frac{20}{25}\right)3 = 2.4 ; i_2(0) = 0.6$$



Parallel short circuit here no

$$i_L(\infty) = 0 ; \quad i_R(\infty) = 0$$

8.5 Refer to the circuit in Fig. 8.66. Determine:

- $i(0^+)$  and  $v(0^+)$ ,
- $di(0^+)/dt$  and  $dv(0^+)/dt$ ,
- $i(\infty)$  and  $v(\infty)$ .


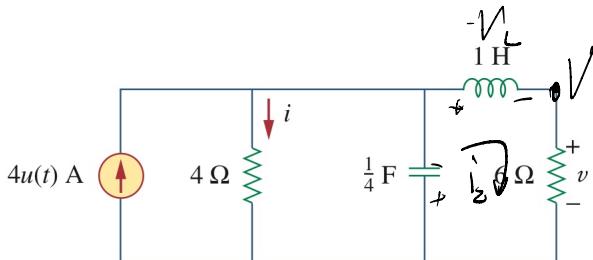


Figure 8.66

For Prob. 8.5.

(a) When  $t < 0$

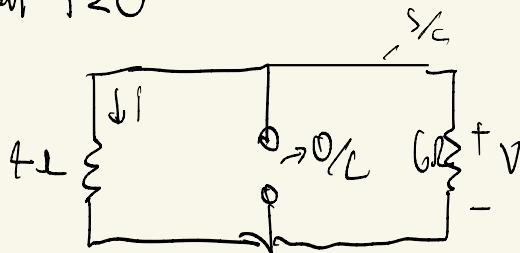


$$V_C(0^+) = V_C(0^-) \approx 0$$

$$\Rightarrow dI_L/dt = 0$$

$$I_L(0^+) = I_L(0^-) = 0$$

$$\Rightarrow V_L = 0$$

When  $t > 0$

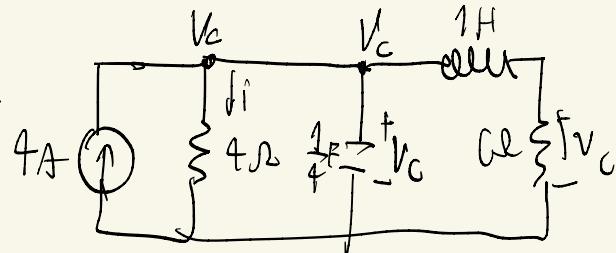

$$i = \frac{V_C}{R}$$

at  $V_C$

$$\frac{dV_C}{dt} = \frac{1}{R} \frac{dV_C}{dt}$$

$$-I + \frac{V_C}{R} + I_L + C \frac{dV_C}{dt}$$

$$\frac{di}{dt} = \frac{1}{4} \times 16$$

$$\frac{di}{dt} = 4$$

$$C \frac{dV_C}{dt} = 4 - \frac{V_C}{2} - I_L$$

$$\frac{dV_C}{dt} = \frac{4}{C} \quad V_C(0) = 0$$

$$\frac{4}{C} = 16$$

HVL at loop L

$$+V_L + V + \frac{1}{4} = 0$$

$$0 + V + \frac{1}{4} = 0$$

$$V = -\frac{1}{4} \rightarrow \frac{dV_{Coil}}{dt} = 0$$


$$V_C = L \frac{di_C}{dt}$$

$$\left\{ \frac{V_C}{L} dt = i_C \right.$$

$$\left. \frac{1}{L} \int V_C dt \right)$$




\*8.21 Calculate  $v(t)$  for  $t > 0$  in the circuit of Fig. 8.75.

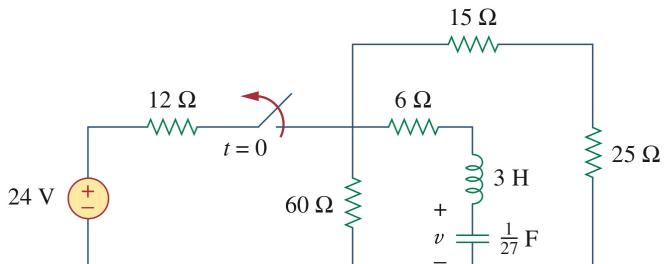


**Figure 8.75**

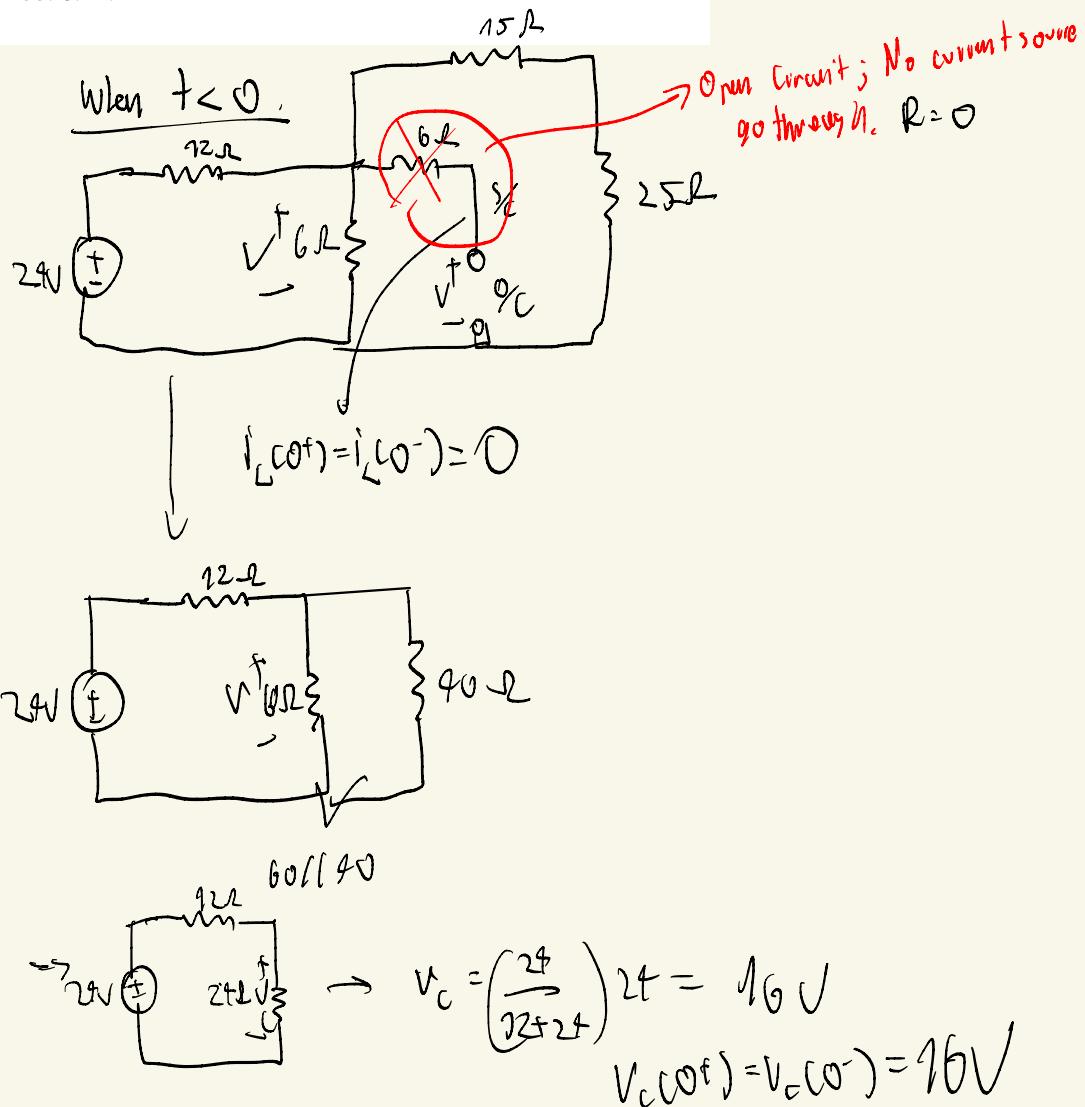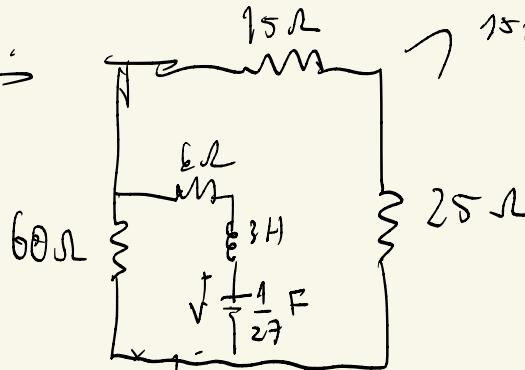For Prob. 8.21.




When  $t > 0$ .



$$15 + 25 = 40$$

$$90 / 40$$

$$= 2.25$$

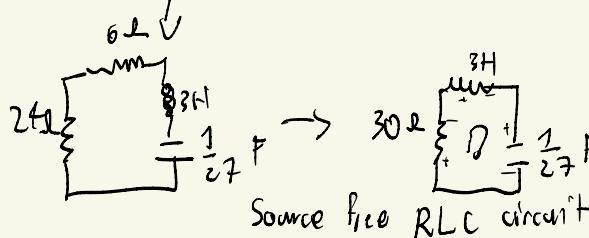

$$i = C \frac{dv}{dt}$$

$$\frac{1}{C} dt = \frac{dv}{v}$$

$$v = \frac{1}{C} \int i dt$$

Source free RLC circuit

$$L \frac{di_L}{dt} + \frac{1}{C} \int i dt + 30i = 0$$

$$L \frac{d^2 i_L}{dt^2} + \frac{i}{C} + 30 \frac{di_L}{dt} = 0$$

$$\frac{d^2 i_L}{dt^2} + \frac{30}{L} \frac{di_L}{dt} + \frac{9}{LC} i = 0$$

$$s^2 + 10s + 9 = 0$$

$$s^2 + 10s + 9 = 0$$

$$100 - 36 > 0$$

Overdamped.

$$\frac{-10 \pm \sqrt{100 - 4(9)(9)}}{2} = 0$$

$$S = -5 \pm 4$$

$$S_1 = -1 \quad ; \quad S_2 = -9$$

$$\text{Response} \rightarrow i(t) \Rightarrow A_1 e^{-t} + A_2 e^{-9t}$$

$$\text{From } \rightarrow L \frac{di_L}{dt} + \frac{1}{C} \int i dt + 30i = 0$$

$$L \frac{di_L}{dt} + V_C + 30i = 0$$

$$L \frac{di_L}{dt} = -16$$

$$\frac{di_L}{dt} \cdot \frac{16}{3} = -\frac{16}{3}$$

$$i(0) = 0 \rightarrow A_1 + A_2 = 0$$

$$i(0) = \frac{-16}{3} \rightarrow i(t) = -A_1 e^{-t} - 9A_2 e^{-9t}$$

$$i(0) = -\frac{16}{3} \rightarrow -A_1 - 9A_2 = -\frac{16}{3}$$

$$A_1 = -\frac{2}{3} \quad ; \quad A_2 = \frac{2}{3}$$

$$\text{if } s \Rightarrow -\frac{2}{3}e^{-t} + \frac{2}{3}e^{-4t}$$

$$V = L \frac{df}{dt} = 3 \left[ \frac{2}{3}e^{-t} - 6e^{-4t} \right]$$

$$V(t) = 2e^{-t} - 18e^{-4t}$$

