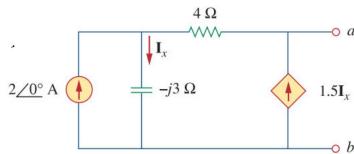





Exercise 5.3 (30%)

(a) (15%) Find the Thevenin equivalent at terminal a-b of the circuit below. And also draw the phasor diagram of the Thevenin equivalent impedance.



Find $Z_{TH} \rightarrow$ close all the independent source and apply $V = 1 < 0^\circ$

$$Z_{TH} = \frac{V}{I_0}$$

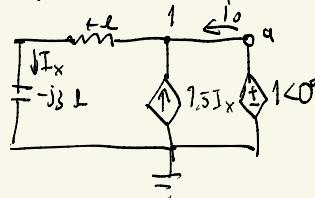

$$\frac{1}{4-j3} - 1.5jx - i_0 = 0$$

$$\text{Also } I_x = \frac{1-0}{4-j3}$$


$$\frac{1}{4-j3} - 1.5 \left(\frac{1}{4-j3} \right) = j0$$

$$i_0 = -0.08 - 0.06j$$

$$i_0 = 0.1 < -143.130^\circ$$

$$Z_{TH} = \frac{V}{I_0} = \frac{1}{0.1 < -143.130^\circ} \approx -8 + 6j$$

Find V_{TH} →

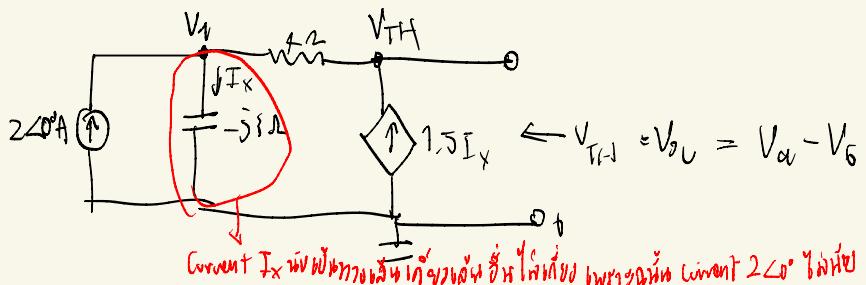

KCL at V₁

$$\left(-2\angle 0 + \frac{V_1}{-3j} + \frac{V_1 - V_{TH}}{4} = 0 \right) - 12j$$

$$2\angle 0 + 4V_1 - 3jV_1 + 3jV_{TH} = 0$$

$$(4 - 3j)V_1 + 3jV_{TH} = -2\angle 0 \rightarrow (1)$$

KCL at V_{TH} $\rightarrow \left(\frac{V_{TH} - V_1}{4} - 1.5I_X = 0 \right) +$

$$V_{TH} - V_1 - 6I_X = 0$$

$$I_X = \frac{V_1}{-3j}$$

$$V_{TH} - V_1 - 6 \left(\frac{V_1}{-3j} \right) = 0$$

$$V_{TH} - V_1 + \frac{2V_1}{3} = 0$$

$$\left(\frac{2}{3} - 1 \right) V_1 + V_{TH} = 0 \rightarrow (2)$$

use 1/2 $\rightarrow \begin{vmatrix} (4 - 3j) & (3j) \\ \frac{2}{3} - 1 & 1 \end{vmatrix} \begin{pmatrix} V_1 \\ V_{TH} \end{pmatrix} = \begin{pmatrix} -2\angle 0 \\ 0 \end{pmatrix}$


$$\Delta = -2$$

$$\Delta_2 \Rightarrow \begin{vmatrix} 4-3j & -24j \\ \frac{2}{3}-1 & 0 \end{vmatrix}$$


$$= 48 - 24j$$

$$V_{TH} = \frac{\Delta_2}{\Delta} = \frac{(48 - 24j)}{-2} \Rightarrow -24 + 12j$$


Thevenin Equivalent:

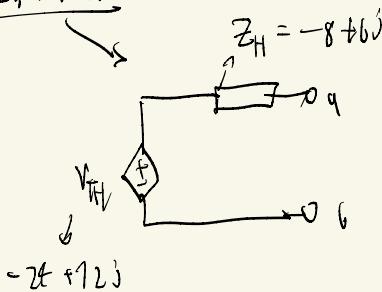

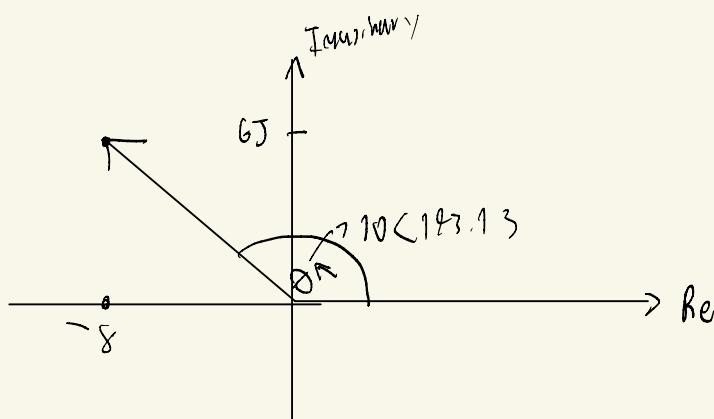Phasor diagram of \bar{Z}_{TH} $\rightarrow -8 + 6j$



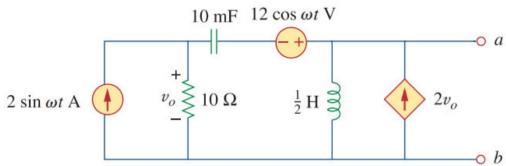(b) (15%) Find the Norton equivalent at terminal a-b of the circuit below. And also draw the phasor diagram of the Norton equivalent impedance. Take $\omega = 10 \text{ rad/s}$.




Find In phasor form

$$10 \text{ mF} = \frac{1}{(10 \times 10^{-3})(10)} j = -10 j$$

$$\frac{1}{2} \text{ H} = (10)(\frac{1}{2}) j = 5 j$$

Find Z_{TH} → close all independent Source and apply 1V

$$1 < 0^\circ$$

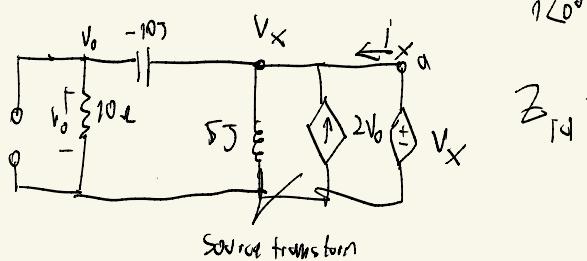

$$Z_{TH} = \frac{V_x}{I_x}$$

KCL at V_o

$$\frac{V_o}{10} + \frac{V_o - V_x}{-10j} = 0$$

$$\frac{V_o}{10} + \frac{1}{10} (jV_o - jV_x) = 0$$

$$\left(\frac{1}{10} + \frac{j}{10}\right)V_o = \frac{j}{10}V_x$$

$$\left(\frac{1+j}{10}\right)V_o = \frac{j}{10}V_x$$

$$V_o = \left(\frac{j}{1+j}\right)V_x$$

KCL at V_x


$$\frac{V_x - V_o}{-10j} + \frac{V_x}{5j} - 2V_o - i_x = 0$$

$$\frac{V_x - (\frac{j}{1+j})V_x}{-10j} + \frac{V_x}{5j} - 2\left(\frac{j}{1+j}\right)V_x = i_x$$

$$\frac{V_x(1 - \frac{1}{1+j})}{-10j} + \left(\frac{1}{5j} - \frac{2j}{1+j}\right)V_x = i_x$$

$$V_x \left(\frac{-19}{20} - \frac{23}{20} j \right) = i_x$$

✓

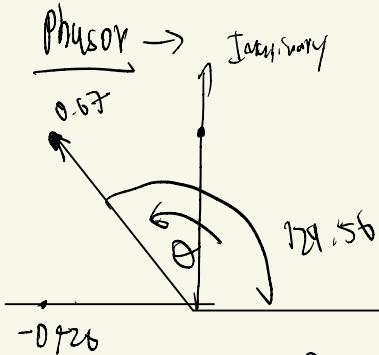

$$V_X = \frac{I_X}{\left(\frac{-19}{20} - \frac{23}{20}j\right)}$$



$$Z_{TH} = \frac{V_X}{I_X} = \frac{\frac{I_X}{I_X}}{\left(\frac{-19}{20} - \frac{23}{20}j\right)} = \frac{1}{\left(\frac{-19}{20} - \frac{23}{20}j\right)}$$


$$= \frac{1}{\left(\frac{-19}{20} - \frac{23}{20}j\right)}$$

$$= -\frac{38}{89} + \frac{46}{89}j \Rightarrow 0.67 \angle 129.56^\circ$$

Find I_n Short Circuit I_s

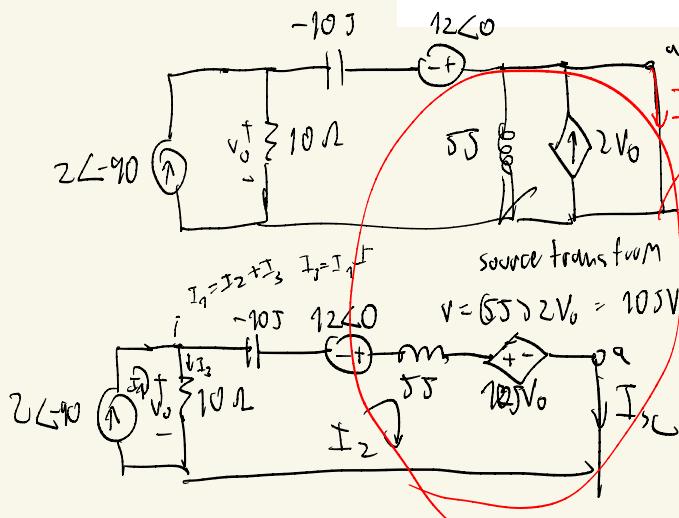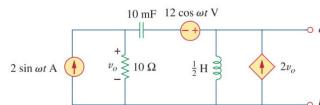(b) (15%) Find the Norton equivalent at terminal a-b of the circuit below. And also draw the phasor diagram of the Norton equivalent impedance. Take $\omega = 10 \text{ rad/s}$.



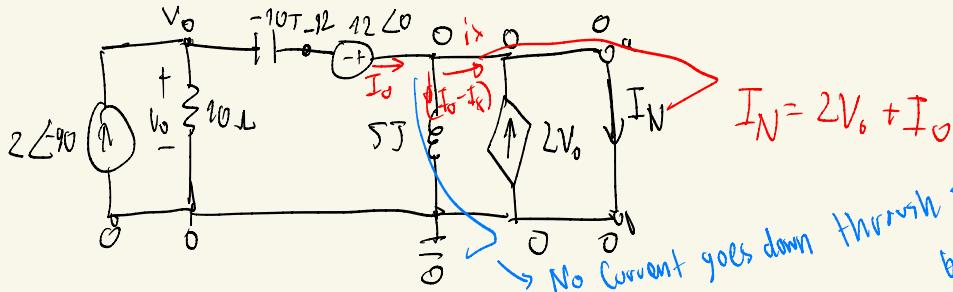

$$\text{KCL at } V_0 \rightarrow \left(-(-2J) + \frac{V_0}{20} + \frac{V_0 + 12}{-10J} = 0 \right) - 10J$$

$$I_x + (I_0 - I_x) = I_0 \quad -20J^2 - JV_0 + V_0 + 12 = 0$$

$$-2V_0 + I_0 + 2V_0 = I_0 \quad 20 - JV_0 + V_0 + 12 = 0$$

$$I_0 = I_0 = I_x \quad (1-J)V_0 = -32$$

$$V_0 = \frac{-32}{(1-J)} \approx -16 - 16J$$


$$I_N = 2V_0 + I_0 \quad \rightarrow I_0 = \frac{V_0 + 12}{-10J}$$

$$= 2(-16 - 16J) + \frac{(-16 - 16J) + 12}{-10J}$$

$$I_N = 44.93 \angle -933.18^\circ$$

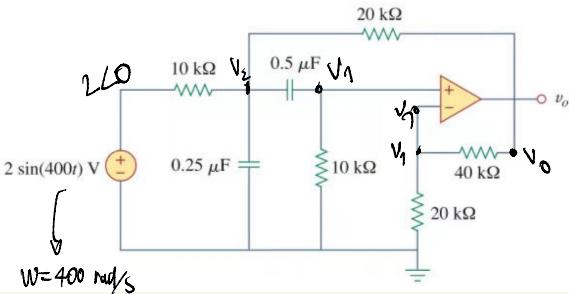Exercise 5.4 (15%)

Determine $v_o(t)$ in the op amp circuit in the figure below.



$$0.5NF = \frac{1}{(400)(0.5 \times 10^{-6})} = -5jK$$

$$0.25NF = \frac{1}{(400)(0.25 \times 10^{-6})} = -10jK$$

$$\text{KCL at } V_2 \rightarrow \left(\frac{V_2 - 2}{10K} + \frac{V_2}{-10jK} + \frac{V_2 - V_o}{20K} + \frac{V_2 - V_1}{-5jK} = 0 \right) 20K$$

$$2jV_2 - 4 + 2jV_2 + V_2 - V_o + 4jV_2 - 4jV_1 = 0$$

$$(3 + 6j)V_2 - 4jV_1 - V_o = 4 \rightarrow (1)$$

$$\text{KCL at } V_1 \rightarrow \left(\frac{V_1 - V_2}{-5jK} + \frac{V_1}{10K} = 0 \right) 10K$$

$$2jV_1 - 2jV_2 + V_1 = 0$$

$$(1 + 2j)V_1 = 2jV_2 \rightarrow V_2 = (1 - 0.5j)V_1 \rightarrow (2)$$

$$\text{KCL at } V_1 \rightarrow \text{other side} \quad \left(\frac{V_1 - V_o}{40K} + \frac{V_1}{20K} = 0 \right) 40K$$

$$V_1 - V_0 + 2V_2 = 0$$

$$3V_1 = V_0$$

$$V_1 = \frac{1}{3}V_0 // \rightarrow (3)$$

$$\underline{K\omega L q + V_0} \rightarrow \left(\frac{V_0 - V_1}{40K} + \frac{V_0 - V_2}{20K} = 0 \right) 40K$$

$$V_0 - V_1 + 2V_0 - 2V_2 = 0$$

$$3V_0 = V_1 + 2V_2$$

$$V_0 = \frac{1}{3}V_1 + \frac{2}{3}V_2$$

Sub (2) and (3) into (1)

$$(3+6j)(1-0.5j)V_1 - 4j\left(\frac{1}{3}V_0\right) - V_0 = 7$$

$$\left(2 + \frac{1}{2}j\right)V_0 - \frac{4}{3}jV_0 - V_0 = 7$$


$$\left(1 + \frac{1}{6}j\right)V_0 = 7$$

$$V_0 = 3.9456 \angle -9.4623^\circ$$

$$\underline{V_0 = 3.9456 \sin(40\omega t - 9.4623)}$$

Thevenin / Norton Equivalence

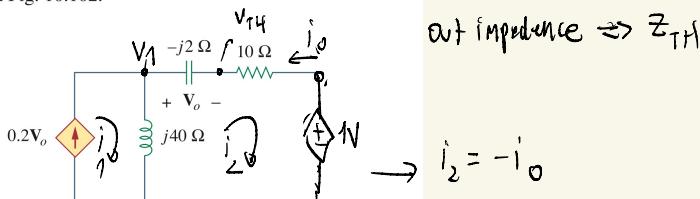- 10.59 Calculate the output impedance of the circuit shown in Fig. 10.102.



out impedance $\Rightarrow Z_{TH}$

$$i_2 = -i_o$$

Figure 10.102

For Prob. 10.59.

$$V_o = -i_o(-j2) = 2j i_o$$

$$\text{KVL at } i_1 \rightarrow i_1 = 0.2V_o$$

$$-j2(i_2) + 10i_2 + 1 + 40j(i_2 - i_1) = 0$$

$$2j i_o - 10i_o + 1 + 40j(-i_o) - 40j i_1 = 0$$

$$(-38j - 10)i_o - 40j(0.2(2j i_o)) = -1$$

$$(-38j - 10)i_o + 16i_o = -1$$

$$(6 - 38j)i_o = -1$$

$$i_o = \frac{-3}{740} - \frac{19}{740}j$$

$$Z_{TH} = \frac{1}{\left(\frac{-3}{740} - \frac{19}{740}j\right)}$$

$$Z_{TH} = -6 + 38j$$

$$Z_{TH} = 38.17 \angle 98.97^\circ$$

- 10.60** Find the Thevenin equivalent of the circuit in Fig. 10.103 as seen from:

(a) terminals $a-b$ (b) terminals $c-d$


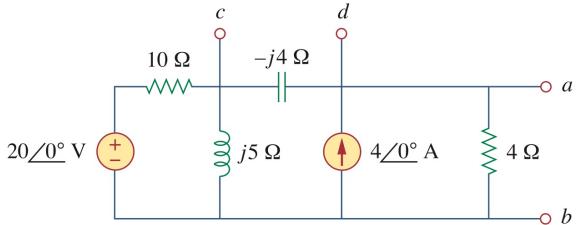


Figure 10.103

For Prob. 10.60.

$$\text{at terminal } a-b; \quad V_{TH} = V_a - V_b$$

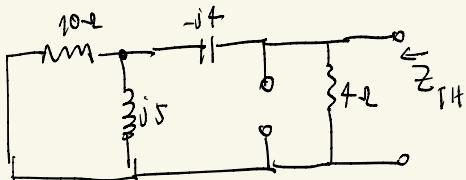Find Z_{TH} \rightarrow Close all independent source




$$10//j5 \rightarrow \frac{50j}{10+j5} - j4 \parallel 4$$

V

$$2//t$$
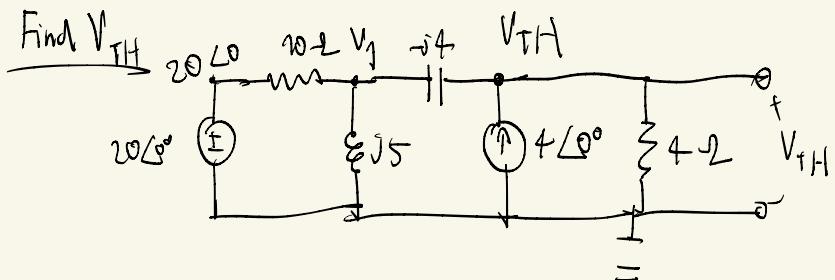
$$= \frac{2 \times t}{t+2} = \frac{8}{6} = \frac{4}{3} \Omega$$



$$\underbrace{\text{KCL at } V_1}_{\rightarrow} \rightarrow \frac{V_1 - 20\angle 0}{10 - j2} + \frac{V_1}{j5} + \frac{V_1 - V_{TH}}{-j4} = 0$$

$$\left(\frac{1}{10} + \frac{1}{20}j \right) V_1 + \frac{1}{j5} V_{TH} = 2 \rightarrow (1)$$

$$\underbrace{\text{KCL at } V_{TH}}_{\rightarrow} \rightarrow \frac{V_{TH} - V_1}{-j4} - 4 + \frac{V_{TH}}{4} = 0$$

$$\left(\frac{1}{4j} V_1 \right) + \left(\frac{1}{4} + \frac{1}{4}j \right) V_{TH} = 4 \rightarrow (2)$$

Find $V_{TH} \rightarrow \text{use } \Delta_2$

$$\begin{vmatrix} \left(\frac{1}{10} + \frac{1}{20}j \right) & \frac{1}{4j} \\ \frac{1}{4j} & \left(\frac{1}{4} + \frac{1}{4}j \right) \end{vmatrix} \begin{Bmatrix} V_1 \\ V_{TH} \end{Bmatrix} = \begin{Bmatrix} 2 \\ 4 \end{Bmatrix}$$

$$\Delta = \frac{3}{40} + \frac{3}{80}j$$

$$\Delta_2 = \begin{vmatrix} \left(\frac{1}{10} + \frac{1}{20}j \right) & 2 \\ \frac{1}{4j} & 4 \end{vmatrix} \Rightarrow \left(\frac{2}{5} + \frac{7}{20}j \right)$$

$$V_{TH} \doteq \frac{\Delta_2}{\Delta} = 8 + \frac{16}{3}j \rightarrow 9.6148 \angle 33.69^\circ$$

10.62 Using Thevenin's theorem, find v_o in the circuit of Fig. 10.105.


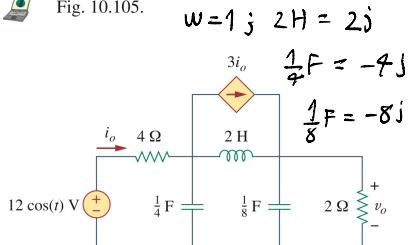


Figure 10.105
For Prob. 10.62. Open circuit at V_0 as we want V_0
find Z_{TH} → close all independent source

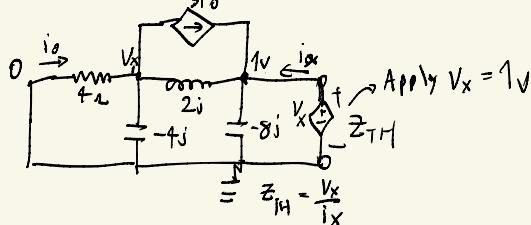

$$\text{At Node } 1 \rightarrow \frac{V_x}{4} + \frac{V_x}{-4j} + \frac{V_x - 1}{2} + 3i_o = 0$$

$$\frac{V_x}{-4j} - \frac{2V_x}{4} = \frac{1 - V_x}{2j}$$

$$V_x = 0.4 + j0.0$$

$$\text{At Node } 1V \rightarrow \frac{1 - V_x}{2} - 3i_o + \frac{1}{-8j} - i_x = 0$$

$$i_o = -\frac{V_x}{4}$$


$$i_x = (0.75 + j0.5)V_x - j\frac{3}{8}$$

$$i_x = -0.4 + 0.4j2.5j$$

$$Z_{TH} = \frac{V}{I_x} = \frac{1}{(0.75 + j0.5)} = -0.5246 - j2.229$$

Find V_{TH}
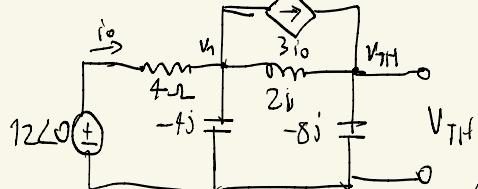
$$Z_{TH} \Rightarrow 2.29 \angle -103.24^\circ$$



$$\text{KCL at } V_1 \rightarrow \frac{V_1 - 12}{4} + \frac{V_1}{-4j} + 3i_o + \frac{V_1 - V_{TH}}{2j} = 0$$

$$\left(\frac{1}{4} - \frac{1}{4j} \right) V_1 - \frac{1}{2j} V_{TH} = 3 - 3i_o \rightarrow (1)$$

$$i_o = \frac{12 - V_1}{4}$$

$$3 - 3i_o \Rightarrow 3 - 3 \left(\frac{12 - V_1}{4} \right)$$

$$\Rightarrow 3 - \left(\frac{36 - 3V_1}{4} \right) = -6 + \frac{3}{4} V_1$$

$$\left(-\frac{1}{2} - \frac{1}{4j} \right) V_1 - \frac{1}{2j} V_{TH} = -6 \rightarrow (2)$$

KCL at V_{TH}

$$\frac{V_{TH} - V_1}{2j} - 3i_o + \frac{V_{TH}}{-8j} = 0$$

$$\frac{V_{TH} - V_1}{2j} - \frac{3i_o}{4} + \frac{3V_1}{4} + \frac{V_{TH}}{-8j} = 0$$

$$\left(\frac{3}{4} + \frac{1}{2}j \right) V_1 - \frac{3}{8}j V_{TH} = 9 \rightarrow (2)$$

Find $V_{TH} \rightarrow \Delta 2$

$$\begin{vmatrix} -\frac{1}{2} - \frac{1}{4}j & -\frac{1}{2j} \\ \frac{3}{4} + \frac{1}{2}j & -\frac{3}{8}j \end{vmatrix} \begin{vmatrix} V_1 \\ V_{TH} \end{vmatrix} = \begin{pmatrix} -6 \\ 9 \end{pmatrix}$$

$$\Delta \Rightarrow \frac{1}{32} - \frac{3}{16}j$$

$$\Delta_2 \Rightarrow \begin{vmatrix} -\frac{1}{2} - \frac{1}{4}j & -6 \\ \frac{3}{4} + \frac{1}{2}j & 9 \end{vmatrix} \Rightarrow \frac{3}{4}j$$

$$V_{TH} = \frac{\Delta_2}{\Delta} = \frac{-144}{61} + \frac{120}{61}j \Rightarrow 3.073 \angle 140.194^\circ$$

$$\text{Circuit diagram: } V_{TH} \text{ is a voltage source in series with } \frac{2}{2+Z_{TH}} \text{ and } 2\Omega. V_o = V_{TH} \left(\frac{2}{2+Z_{TH}} \right)$$

$$V_o = \frac{2(3.073 \angle -24.8^\circ)}{1.4754 - j2.229}$$

$$V_o \rightarrow 2.3 \angle -163.3^\circ$$

$$V_o = 2.3 \cos(t - 163.3) V.$$

- 10.63** Obtain the Norton equivalent of the circuit depicted in Fig. 10.106 at terminals *a-b*.



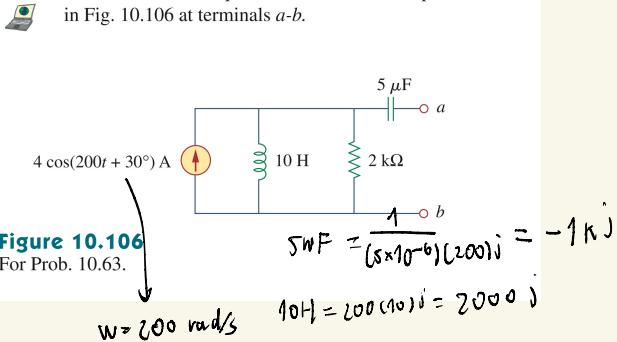


Figure 10.106
For Prob. 10.63.

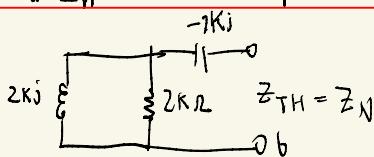
find $Z_N \rightarrow$ close all independent Source.


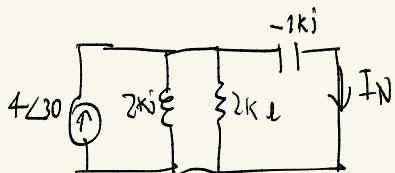
$$= \frac{4k^2}{2k + 2k} - 1k = 1k \rightarrow Z_{TH} = 1k \Omega = Z_N$$



$$(j2 // 2 = \frac{j2}{2+2j} = 1+j)$$

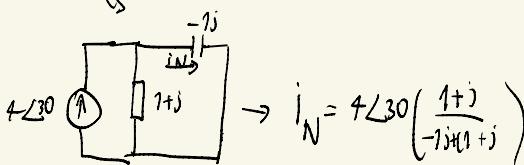

$$I_N = 5.65 \angle 75^\circ$$

- 10.64** For the circuit shown in Fig. 10.107, find the Norton equivalent circuit at terminals *a*-*b*.


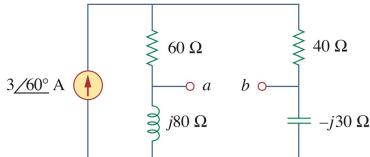


Figure 10.107


For Prob. 10.64.

$$\text{Find } Z_{TH} = Z_N$$

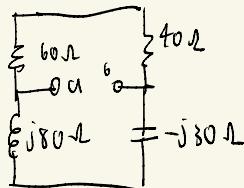

$$Z_{TH} \rightarrow 100//50j = 20 + j10 = 22.36 \angle 63.43^\circ$$
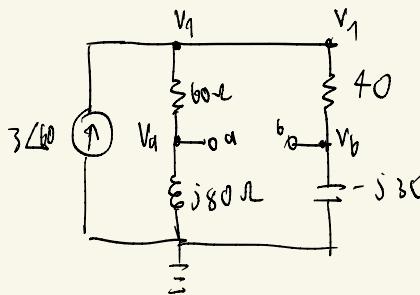
$$\text{Find } V_{TH} \rightarrow V_a - V_b$$



$$\text{KCL at } V_1 \rightarrow -3 \angle 60^\circ + \frac{V_1 - V_a}{60} + \frac{V_1 - V_b}{40} = 0$$

$$\left(\frac{1}{24}\right)V_1 - \frac{1}{60}V_a - \frac{1}{40}V_b = 3 \angle 60^\circ \rightarrow (1)$$

$$\text{KCL at } V_a \rightarrow \frac{V_a - V_1}{60} + \frac{V_a}{j80} = 0$$

$$\left(\frac{1}{60} - \frac{1}{80}j\right)V_a = \frac{V_1}{60}$$

$$V_1 = \left(1 - \frac{3}{4}j\right) V_a \rightarrow V_a = \underbrace{\left(\frac{16}{25} + \frac{12}{25}j\right)}_{V_1} V_1$$

KCL at V_b $\rightarrow \frac{V_b - V_1}{40} + \frac{V_b}{-j30} = 0$

$$\left(\frac{1}{40} + \frac{1}{30}j\right) V_b = \frac{V_1}{40}$$

$$V_b = \left(\frac{9}{25} - \frac{12}{25}j\right) V_1$$

$$\left(\frac{1}{14}\right) V_1 - \frac{1}{60} \left(\frac{16}{25} + \frac{12}{25}j\right) V_1 - \frac{1}{90} \left(\frac{9}{25} - \frac{12}{25}j\right) V_1 = 3 \angle 60^\circ$$

$$\left(\frac{11}{500} + \frac{1}{250}j\right) V_1 = 3 \angle 60^\circ$$

$$V_1 = 86.7846 + 102.3953j$$

$$\begin{matrix} \uparrow \\ 134.161 < 49.695 \end{matrix}$$

$$V_a = 6.431 + 107.738j$$

$$V_b = 80.354 - 4.8233j$$

$$V_{TH} = V_a - V_b \Rightarrow -73.923 + 111.96j$$

$$I_N = \frac{V_{TH}}{Z_{TH}} = 3 \angle 60^\circ$$

  10.67 Find the Thevenin and Norton equivalent circuits at terminals $a-b$ in the circuit of Fig. 10.110.

ML


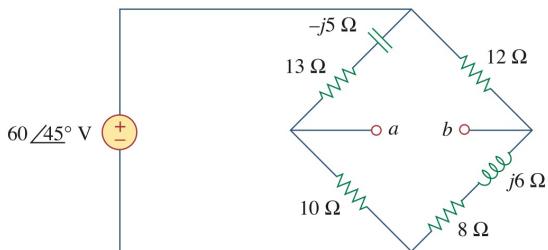


Figure 10.110

For Prob. 10.67.

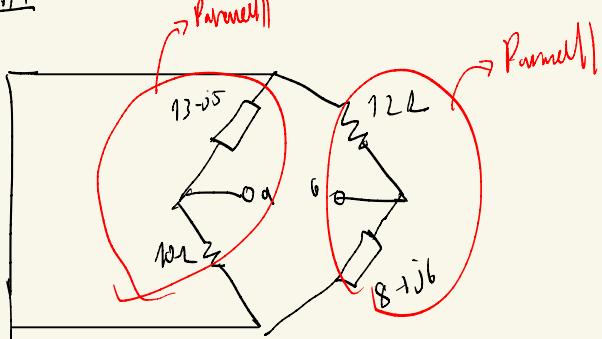$Z_{TH} \rightarrow$ Close all independent Source.



10.68 Find the Thevenin equivalent at terminals $a-b$ in the circuit of Fig. 10.111.

ML


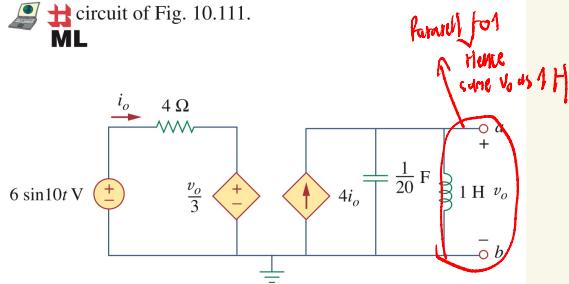


Figure 10.111

For Prob. 10.68.

Find $Z_{TH} \rightarrow$ Close all independent Source

$\omega = 10 \text{ rad/s}$

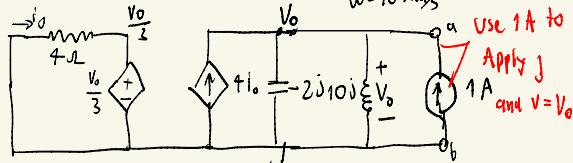

$$\text{KCL at } \frac{V_o}{3} \rightarrow i_o = -\frac{V_o}{\frac{3}{4}} = -\frac{V_o}{12}$$

$$\text{KCL at } V_o \rightarrow -4i_o - 1 + \frac{V_o}{-2j} + \frac{V_o}{10j} = 0$$

$$-\frac{V_o}{-2j} + \frac{V_o}{10j} = 1 + 4\left(\frac{-V_o}{12}\right)$$


$$\frac{V_o}{-2j} + \frac{V_o}{10j} = 1 + -\frac{V_o}{3}$$

$$\frac{V_o}{-2j} + \frac{V_o}{10j} + \frac{V_o}{3} = 1$$

$$\left(\frac{1}{3} + \frac{2}{5}j\right)V_o = 1$$

$$V_o = \frac{75}{61} - \frac{40}{61}j \approx 1.92 \angle -50.196^\circ$$
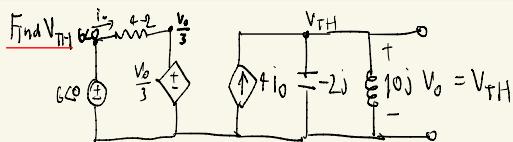
$$Z_{TH} = \frac{V_o}{I_A} = \frac{V_o}{1A} = 1.2291 - 1.475j \approx 1.92 \angle -50.196^\circ$$



$$\text{KCL at } \frac{V_o}{3} \rightarrow i_o = \frac{6 - V_o}{4} \rightarrow V_{TH} = V_o$$

$$\text{KCL at } V_{TH} \rightarrow -4i_o + \frac{V_{TH}}{-2j} + \frac{V_{TH}}{10j} = 0$$

$$-4\left(\frac{6 - V_o}{4}\right) + \frac{V_{TH}}{-2j} + \frac{V_{TH}}{10j} = 0$$

$$-6 + \frac{V_o}{3} + \frac{V_{TH}}{-2j} + \frac{V_{TH}}{10j} = 0$$

$$\left(\frac{1}{3} + \frac{2}{5}j\right)V_{TH} = 6$$

$$V_{TH} = \left(\frac{450}{61} - \frac{540}{61}j\right) \approx 11.523 \angle -50.194^\circ V$$

10.76 Determine V_o and I_o in the op amp circuit of

Fig. 10.119.

ML

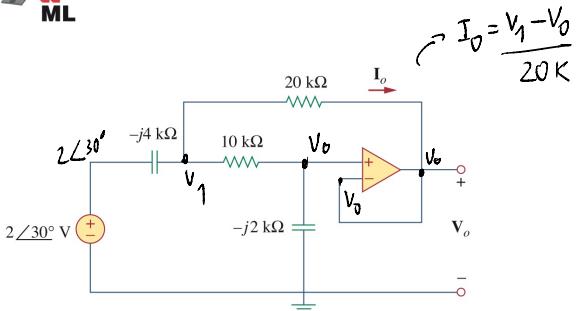


Figure 10.119

For Prob. 10.76.

$$\text{KCL at } V_1 \rightarrow \frac{V_1 - 2\angle 30^\circ}{-j4} + \frac{V_1 - V_o}{20} + \frac{V_1 - V_o}{10} = 0$$

$$\left(\frac{3}{20} + \frac{1}{4}j\right)V_1 - \frac{3}{20}V_o = \frac{\sqrt{3}}{4}j - \frac{1}{4} \quad \rightarrow (1)$$

$$\text{KCL at } V_o \rightarrow \left(\frac{V_o - V_1}{10} + \frac{V_o}{-j2} = 0 \right) \quad (2)$$

$$V_o - V_1 + \frac{5V_o}{-j2} = 0$$

$$(1 + 5j)V_o = V_1$$

$$V_o = \left(\frac{1}{1+5j}\right)V_1$$

$$\left(\frac{3}{20} + \frac{1}{4}j\right)V_1 - \frac{3}{20} \left(\frac{1}{1+5j}\right)V_1 = \frac{\sqrt{3}}{4}j - \frac{1}{4}$$

$$\left(\frac{15}{104} + \frac{29}{104}j\right)V_1 = \left(\frac{\sqrt{3}}{4}j - \frac{1}{4}\right)$$

$$V_1 = 0.859 + 1.341j$$

$$V_0 = 0.2409 - 0.114j \rightarrow 312.4 \angle -21.34^\circ \text{ mV}$$

$$I_0 = \frac{V_1 - V_0}{20} = \frac{0.0284 + 0.0727j}{V}$$

$$\approx 0.078 \angle 68.67^\circ \text{ mA}$$


Exercise 6.3 (30%)

→ **real power**

A 240-V rms 60-Hz source supplies a parallel combination of a 5-kW heater and a 30-kVA induction motor whose power factor is 0.82. Determine:

1. the system apparent power
2. the system reactive power
3. Sketch the power triangle for the current system and label $|S|$, P , and Q
4. the power factor of the current system
5. the kVA rating of a capacitor required to adjust the system power factor to 0.9 lagging
6. the value of the capacitor required


1)

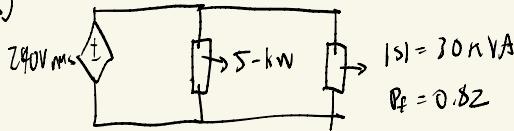

$$S_1 = 5 \text{ kW} + 0 \quad \rightarrow |S_1| = \sqrt{P^2 + Q^2} = 5$$

real power

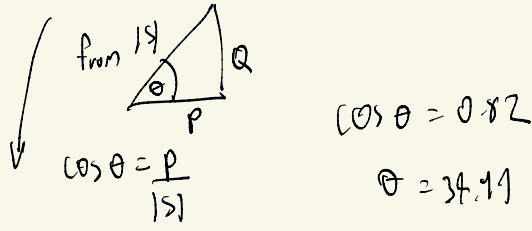need to find $S_2 \rightarrow S = 30 \text{ kVA}$ and $\cos \phi_f = 0.82$



$$P = \cos \theta |S|$$

$$P_f = \cos \theta = 0.82$$

$$P = 0.82 \times 30 \text{ kVA} = 24.6 \text{ kW}$$

$$\tan \theta = \frac{Q}{P} \Rightarrow Q = P \tan \theta$$

$$= 24.6 \tan 34.91^\circ$$

$$Q = 17.1676 \text{ VAR}$$

$$S_2 = P + jQ = 24.6 + 17.1676j$$

$$S_{\text{total}} = S_1 + S_2 \rightarrow 24.6 + 17.1676j$$

Apparent Power

$$= |S|$$

$$= \sqrt{24.6^2 + 17.1676^2}$$


$$|S| = 34.22 \text{ kVA}$$

Exercise 6.4 (20%)

Two wattmeters are properly connected to the unbalanced load supplied by a balanced source such that $V_{ab} = 208\angle 0^\circ$ V with positive phase sequence.

- Determine the reading of each wattmeter.
- Calculate the total apparent power absorbed by the load.

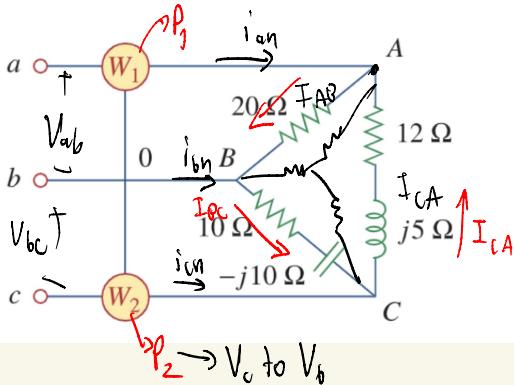Unbalance load
 Cannot eq
 $P = V_p I_p \cos\theta$
 Phase voltage / comp.



$$V_{ab} = 208 \angle 0^\circ$$

$$V_{bc} = 208 \angle -120^\circ$$

$$V_{ca} = 208 \angle 120^\circ$$

$$P_1 = |V_{ab}| |I_{an}| \cos(\theta_b - \theta_a)$$

$$I_{an} \Rightarrow I_{AB} - I_{CA}$$

$$I_{AB} = \frac{208\angle 0^\circ}{20} = 10.4 \angle 0^\circ$$

$$I_{CA} \Rightarrow \frac{208\angle 120^\circ}{12 + j5} = 16 \angle 47.38^\circ$$

$$I_{an} \Rightarrow 12.455 - 15.867 j \approx 20.17716 \angle -51.8697^\circ$$

always express in polar form

$$P_1 = |208| (20, 17) \cos (\theta - (-51.697))$$

$$= 2510 \text{ kW}$$

$$P_2 = |V_{cb}| |I_{cn}| \cos (\theta_v - \theta_i)$$

↓

$$\text{flip from } V_{bc} \text{ to } V_{cb} \rightarrow 208 \angle -120 + 180$$

$$V_{cb} = 208 \angle +60$$

$$\tilde{I}_{cn} = \tilde{I}_{ca} - \tilde{I}_{sc}$$

↓

$$\tilde{I}_{ca} \Rightarrow \frac{208 \angle 120}{12 + j5} = 16 \angle 97.38$$

$$\tilde{I}_{sc} \Rightarrow \frac{208 \angle -120}{10 - j0} = 14.708 \angle -75^\circ$$

$$\tilde{I}_{cn} = 30.4 \angle 101.0294$$

$$P_2 = |208| (30.4) \cos (60 - 101.03)$$

$$= 4808 \text{ kW}$$

$$\text{Ans} \quad |S| = \sqrt{s^2}$$

↓
find complex Power = $P + jQ$

$$P = P_T = 4.898 + 2.590 = 7.398$$


for Watt motor $\rightarrow Q_T = \sqrt{3}(P_2 - P_1) = 38 + 0.25$

$$S_T = 7.398 + 3.840j$$

$$\frac{|S|}{T} = 8.575 \text{ kVA}$$

Exercise 3.5 (20%) For the three-phase circuit below, find the average power absorbed by the delta-connected load with

$$Z_{\Delta} = 21 + j24 \Omega.$$

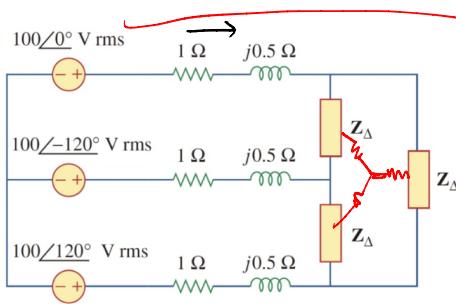

for balance load we know
 $Z_{\Delta} = 3Z_Y \rightarrow Z_Y = \frac{1}{3}Z_{\Delta}$

$$Z_Y = 7 + 8j \Omega.$$

for Y-connected load, $I_L = I_P$; $V_L = \sqrt{3}V_P$

Average power $\rightarrow 3I_P^2Z_P$

$$I_L = \left(\frac{100\angle 0^\circ}{1+j0.5+7+8j} \right) = 8.567 \angle -46.736$$

$$\approx 3(8.567)^2(7+8j)$$


$$S \Rightarrow 1541.263 + 1761.444j$$

$$\begin{matrix} P & \checkmark \\ Q & \downarrow \end{matrix}$$


Hence the average power absorb by the load Z_P

$$= 1541.263 \text{ W}$$

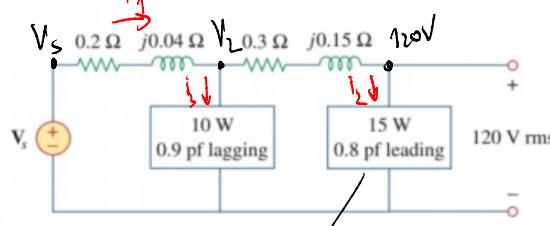Exercise 6.1 (30%) For the circuit, find V_s .



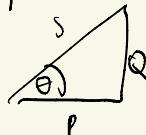for $S_1 = 15 \text{ W}$ and 0.8 pf leading



$$\tan \theta = \frac{Q}{P} \rightarrow Q = P \tan \theta \quad (\cos \theta = 0.8)$$

$\theta \Rightarrow -36.87^\circ$
leading

$$= 15 (\tan(-36.87))$$

$$Q \Rightarrow -11.25$$

$$S_1 = 15 - 11.25j$$

$$S_2 = 10 \text{ W} \rightarrow Q = P \tan \theta \quad (\cos \theta = 0.9)$$

$$\theta = 25.842^\circ$$

$$Q = 10 \tan(25.842)$$

$$\Rightarrow 4.8432 \text{ VAR}$$

$$S_2 = 10 + 4.8432j$$

$$\text{from } S_1 = \tilde{V}_{\text{rms}} \tilde{I}_{\text{rms}}^* \rightarrow \tilde{I}_{\text{rms}}^* = \frac{S_1}{\tilde{V}_{\text{rms}}} = \frac{15 - 11.25j}{120}$$

$$\underline{I}_2^* \Rightarrow 0.125 - j0.09375$$

$$\underline{I}_2 = 0.125 + 0.09375j$$

From the diagram $\rightarrow i_2 = \frac{V_2 - 120}{0.3 + j0.15}$

$$V_2 = (0.125 + 0.09375j)(0.3 + j0.15) + 120$$

$$V_2 \Rightarrow 120.035 + 0.04687j$$



$$120.035 + 0.04687j \\ i_{S0} \quad S_2 = 90 + 4.8432j$$

$$S = V_{rms} \underline{I}_2^*$$

$$\underline{I}_B^* = \frac{S}{V_{rms}} = \frac{(90 + 4.8432j)}{(120.035 + 0.04687j)}$$

$$\underline{I}_B^* = 0.09256 \angle 25.85^\circ$$

$$\underline{I}_3 = 0.09256 \angle -25.85^\circ$$


$$= 0.0867 - j0.0105$$

$$i = i_2 + i_3 = (0.2087 + 0.05325j)$$


$$j = \frac{V_s - V_2}{0.2 + j0.04} \Rightarrow$$

$$V_s \Rightarrow 120.06 \angle 0.03^\circ V$$

Exercise 6.2 (15%) Obtain the average power absorbed by the 6-kΩ resistor in the circuit.

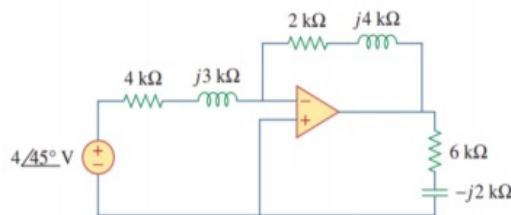

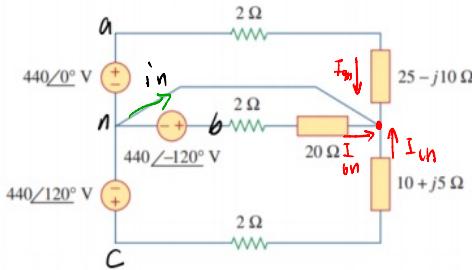Exercise 6.3 (20%) Determine the current in the neutral line.



$$i_n = -(i_a + i_b + i_c)$$

$$i_a = \frac{440 \angle 0^\circ}{2 + (25 - j10)} \Rightarrow (11.33 + 5.3076j)$$

$$i_b = \frac{440 \angle -120^\circ}{2 + 20} = -10 - 17.32j$$

$$i_c = \frac{440 \angle 120^\circ}{2 + (10 + j5)} = -4.35 + 33.565j$$


$$i_n = -(i_a + i_b + i_c)$$

$$i_n = 0.02 - 21.553j$$


↓

$$i_n = 21.553 \angle -89.95^\circ$$

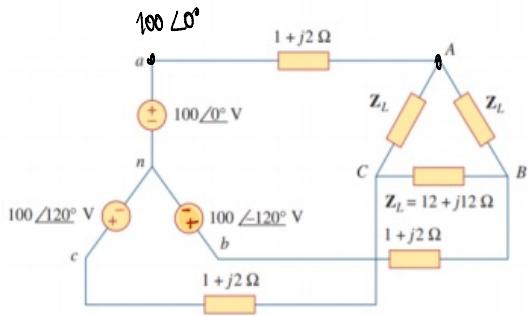Exercise 6.4 (15%) Obtain the line currents in the three-phase circuit.



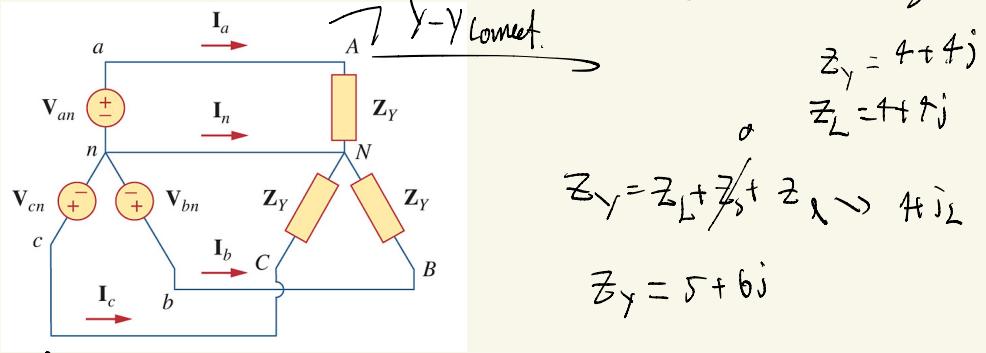Change to Y-Y Connection as it's easier $\rightarrow Z_\Delta = 3Z_Y \rightarrow Z_Y = \frac{1}{3}Z_\Delta$




for Y-Y connected

$$I_a = \frac{V_{an}}{Z_Y} = \frac{100}{5+6j} = 12.8036 \angle -50.197^\circ$$

$$I_b = 12.8036 \angle -170.197^\circ$$

$$I_c = 12.8036 \angle 69.8058^\circ$$

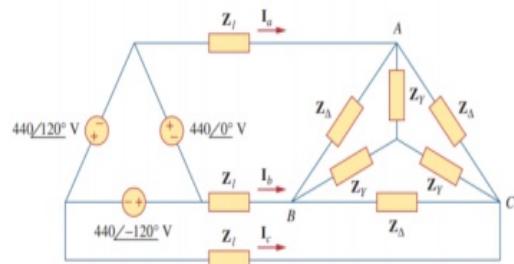Exercise 6.5 (20%) Find the line currents in the three-phase network. Take $Z_{\Delta} = 12 - j15\Omega$, $Z_Y = 4 + j6\Omega$, $Z_l = 2\Omega$.



Example 12.8 Two balanced loads are connected to a 240-kV rms 60-Hz line, as shown in Fig. 12.22(a). Load 1 draws 30 kW at a power factor of 0.6 lagging, while load 2 draws 45 kVAR at a power factor of 0.8 lagging. Assuming the *abc* sequence,

Load 1 $\rightarrow 30 \text{ kW}$; $p_f = 0.6 \rightarrow$ lagging θ ; $\angle \theta$

$$P$$


$$P_f = \frac{P}{|S|} = 0.6 = \frac{30 \text{ kW}}{|S|} \rightarrow |S| = \frac{30 \text{ kW}}{0.6} = 50 \text{ kV}$$

$$\cos \theta = 0.6 \rightarrow \theta = 53.13^\circ$$

$$(\theta_2 - \theta_1)$$

$$(\text{Complex power load 1}) \rightarrow S = |S| \angle \theta_2 - \theta_1 \rightarrow 50 \angle 53.13^\circ \approx 30 + 40j \text{ kW}$$

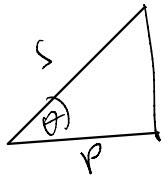Load 2: $Q = 45 \text{ kVAR}$; $p_f = 0.8 \rightarrow \cos \theta = 0.8 \rightarrow \theta = 36.87^\circ$



$$\tan \theta = \frac{Q}{P} \rightarrow P = \frac{Q}{\tan \theta} = \frac{45 \text{ kVAR}}{\tan 36.87^\circ}$$

$$P = 60$$

$$S = (60 + 45j) \text{ kW}$$

$$(\text{Total} \rightarrow S_{\text{total}} = S_1 + S_2 = (30 + 40j) + (60 + 45j) = 90 + 85j \text{ kVA})$$

$$P = 90$$

$$Q = 85$$

The line current $\rightarrow P = \sqrt{3} V_L I_w \cos \theta$

$$\sqrt{3} \frac{240}{(240 \angle (0.53.13^\circ))} = I_L \rightarrow I_L = 0.2978 \text{ A}$$

(L) The kVAR rating = $Q_C \rightarrow P_C \tan \theta_1 - \tan \theta_2$)

$$= \theta_1 = 53.13^\circ; \theta_2 \rightarrow$$

$$\cos \theta = 0.8$$

$$\theta_C = 25.84^\circ$$

determine: (a) the complex, real, and reactive powers absorbed by the combined load, (b) the line current, and (c) the kVAR rating of the three capacitors Δ -connected in parallel with the load that will raise the power factor to 0.9 lagging and the capacitance of each capacitor.



$$= 90 \text{ C tan}(43.36) - \tan(25.892)$$

$$Q_c = 41.400 \text{ kVAR}$$

\rightarrow Capacitance of each capacitor $\rightarrow C = \frac{Q_c}{WV^2}$ for each capacitor need to divide by 3

$$= \frac{Q_c}{3} = \frac{41.400}{3} \approx 13.8$$

$$C = \frac{13.8 \times 10^{-9}}{(2\pi \times 60)(240)^2}$$

$$= 6.355 \times 10^{-10} \text{ F}$$

Example 12.9 The unbalanced Y-load of Fig. 12.23 has balanced voltages of 100 V and the acb sequence. Calculate the line currents and the neutral current. Take $Z_A = 15 \Omega$, $Z_B = 10 + j5 \Omega$, $Z_C = 6 - j8 \Omega$.

balance voltage of 100V.

$$\tilde{V}_{AB} \Rightarrow 100 \angle 0^\circ$$

$$\tilde{V}_{BN} \Rightarrow 100 \angle 120^\circ$$

$$\tilde{V}_{CN} \Rightarrow 100 \angle -120^\circ$$

$$I_A = \frac{\tilde{V}_{AB}}{Z_A} = \frac{100 \angle 0^\circ}{15} = 6.667 \angle 0^\circ \quad ; \quad I_B = \frac{\tilde{V}_{BN}}{Z_B} = \frac{100 \angle 120^\circ}{10 + j5} = 8.943 \angle 93.73^\circ$$

$$I_C = \frac{\tilde{V}_{CN}}{Z_C} = \frac{100 \angle -120^\circ}{6 - j8} \approx 10 \angle -66.87^\circ$$

$$\tilde{I}_n = -(\tilde{I}_A + \tilde{I}_B + \tilde{I}_C)$$

$$\tilde{I}_n = -10.0598 + j0.2679 \approx 10.0634 \angle 178.73^\circ$$


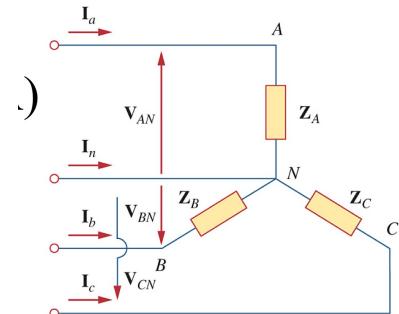


Figure 12.23 Unbalanced three-phase Y-connected load.

Chapter 13 Problem

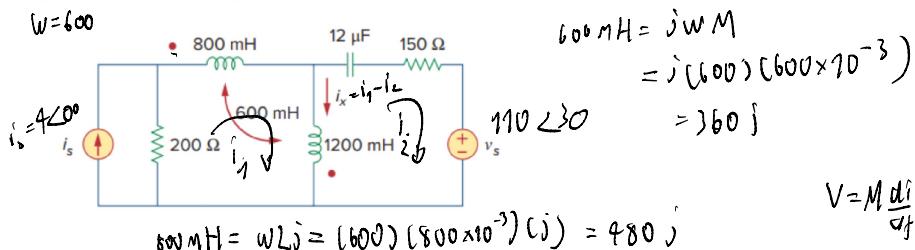
Exercise 7.1 (20%) Find the unknown current i_x in the circuit below, where $i_s = 4 \cos(600t) A$ and $v_s = 110 \cos(600t + 30^\circ) V$



$$1200 \text{ mH} \Rightarrow (1200 \times 10^{-3}) L (600) (j) = 720 j$$

$$12 \text{ NF} = \frac{1}{(600)(12 \times 10^{-6})} j = -138.88 j$$

Change Mutual inductance to phasor form

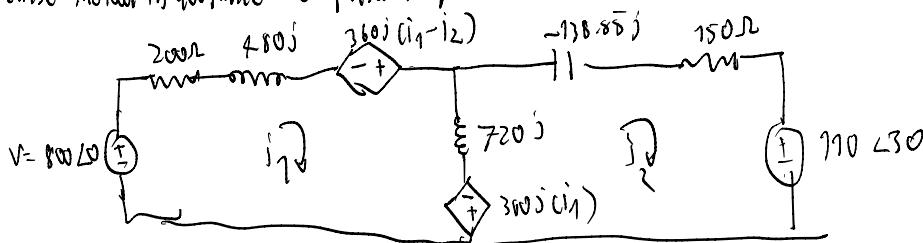

$$\begin{aligned} \text{KVL at } I_1 &\rightarrow 200i_1 + 480j i_1 - 360j(i_1 - i_2) + 720j(i_1 - i_2) \\ &- 360j i_1 - 800\angle 0^\circ = 0 \end{aligned}$$

$$(480j + 200)i_1 + (-360j) i_2 = 800 \rightarrow (1)$$

$$\begin{aligned} \text{KVL at } I_2 &\rightarrow -138.88j i_2 + 150i_2 + 110 + 360j i_1 + 720j(i_2 - i_1) \\ &= 0 \\ (-360j) i_1 + (581.12j + 150) i_2 &= -110 \rightarrow (2) \end{aligned}$$

$$\begin{vmatrix} (480j + 200) & -360j \\ -360j & (581.12j + 150) \end{vmatrix} \begin{vmatrix} i_1 \\ i_2 \end{vmatrix} = \begin{pmatrix} 800 \\ -110 \end{pmatrix}$$

$$\Delta = 222867 \angle 122.375^\circ$$

$$\Delta_1 = \begin{vmatrix} 800 & -360j \\ -790 & (581.72) + 150j \end{vmatrix} \Rightarrow 441901.2793 \angle 74.2432^\circ$$

$$\Delta_2 = \begin{vmatrix} (400j + 200) & 800 \\ -360j & -790 \end{vmatrix} \Rightarrow 236226.67 \angle 95.34325^\circ$$

$$i_1 = \frac{\Delta_1}{\Delta} = 1.9828 \angle -48.1378^\circ$$


$$i_2 = \frac{\Delta_2}{\Delta} = 1.05994 \angle -27.0313^\circ$$

$$i_x = i_1 - i_2 \Rightarrow 1.0646 \angle -69.134^\circ$$


}

$$i_x = 1.9 \cos(600t - 66.0^\circ) A$$

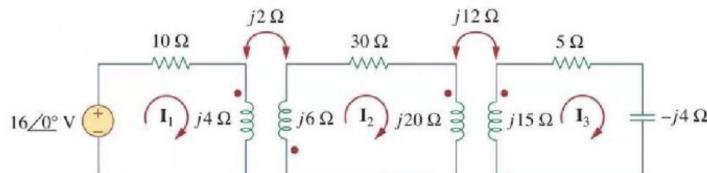Exercise 7.3 Determine I_1, I_2, I_3 in the circuit.



Phasor form

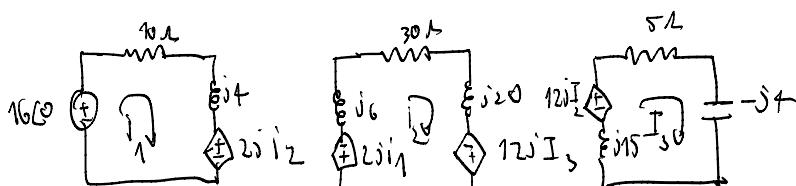

$$\text{KVL } I_1 \quad 10i_1 + 4j i_1 + 2j i_2 - 16 = 0$$

$$(10+4j) i_1 + 2j i_2 = 16 \rightarrow (1)$$

$$\text{KVL } I_2 \quad 30i_2 + 20j i_2 - 12j I_3 + 2j i_1 + 6j i_2 = 0$$

$$2j i_1 + (30+26j) i_2 - 12j I_3 = 0 \rightarrow (2)$$

$$\text{KVL } I_3 \rightarrow 5I_3 - 4j I_3 + 15j I_3 - 12j I_2 = 0$$

$$-12j I_2 + (11j + 5) I_3 = 0 \rightarrow (3)$$

From (1.)

$$(10+4j) i_1 = 16 - 2j i_2$$

$$i_1 = \frac{16}{10+4j} - \frac{2j i_2}{10+4j} \rightarrow \text{Plug into (2)}$$

$$2j \left(\frac{16}{10+4j} - \frac{2j i_2}{10+4j} \right) + (30+26j) i_2 - 12j I_3 = 0$$

$$\left(\frac{32}{29} + \frac{80}{29} j \right) + \left(\frac{880}{29} + \frac{750}{29} j \right) I_2 - 12j I_3 = 0$$

↓
(4)

solve 4 and 3

$$\begin{vmatrix} -12j & (11j+5) \\ \left(\frac{880}{29} + \frac{750}{29} j \right) & -12j \end{vmatrix} \begin{matrix} I_2 \\ I_3 \end{matrix} = \begin{vmatrix} 0 \\ -\frac{32}{29} - \frac{80}{29} j \end{vmatrix}$$

$$\Delta = 463.24 \angle -99.39^\circ$$


$$\Delta_1 = \begin{vmatrix} 0 & (11j+5) \\ -\frac{32}{29} - \frac{80}{29} j & -12j \end{vmatrix}$$

$$\downarrow \angle = 35.9 \angle 133.754^\circ$$

$$\Delta_2 \Rightarrow \begin{vmatrix} -12j & 0 \\ \left(\frac{880}{29} + \frac{750}{29} j \right) & -\frac{32}{29} - \frac{80}{29} j \end{vmatrix}$$

$$\downarrow \angle = 35.653 \angle 158.198^\circ$$

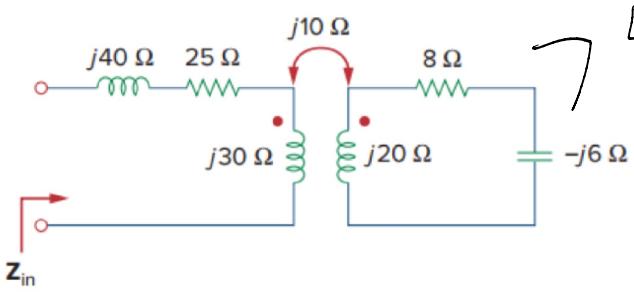Exercise 7.4 Find the input impedance Z_{in} of the circuit below.



Linear transformer

$$jWM = 10$$

$$WM = 10$$

$$Z_{in} = R_1 + jWL_1 + \frac{W^2 M^2}{R_2 + jWL_2 + Z_L}$$

$$\Rightarrow (j40 + 25) + 30j + \frac{(WM)^2}{(8 - j6) + j20}$$

$$Z_1 = 70j + 25 + \frac{10^2}{8 + 1j}$$

$$Z_{in} = 70.452 \angle 66.53^\circ$$

- 13.20** Determine currents \mathbf{I}_1 , \mathbf{I}_2 , and \mathbf{I}_3 in the circuit of Fig. 13.89. Find the energy stored in the coupled coils at $t = 2$ ms. Take $\omega = 1,000 \text{ rad/s}$.


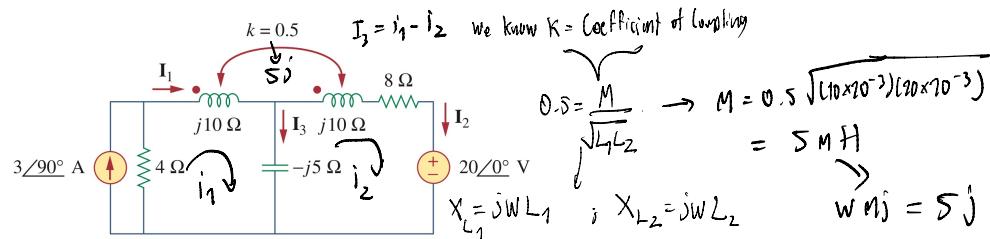


Figure 13.89

For Prob. 13.20.
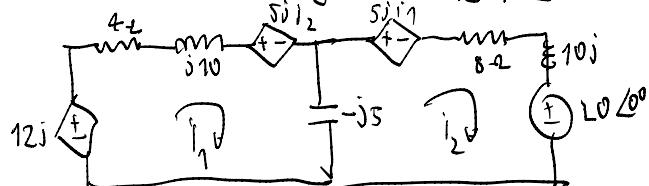
$$\text{Energy Store} \rightarrow W = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + M_{12} I_1 I_2$$



$$\text{KVL at } i_1 \rightarrow 4i_1 + 10j i_1 + 5j i_2 - 5j(i_1 - i_2) - 12j = 0$$

$$(4 + 5j)i_1 + 10j i_2 = 12j \rightarrow (1)$$

$$\text{KVL at } i_2 \rightarrow 5j i_1 + 8i_2 + 20 - 5j(i_2 - i_1) + 10j i_2 = 0$$

$$10j i_1 + (5j + 8)i_2 = -20 \rightarrow (2)$$

$$\begin{vmatrix} (4+5j) & 10j \\ 10j & (5j+8) \end{vmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} 12j \\ -20 \end{pmatrix}$$

$$\Delta = 107 + 60j$$

$$\Delta_1 = \begin{vmatrix} 12j & 10j \\ -20 & (5j+8) \end{vmatrix} = -60 + 296j$$

$$\Delta_2 = \begin{vmatrix} (t+5j) & 12j \\ 10j & -20 \end{vmatrix} = 40 - 100j$$

$$i_1 = \frac{\Delta_1}{\Delta} = 2.46196 \angle 72.977^\circ$$

$$i_2 = \frac{\Delta_2}{\Delta} = 0.878 \angle -97.48^\circ$$

$$i_1 = i_1 - i_2 \Rightarrow 3.329 \angle 74.89^\circ$$

Energy Store $\rightarrow W = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + M_{12} I_1 I_2$ \curvearrowright Need to use instantaneous value.

$$i_1(t) = 2.46196 \sqrt{2} (\cos(1000t + 72.977))$$

Convert to peak R

$$i_2(t) = 0.878 \sqrt{2} (\cos(1000t - 97.48))$$

$$\text{at } t = 2 \text{ ms} = 0.002 = 1000t \approx 2 \text{ rad} = 114.6 \rightarrow 2 \left(\frac{180}{\pi}\right)$$

$$i_1(t) = 2.46196 \sqrt{2} (\cos(114.6 + 72.977)) = -3.47$$

$$i_2(t) = 1.19$$

$$W = \frac{1}{2}(0.01)(-3.45)^2 + \frac{1}{2}(0.01)(1.19)^2 + \frac{1}{6}(5 \times 10^{-3}) (-3.45)(1.19)$$

$$W = 0.046 \text{ J}$$

13.49 Find current i_x in the ideal transformer circuit shown in Fig. 13.114.

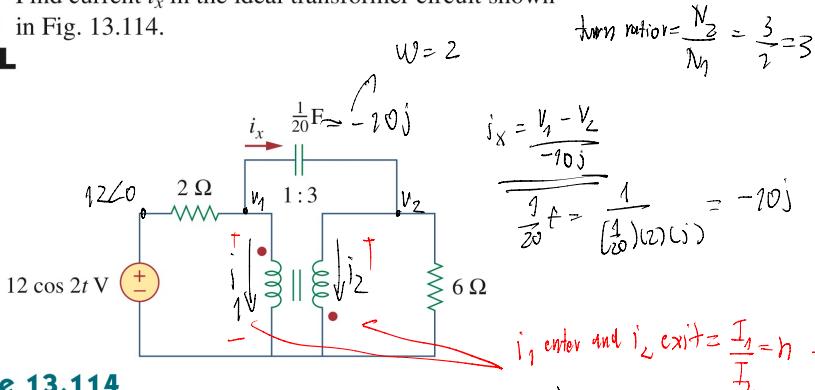


Figure 13.114

For Prob. 13.49.

$$\text{KVL at } v_1 \rightarrow \frac{v_1 - 12\angle 0}{2} + \frac{v_1 - v_2}{-10j} + i_1 = 0 \quad \frac{v_2}{v_1} = -3 \rightarrow \frac{v_2}{v_1} = -3$$

$$(\frac{1}{2} + \frac{1}{10}j)v_1 + (-\frac{1}{10}j)v_2 + i_1 = 0 \rightarrow (1)$$

KVL at v_2

$$\frac{v_2 - v_1}{-10j} + \frac{v_2}{6} + i_2 = 0$$

$$(-\frac{1}{10}j)v_1 + (\frac{1}{6} + \frac{1}{10}j)v_2 + i_2 = 0 \rightarrow (2)$$

$$v_2 = -3v_1$$

$$\text{apply } v_2 = -3v_1 \text{ and } i_1 = 3i_2$$

$$(\frac{1}{2} + \frac{1}{10}j)v_1 + (-\frac{1}{10}j)(-3v_1) + 3i_2 = 0$$

$$(\frac{1}{2} + \frac{2}{5}j)v_1 + 3i_2 = 0 \rightarrow (3)$$

$$(-\frac{1}{10}j)v_1 + (\frac{1}{6} + \frac{1}{10}j)(-3v_1) + i_2 = 0$$

$$(-\frac{1}{2} - \frac{2}{5}j)v_1 + i_2 = 0 \rightarrow (4)$$

$$\text{Solve 3/4} \rightarrow \begin{vmatrix} \left(\frac{1}{2} + \frac{2}{5}j\right) & 3 \\ \left(-\frac{1}{2} - \frac{2}{5}j\right) & 1 \end{vmatrix} \begin{vmatrix} |v_1| \\ |i_2| \end{vmatrix} = \begin{vmatrix} 0 \\ 0 \end{vmatrix}$$

$$\Delta \Rightarrow 2 + \frac{8}{3}j$$

$$\Delta_1 = \begin{vmatrix} 6 & 3 \\ 0 & 1 \end{vmatrix}$$

$$\Delta_2 = \begin{vmatrix} 6 & \left(\frac{1}{2} + \frac{2}{5}j\right) \\ 0 & \left(-\frac{1}{2} - \frac{2}{5}j\right) \end{vmatrix}$$

$$\Rightarrow \left(3 + \frac{12}{5}j\right)$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{6}{\left(2 + \frac{8}{5}j\right)} = 2.3426 \angle -38.66^\circ$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{\left(3 + \frac{12}{5}j\right)}{\left(2 + \frac{8}{5}j\right)} = \frac{3}{2} A$$

$$V_1 = 1.83 - 1.46j$$

$$V_2 = -3V_1 = -5.487 + 4.39j$$

$$I_X = \frac{V_1 - V_2}{-10j} = 0.585 + 0.7397j$$

↓

$$0.937 \angle 51.36^\circ$$

- 13.12 Determine the equivalent L_{eq} in the circuit of Fig. 13.81.

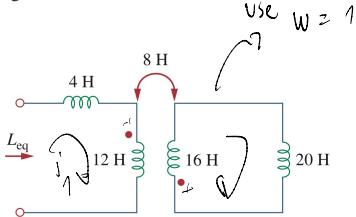


Figure 13.81

For Prob. 13.12.

$$Z_{in} = \frac{V}{I_0} \rightarrow \frac{V}{I} \rightarrow \text{apply } V=1$$

$$i_0 = j_1$$

$$i_0 = 4j \quad i_1 = 8j i_2 \quad i_2 = 16j i_1 + 20j$$

$$kv i_1 + 4j i_1 + 8j i_2 + 12j i_1 - 1 = 0$$

$$16j i_1 + 8j i_2 = 1 \rightarrow (1)$$

$$kvl i_2 \rightarrow 20j i_2 + 16j i_2 + 8j i_1 = 0$$

$$8j I_1 + 36j i_2 = 0 \rightarrow (2)$$

$$\begin{vmatrix} 16j & 8j \\ 8j & 36j \end{vmatrix} \begin{vmatrix} i_1 \\ i_2 \end{vmatrix} = \begin{matrix} 1 \\ 0 \end{matrix}$$

$$\Delta = -512$$

$$\Delta_1 = \begin{vmatrix} 1 & 8j \\ 0 & 36j \end{vmatrix} = 36j$$

$$\Delta_2 = \begin{vmatrix} 16j & 1 \\ 8j & 0 \end{vmatrix} = -8j$$

$$i_1 = \frac{\Delta_1}{\Delta} = -\frac{9}{128}j \quad i_2 = \frac{\Delta_2}{\Delta} = \frac{1}{64}j$$

$$j i_1 = i_0$$

$$Z_{in} = \frac{1}{\left(\frac{-9}{128}j\right)} = \frac{128}{9}j$$

$$jL = Z_{in}$$

$$\frac{1}{jL} = jL_{eq}$$

$L =$

$$L_{eq} = \frac{1}{j\left(\frac{-9}{128}j\right)}$$

$$= 14.2275$$

13.9 Find V_x in the network shown in Fig. 13.78.


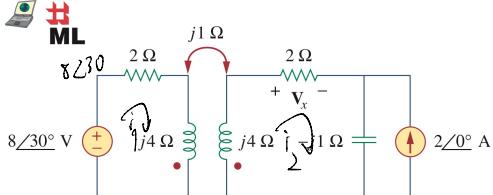


Figure 13.78

For Prob. 13.9.

Phasor form

s and voltages are rms.

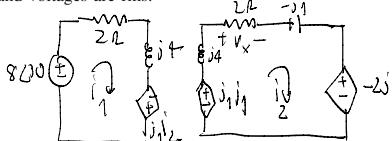

$$\text{KVL at } i_1 \rightarrow 2i_1 + 4j i_1 - j i_2 - 8\angle 30^\circ = 0$$

$$(2+4j)i_1 - j i_2 = 8\angle 30^\circ \rightarrow (1)$$

$$\text{KVL at } i_2 \rightarrow 2i_2 - j i_2 - 2j - j i_1 + 4j i_2 = 0$$

$$-j i_1 + (2+3j) i_2 = 2j \rightarrow (2)$$

$$\begin{vmatrix} 2+4j & -j \\ -j & 2+3j \end{vmatrix} \begin{vmatrix} i_1 \\ i_2 \end{vmatrix} = \begin{vmatrix} 8\angle 30^\circ \\ 2j \end{vmatrix}$$

$$\Delta = -7+14j$$

$$\Delta_1 = \begin{vmatrix} 8\angle 30^\circ & -j \\ 2j & 2+3j \end{vmatrix} \Rightarrow -0.1936 + 28.78j$$

$$\Delta_2 = \begin{vmatrix} 2+4j & 8\angle 30^\circ \\ -j & 2j \end{vmatrix} \Rightarrow -12 + 10.93j$$

$$i_2 = \frac{\Delta_2}{\Delta} = 0.967 + 0.373j \approx 1.037 \angle 21.106^\circ$$

$$V_x = i_2(1\Omega) = 1.935 + 0.747j$$

13.14 Obtain the Thevenin equivalent circuit for the circuit in Fig. 13.83 at terminals a-b.


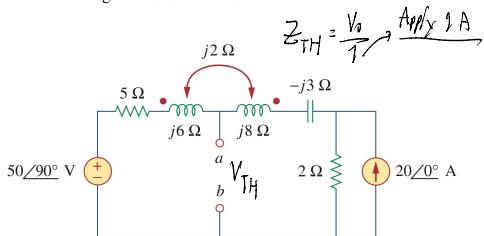


Figure 13.83

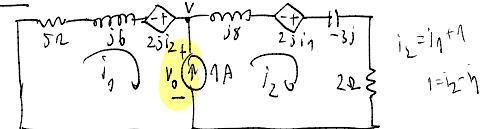Find $Z_{TH} \rightarrow$ Close all independent source apply current 1A



$$\text{Super mesh } i_1, i_2 \rightarrow 5i_1 + 2j i_1 - 2j i_2 + 8j i_2 - 2j i_1 - 3j i_2 + 2j = 0$$

$$(5+4j)i_1 + (3j+2)i_2 = 0 \rightarrow (1)$$

$$j_3 - i_1 = 1 \rightarrow i_1 = j_3 - 1 \rightarrow (2)$$

$$\text{sub (2) to (1) give } i_1 = -(2+j)3 / 7+j7$$

$$\text{Also from left loop KVL } \rightarrow (5+6j)i_1 - 2j(i_1 + 1) + V_o = 0$$

$$(5+6j)i_1 + 2j + V_o = 0$$

$$V_o = 2j - [(5+6j)(-\frac{(2+j)3}{7+j7})]$$

$$V_o = 1.5 + 3.7857j \approx 4.07 \angle 68.385^\circ$$

find V_{TH}

*13.22 Find current \mathbf{I}_o in the circuit of Fig. 13.91.

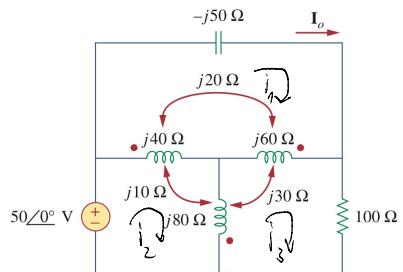


Figure 13.91

For Prob. 13.22.

13.18 Find the Thevenin equivalent to the left of the load

Z in the circuit of Fig. 13.87.

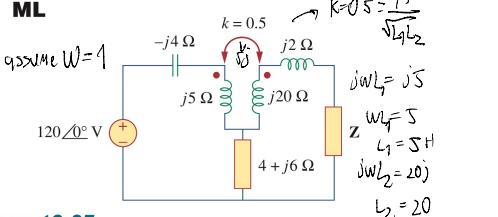


Figure 13.87

For Prob. 13.18.


Note that we need to find $\bar{Z}_{TH} \rightarrow \frac{V_{TH}}{I_{SC}}$

$$M = 0.5 \sqrt{1000}$$

$$= 5 \text{ H}$$

$$\text{jwL} = 5\text{j}$$

$$L_2 = 20$$

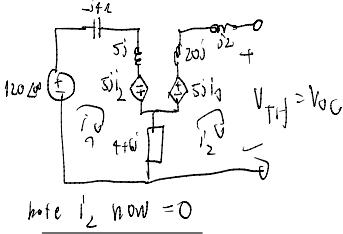

$$\text{note } i_2 \text{ now } = 0$$

$$\text{KVL mesh } i_1 \rightarrow -9j i_1 + j5 i_1 - 5j i_2 + (4+6j)(i_1 - i_2) = 120$$

$$(4+7j)i_1 = 120$$

$$i_1 = 14.88 \angle -60.28^\circ$$

To find $V_{TH} \rightarrow \text{KVL at } i_2$


$$V_{TH} + 4+6j(i_2 - i_1) - 5j i_1 = 0$$

$$V_{TH} = 5j i_1 + (4+6j)i_1$$

$$= (4+11j)i_1$$

$$V_{TH} = 179.22 \angle 9.71^\circ$$

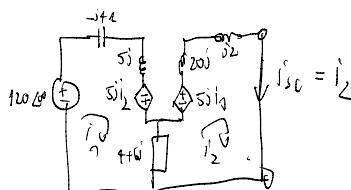To find $I_{SC} \rightarrow$ We short circuit



$$-9j i_1 + 5j i_1 - 5j i_2 + (4+6j)(i_1 - i_2) = 120$$

$$(4+7j)i_1 - (4+11j)i_2 = 120 \rightarrow (1)$$

$$\text{Mesh 2: } j2 i_2 + (4+6j)(i_2 - i_1) - 5j i_1 + 20j i_2 = 0$$

$$-(4+11j)i_1 + (9+14j)i_2 = 0 \rightarrow (2)$$

Solve (1) / (2) \Rightarrow

$$I_2 = I_{SC} = 18.3891 \angle -75.2481^\circ$$

$$\bar{Z}_{TH} = \frac{V_{TH}}{I_{SC}} \Rightarrow 19.32 \angle 85.01^\circ$$

Chapter 14 Practice

14.11 Sketch the Bode plots for

$$H(\omega) = \frac{0.2(10 + j\omega)}{j\omega(2 + j\omega)}$$

$$H(\omega) = \frac{0.2 \times 10 \left(1 + \frac{j\omega}{10} \right)}{2 \times j\omega \left(1 + \frac{j\omega}{2} \right)}$$

$$= \frac{\left(1 + \frac{j\omega}{10} \right)}{j\omega \left(1 + \frac{j\omega}{2} \right)}$$

Type 2 Pole

$$(j\omega)^{-1} \rightarrow H(\omega) \Rightarrow -20 \log_{10}(j\omega)$$

$$\phi = -90$$

$$\text{Type 3 Zeros} \rightarrow H(\omega) \rightarrow 0 \quad \omega \leq 10$$

$$20 \quad \omega \geq 10$$

$$\phi \rightarrow 0 \quad \omega \leq 1$$

$$45 + 45 \log_{10}\left(\frac{\omega}{10}\right) \quad 1 \leq \omega \leq 100$$

↑ 5 db/decade



90° $\omega \geq 100$

↓ magnitude slope = 0

$$\text{Type 3 Pole} \rightarrow H(\omega) \rightarrow 0 \quad \omega \leq 2$$

$$\phi \rightarrow 0 \quad w \leq 0.2$$
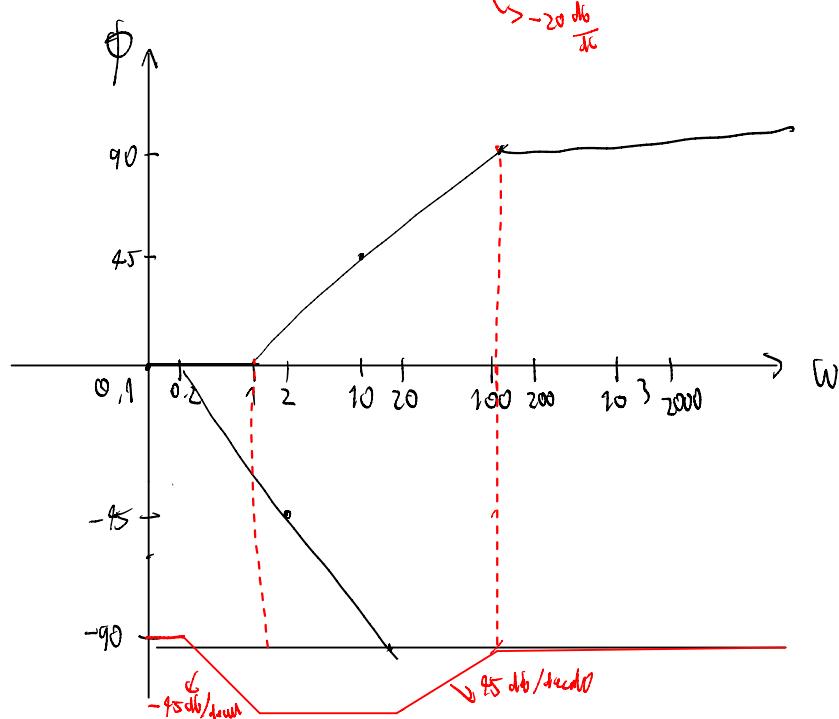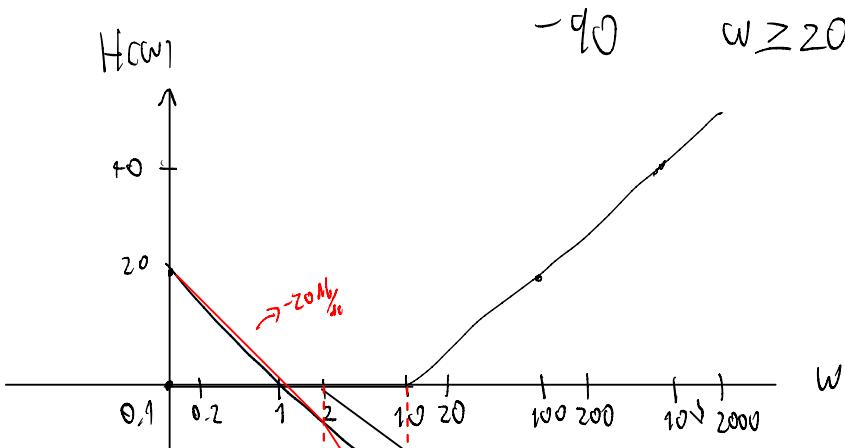
$$-45 - 45 \log_{\frac{1}{2}}(0.2) \leq w \leq 20$$



14.12 A transfer function is given by

$$T(s) = \frac{100(s + 10)}{s(s + 10)}$$

Sketch the magnitude and phase Bode plots.

$$\begin{aligned} S=j\omega \\ T(s) &= \frac{100(j\omega + 10)}{j\omega(j\omega + 10)} \xrightarrow{\text{Type 1}} \frac{100}{j\omega} \left(\frac{j\omega}{10} + 1 \right) \xrightarrow{\text{Type 1} \text{ Zeros}} \\ &= \frac{100 \times 10 \left(\frac{j\omega}{10} + 1 \right)}{j\omega \times 10 \left(\frac{j\omega}{10} + 1 \right)} \xrightarrow{\text{Type 2 } (j\omega)^{-1}} \frac{100}{j\omega} \left(\frac{j\omega}{10} + 1 \right) \xrightarrow{\text{Type 2 } (j\omega)^{-1} \text{ Pole}} \\ &\xrightarrow{\text{Type 1 } H(\omega) \rightarrow 20 \log_{10}(100) = 40} K \end{aligned}$$

$$\phi \rightarrow \text{as } K > 0 \rightarrow \phi = 0$$

$$\text{Type 2 } j\omega^{-1} \rightarrow f(\omega) = -20 \rightarrow \text{slope}$$

$$\phi = -90^\circ$$


$$\text{Type 3-} \quad H(\omega) \begin{cases} 0 & \omega \leq 10 \\ 20 & \omega \geq 10 \end{cases}$$

$$\phi \begin{cases} 0 & \omega \leq 1 \\ 45^\circ_{\text{dec}} & 1 \leq \omega \leq 100 \\ 90^\circ & \omega \geq 100 \end{cases} \rightarrow \text{slope} = 0$$

$$\text{Type 3 Pole} \rightarrow H(\omega) \begin{cases} 0 & \omega \leq 10 \\ -20 & \omega \geq 10 \end{cases}$$

$$\phi \begin{cases} 0 & \omega \leq 1 \\ -45^\circ & 1 \leq \omega \leq 100 \\ -90^\circ & \omega \geq 100 \end{cases}$$
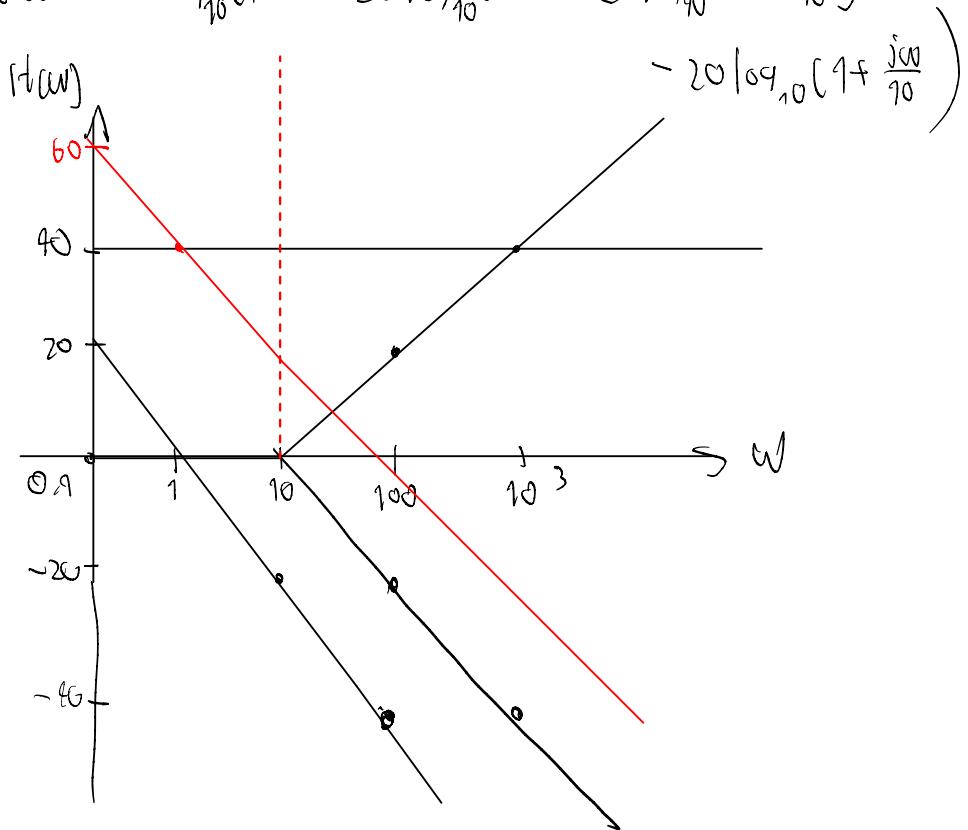
$$H(j\omega) = 20 \log_{10}(100) - 20 \log_{10}(j\omega) + 20 \log_{10}\left(1 + \frac{j\omega}{10}\right)$$



14.13 Construct the Bode plots for

$$G(s) = \frac{0.1(s + 1)}{s^2(s + 10)}, \quad s = j\omega$$

$$G(j\omega) = \frac{0.1(j\omega + 1)}{j\omega^2(j\omega + 10)} = \frac{0.1(j\omega + 1)}{j\omega^2 \times 10(\frac{j\omega}{10} + 1)} = \frac{\frac{1}{100}(j\omega + 1)}{j\omega^2 (\frac{j\omega}{10} + 1)}$$

as constant $K > 0 \rightarrow \phi = 0$

$$H(j\omega) \rightarrow 20 \log_{10} \left(\frac{1}{100} \right) = -40$$

$$\phi = 0$$

Type 2 pole $(j\omega)^{-2}$

$$H(j\omega) = -40 \frac{db}{decade}$$

$$\phi = -90^\circ$$

Type 3 zero $\rightarrow (j\omega + 1)$ $\rightarrow z_1 = 1$

$$H(j\omega) \rightarrow 0 \quad \omega \leq 1$$

$$20 \quad \omega \geq 1$$

$$\phi \rightarrow 0 \quad \omega \leq 0.1$$

$$45 \frac{db}{decade} \quad 45 + 45 \log_{10} \left(\frac{\omega}{0.1} \right) \quad 0.1 \leq \omega \leq 10$$

$$90 \quad \omega \geq 10$$

$$\text{slope} = 0; 90^\circ \rightarrow z_1 = 10$$


$$\text{Type 3 Pole} \rightarrow \frac{1}{(j\omega/10 + 1)} \rightarrow H(j\omega) \rightarrow 0 \quad \omega \leq 10$$

$$-20 \quad \omega \geq 10$$

$$\phi \rightarrow \begin{cases} 0 & \omega \leq 1 \\ -45 & 1 \leq \omega \leq 100 \\ -90 & \omega \geq 100 \end{cases}$$


$$H(\omega) = 20 \log_{10} \left(\frac{1}{\sqrt{10}} \right) - 40 \log_{10} (j\omega) + 20 \log_{10} (j\omega + 1) - 20 \log_{10} \left(\frac{j\omega}{10} + 1 \right)$$
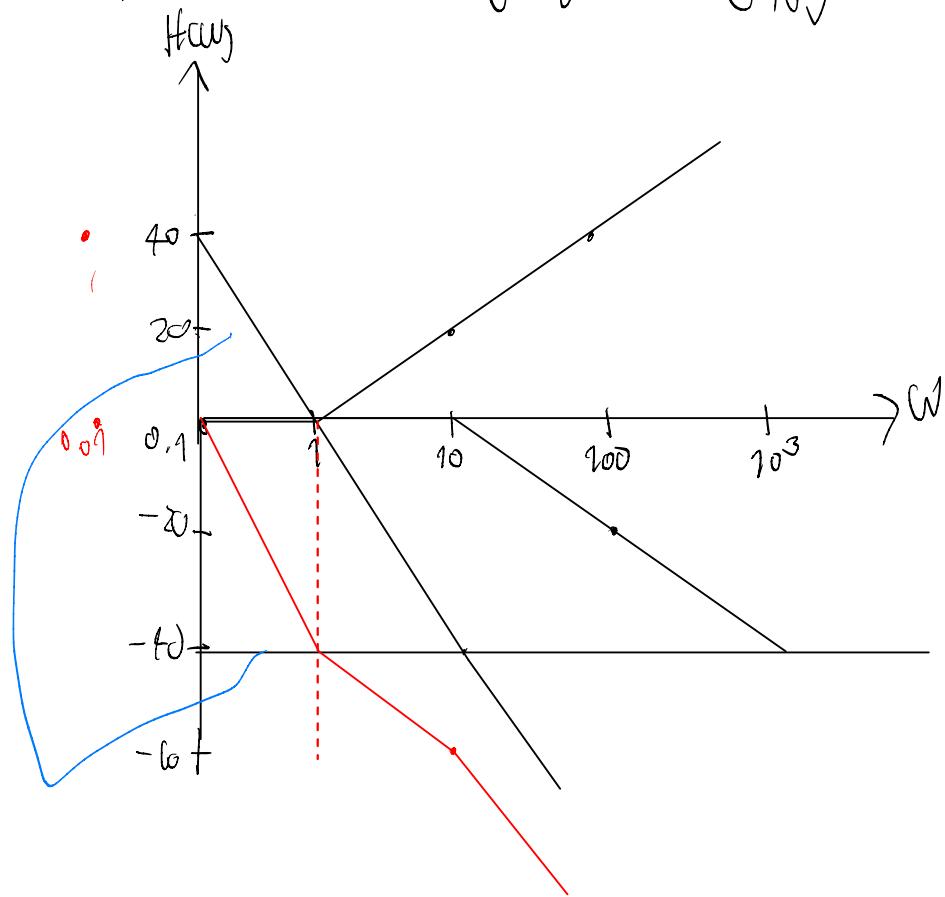
$$\phi \Rightarrow -180 + \tan^{-1} \left(\frac{\omega}{1} \right) - \tan^{-1} \left(\frac{\omega}{10} \right)$$



$\text{magnitude slope} = -40$; $\delta H(\omega) \Rightarrow \text{straight line} = -90$

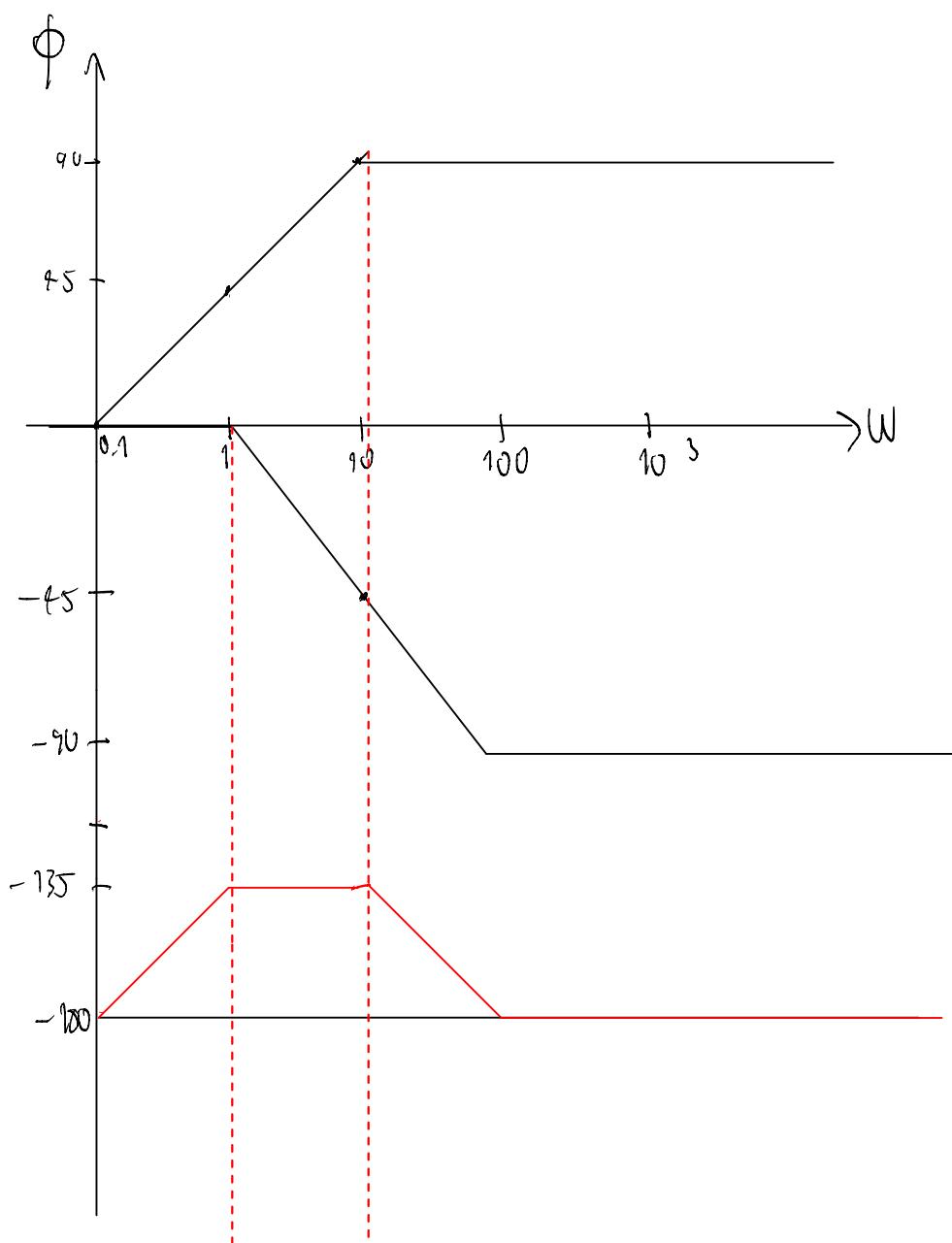$\text{magnitude slope without corner shift} \approx -40 \text{ dB}$



14.15 Construct the Bode magnitude and phase plots for

$$H(s) = \frac{2(s+1)}{(s+2)(s+10)}, \quad s = j\omega$$

$$\begin{aligned} H(s) &= \frac{2(j\omega + 1)}{(j\omega + 2)(j\omega + 10)} \\ &= \frac{2(j\omega + 1)}{10 \times 2 \times \left(\frac{j\omega}{2} + 1\right)\left(\frac{j\omega}{10} + 1\right)} = \frac{\frac{1}{10}(j\omega + 1)}{\left(\frac{j\omega}{2} + 1\right)\left(\frac{j\omega}{10} + 1\right)} \end{aligned}$$

for constant $\rightarrow \frac{1}{10} \rightarrow 20 \log_{10}\left(\frac{1}{10}\right) \rightarrow H(\omega) \rightarrow -20$

$$\phi \rightarrow 0 \text{ as } k > 0$$

for $j\omega + 1$ $\rightarrow H(\omega) \begin{cases} 0 & \omega \leq 1 \\ 20 & \omega \geq 1 \end{cases}$

$$\phi \begin{cases} 0 & \omega \leq 0.1 \\ 45 & 0.1 \leq \omega \leq 10 \end{cases}$$

$$\underbrace{\frac{1}{(j\omega + 1)}}_{\substack{90^\circ \\ \downarrow \text{slope} = 0}} \rightarrow H(\omega) \begin{cases} 0 & \omega \leq 2 \\ -20 & \omega \geq 2 \end{cases}$$



$$\phi \begin{cases} 0 & \omega \leq 0.2 \\ -45 & 0.2 \leq \omega \leq 20 \\ -90^\circ & \omega \geq 20 \end{cases}$$

$\downarrow \text{slope} = 0$

for $\frac{1}{(\frac{jw}{10} + 1)} \rightarrow H(j\omega) \left\{ \begin{array}{ll} 0 & w \leq 10 \\ -20 & w \geq 10 \end{array} \right.$

$$\phi \left\{ \begin{array}{ll} 0 & w \leq 1 \\ -45 & 1 \leq w \leq 100 \\ -90 & w \geq 100 \end{array} \right.$$

$H(j\omega)$

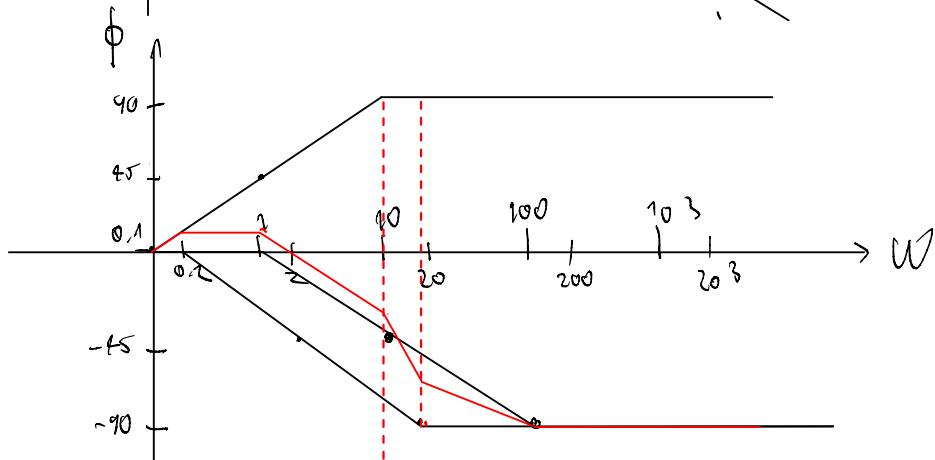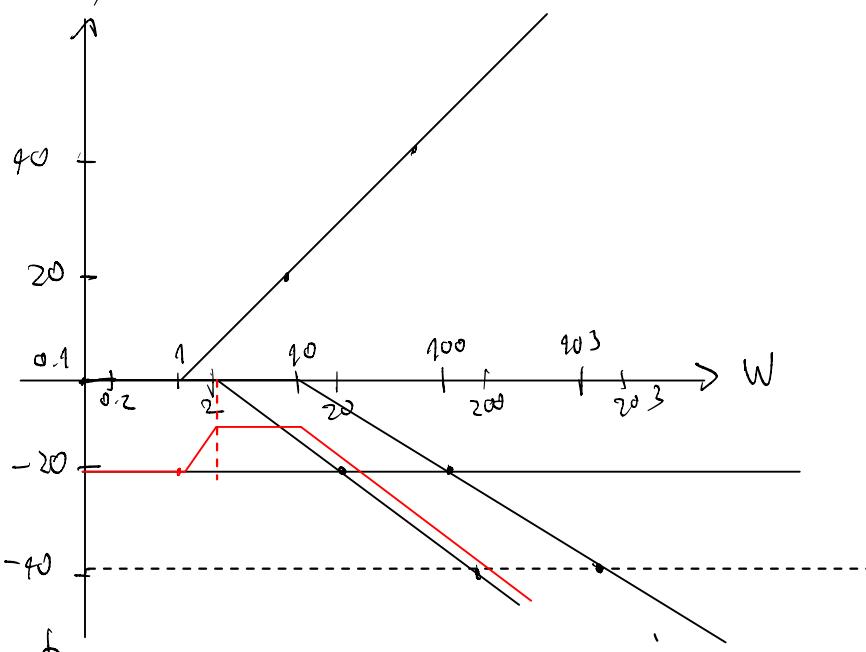

14.16 Sketch Bode magnitude and phase plots for

$$H(s) = \frac{1.6}{s(s^2 + s + 16)}, \quad s = j\omega$$

$$\begin{aligned} H(s) &= \frac{1.6}{j\omega(j\omega^2 + j\omega + 16)} = \frac{1.6}{j\omega \left(\left(\frac{j\omega}{4}\right)^2 + \frac{j\omega}{16} + 1 \right)} \times 16 \\ &\quad \downarrow \\ &= \frac{0.1}{j\omega \left(\left(\frac{j\omega}{4}\right)^2 + \frac{j\omega}{16} + 1 \right)} \end{aligned}$$

Type 1 constant $\rightarrow 0.1$

$$H(\omega) = 20 \log_{10}(0.1) \approx -20$$

$$\phi \Rightarrow 0$$

Type 2 $j\omega^{-1} \rightarrow$

$$H(\omega) \rightarrow -20 \rightarrow \text{slope } \frac{d\phi}{\omega \text{ rad/s}}$$




$$\phi \rightarrow -90^\circ$$

Type 4 $\omega_n = 4$

$$H(\omega) = \begin{cases} 0 & \omega \leq 4 \\ -40 & \omega \geq 4 \end{cases}$$

$$\phi = \begin{cases} 0 & \omega \leq 0.4 \\ -90 - 90 \log_{10} \left(\frac{\omega}{2} \right) & 0.4 \leq \omega \leq 40 \\ -180 & \omega \geq 40 \end{cases}$$

$\rightarrow \text{slope } 0$

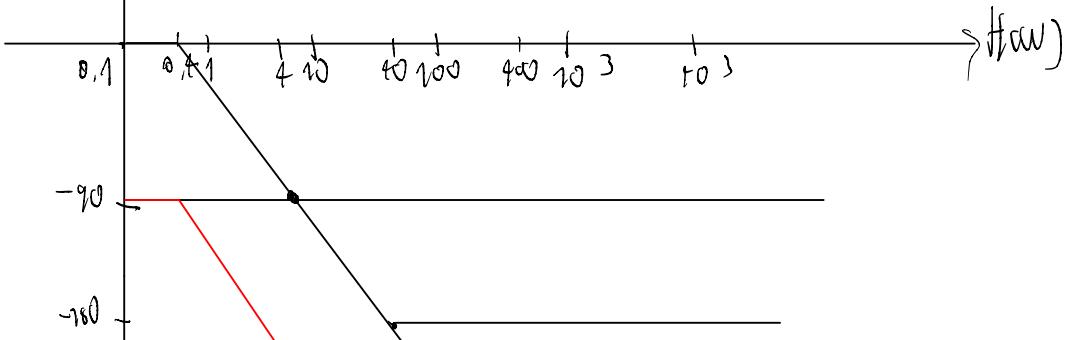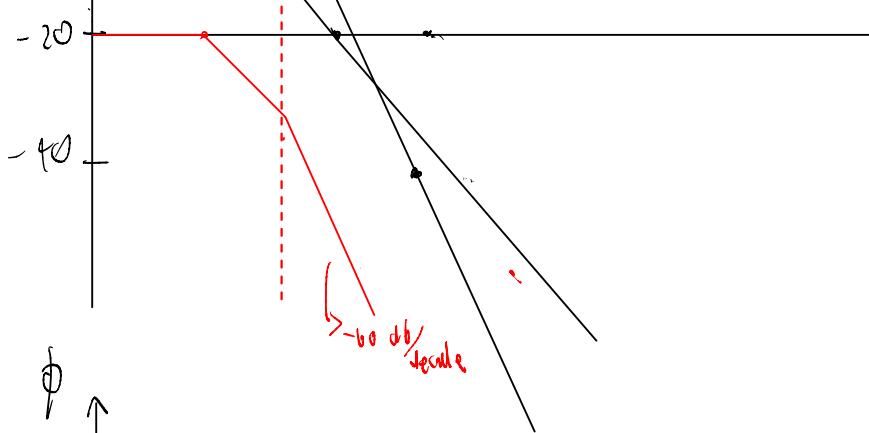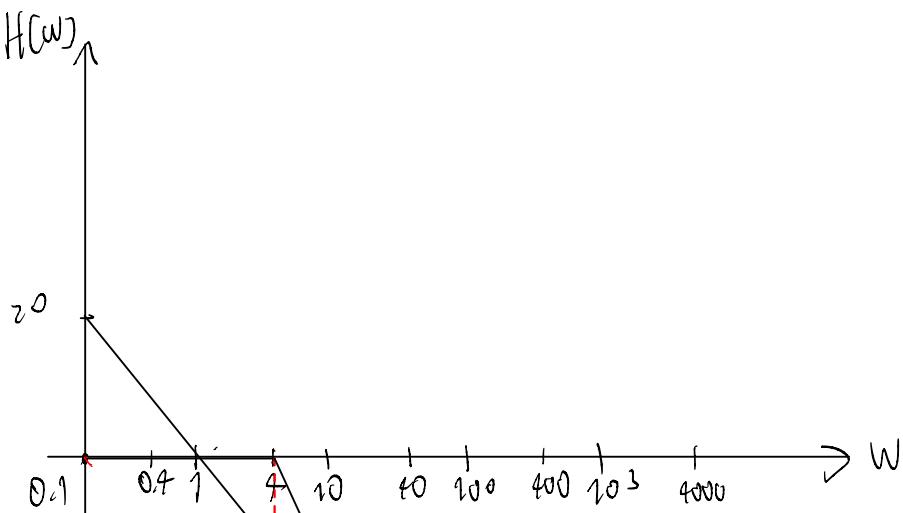

-270

14.17 Sketch the Bode plots for

$$G(s) = \frac{s}{(s+2)^2(s+1)}, \quad s = j\omega$$

$$\begin{aligned} G(j\omega) &= \frac{j\omega}{(j\omega+2)^2(j\omega+1)} \\ &\downarrow \\ &+ \frac{j\omega}{\left(\frac{j\omega}{2}+1\right)^2(j\omega+1)} = \frac{\frac{1}{2}(j\omega)}{\left(\frac{j\omega}{2}+1\right)^2(j\omega+1)} \end{aligned}$$

for type 1 $\rightarrow \frac{1}{4}$

$$H(\omega) = 20 \log_{10}\left(\frac{1}{4}\right) = -12$$

$$\phi = 0 \Rightarrow K > 0$$

for type 2 $\rightarrow H(\omega) = 20 \rightarrow \frac{db}{decade}$

$$\phi = 90$$



for type 3 pole $(\frac{j\omega}{2}+1)^2$

$$H(\omega) \begin{cases} 0 & \omega \leq 2 \\ -40 & \omega \geq 2 \end{cases}$$


$$\phi \begin{cases} 0 & 0.2 \leq \omega \\ -90^\circ & 0.2 \leq \omega \leq 2 \\ -180^\circ & \omega \geq 2 \end{cases}$$

for type 3 $\rightarrow \frac{1}{jw+1} \rightarrow$
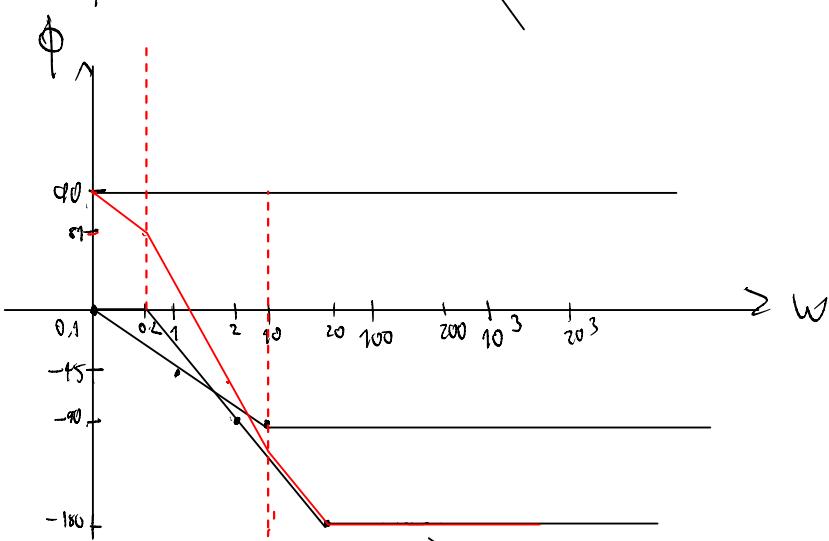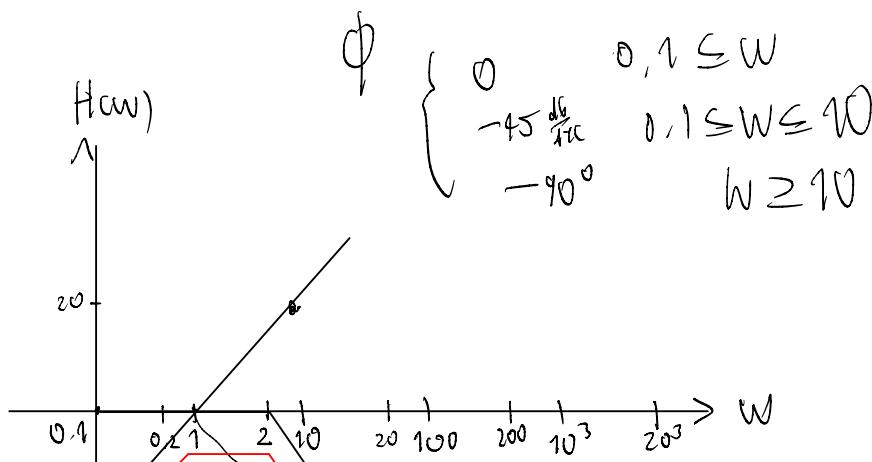
$$H(w) \begin{cases} 0 & w \leq 1 \\ -2\omega > 1 & \end{cases}$$



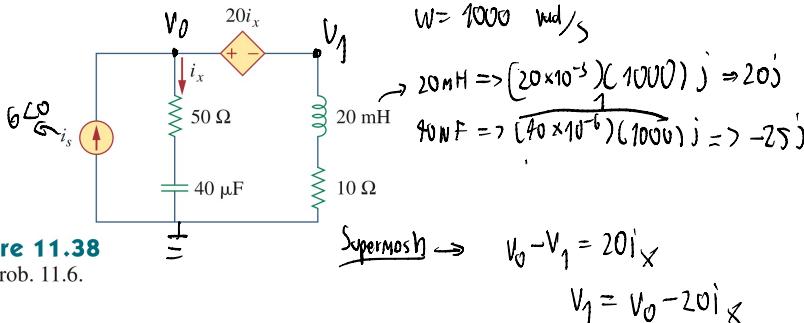- 11.6 For the circuit in Fig. 11.38, $i_s = 6 \cos 10^3 t$ A. Find the average power absorbed by the 50Ω resistor.



$$\text{kVL at } V_0: -6 + \frac{V_0}{50 - 25j} + \frac{V_1}{20j + 10} = 0$$

$$\frac{V_0}{50 - 25j} + \frac{V_0 - 20i_x}{20j + 10} = 6 \quad \text{if so } i_x = \frac{V_0}{50 - 25j}$$

Solve and do it all

- 11.7** Given the circuit of Fig. 11.39, find the average power absorbed by the $10\text{-}\Omega$ resistor.


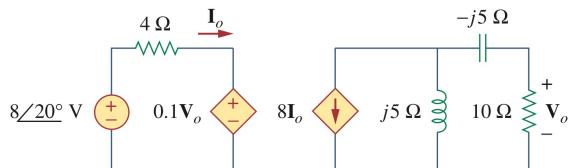


Figure 11.39

For Prob. 11.7.

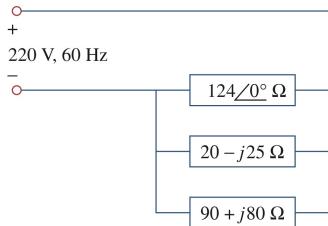- 11.38** For the power system in Fig. 11.67, find: (a) the average power, (b) the reactive power, (c) the power factor. Note that 220 V is an rms value.



We know from Complex Power

$$S = P + jQ$$

Average Power from Complex Power:

Figure 11.67
For Prob. 11.38.

$$S = P + jQ \rightarrow$$

(a) We know Relation $\rightarrow S_2 = \frac{V_{rms}^2}{Z_2} \rightarrow S_1 = \frac{(220)^2}{124} = 390.32$

$$S_2 = \frac{(220)^2}{20+j25} \Rightarrow 949.4 - 1180.5 j$$

$$S_3 = \frac{V^2}{Z_3} \Rightarrow \frac{(220)^2}{90-j80} = 200 + 267.05 j$$

$$S = S_1 + S_2 + S_3 = \text{Total Complex Power} \Rightarrow 1872.6 \angle -29.796 \text{ VA}$$

$$S = 1634.7 - 913.4 j$$



Average Power P

$$= 1634.7 \text{ W}$$

∴ Real Power $\Rightarrow 1634.7 \text{ VA}$

(c) $P_f = \frac{P}{|S|} \rightarrow \frac{1634.7}{1872.61} = 0.8732$

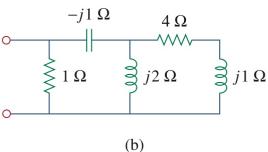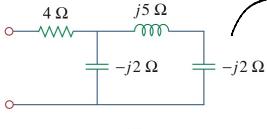- 11.41** Obtain the power factor for each of the circuits in Fig. 11.68. Specify each power factor as leading or lagging.



We know $P_f \text{ angle} = Z \angle \theta_v - \theta_i$

$$\text{a) } Z_{eq} \Rightarrow 4 - j5 \approx 2\sqrt{3} \angle -56.3^\circ \\ = \cos(-56.3^\circ) \rightarrow \text{leading} \rightarrow \theta_i > \theta_v$$

$$P_f = 0.5547$$

Figure 11.68

For Prob. 11.41.

- 11.42** A 110-V rms, 60-Hz source is applied to a load impedance \mathbf{Z} . The apparent power entering the load is 120 VA at a power factor of 0.707 lagging.

- (a) Calculate the complex power.
- (b) Find the rms current supplied to the load.
- (c) Determine \mathbf{Z} .
- (d) Assuming that $\mathbf{Z} = R + j\omega L$, find the values of R and L .

$$(a) S = \tilde{V} \tilde{I}_{rms}^*$$

$$\tilde{I}_{rms} = \frac{\tilde{V}}{R}$$

$$P_f = \frac{P}{S} \rightarrow P_{\text{power}} = (0.707)(120)$$

$$\Rightarrow 84.84 \text{ W + j } 1$$

To find $Q \rightarrow$ $Q = P \tan \theta$

$$\cos \theta = 0.707 \rightarrow \theta \approx 45^\circ$$

$$Q = 84.84 \tan 45^\circ$$

$$Q = 84.84$$

I_{rms} $\rightarrow S = P + jQ \Rightarrow 84.84 + 84.84j$

$$(b^c) \quad S = \sqrt{I_{rms}^2 + I_{rms}^2}$$

$$\tilde{I}_{rms}^2 = \frac{S}{\sqrt{2}} = \frac{(84.84 + 84.84j)}{\sqrt{10}} \Rightarrow 0.7793 + 0.7793j$$

↓

$$\text{or } 1.0907 \angle 45^\circ$$

$$\tilde{I}_{rms} = \underbrace{1.0907 \angle -45^\circ}_{\text{Ans}}$$

$$(c^-) \quad S = (I_{rms})^2 Z$$

$$Z = \frac{84.84 + 84.84j}{(1.0907)^2} \Rightarrow 71.3915 + 71.3915j$$

$$R = 71.3915$$

$$WL = 71.3915$$

$$L = \frac{71.3915}{(2\pi \times 60)}$$

$$= \underline{0.9891 H}$$

- 11.44 Find the complex power delivered by v_s to the network in Fig. 11.69. Let $v_s = 100 \cos 2000t$ V

Don't know if it's RMS or not use

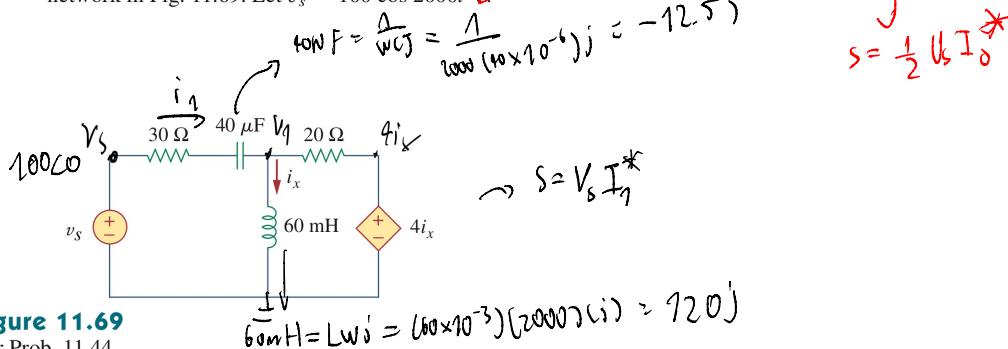


Figure 11.69

For Prob. 11.44.

$$\text{KCL at } V_1 \rightarrow \frac{V_1 - 100}{30 - 12.5j} + \frac{V_1}{120j} + \frac{V_1 - 4i_x}{20} = 0$$

$$i_x = \frac{V_1}{120j}$$

$$\frac{V_1 - 100}{30 - 12.5j} + \frac{V_1}{120j} + \frac{V_1 - 4 \left(\frac{V_1}{120j} \right)}{20} = 0$$

↙

$$\frac{1}{30 - 12.5j} V_1 + \frac{1}{120j} V_1 + \frac{1}{20} V_1 - \frac{1}{600j} V_1 - \frac{1}{30j} V_1 = \left(\frac{53}{676} + \frac{131}{23350} j \right) V_1 = \left(\frac{480}{767} + \frac{200}{767} j \right)$$

$$= \frac{100}{30 - 12.5j} \quad V_1 = 37.06 + 12.652j$$

$$\approx 39.71 \angle 18.85^\circ$$

$$I_1 = \frac{100 - (34.76 \angle 18.85^\circ)}{30 - 12.5j}$$

$$1.937 + 0.3855j$$

$$\text{or } 1.975 + 11.259^\circ$$

$$S = \sum V_s I^*$$

$$= 100(1.975 + j - 11.2560)$$

11.46 For the following voltage and current phasors, calculate the complex power, apparent power, real power, and reactive power. Specify whether the pf is leading or lagging.

(a) $V = 220 \angle 30^\circ$ V rms, $I = 0.5 \angle 60^\circ$ A rms

(b) $V = 250 \angle -10^\circ$ V rms,
 $I = 6.2 \angle -25^\circ$ A rms

(c) $V = 120 \angle 0^\circ$ V rms, $I = 2.4 \angle -15^\circ$ A rms

(d) $V = 160 \angle 45^\circ$ V rms, $I = 8.5 \angle 90^\circ$ A rms

(a) Complex power $\rightarrow S = \tilde{V}_{rms} \tilde{I}_{rms}^*$

$$= 220 \angle 30 (0.5 \angle 60)$$

$$= 110 \angle 30$$


$$S = 95.2628 - 55j$$

$$\frac{1}{4} - \frac{\sqrt{3}}{4}j$$

$\Rightarrow Q = 55$
 This is lagging

$$\text{real power} = 95.2628 \text{ - } j \text{ Reactive Power} \Rightarrow 55 \text{ VA}$$

$$|S| = 110,$$

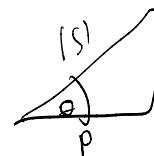

$$\cos \theta = \frac{P}{|S|} = \frac{95.2628}{110} = 0.866$$

$$\cos \theta = 0.866$$

- 11.52** In the circuit of Fig. 11.71, device A receives 2 kW at 0.8 pf lagging, device B receives 3 kVA at 0.4 pf leading, while device C is inductive and consumes 1 kW and receives 500 VAR.

(a) Determine the power factor of the entire system.

(b) Find \mathbf{I} given that $\mathbf{V}_s = 120 \angle 45^\circ$ V rms.

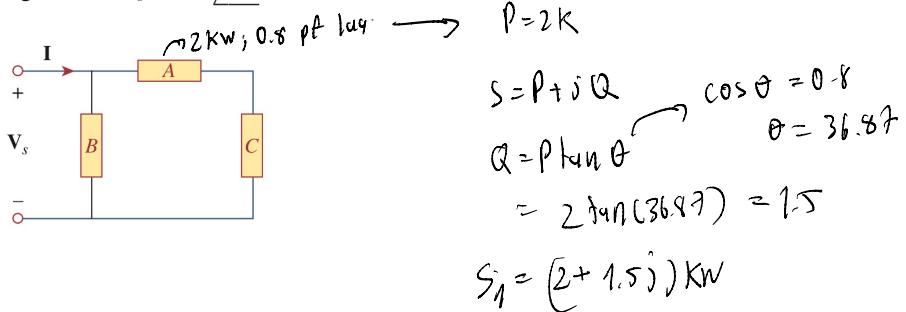


Figure 11.71

For Prob. 11.52.

$$\underline{A + Q} \quad |S| = 3 \text{ kW} - P_f = 0.5$$

$$P_f = \frac{P}{|S|} \rightarrow P = 0.4 \times 3 = 1.2 \text{ kW}$$

$$\cos \theta = 0.4$$

$$\theta = -66.422 \rightarrow \text{leading}$$

$$Q = P \tan \theta \rightarrow 1.2 \tan(-66.422)$$

$$\Rightarrow -2.7495$$

$$S_2 = (1.2 - 2.7495j) \text{ kW}$$

$$\underline{A + C} \quad 1 \text{ kW} ; +500 \rightarrow Q$$

$$S_3 = (1 + 0.5j) \text{ kW}$$

$$S = 4.2 - 0.7495j$$

$$PF = \frac{P}{|S|} = \frac{4.2}{4.26635} = 0.9844$$


(b) I

$$S = \bar{V}_{rms} \bar{I}_{rms}^*$$

$$\bar{I}_{rms}^* = \sum \bar{V}_{rms}$$

$$\bar{I}_{rms} = 35.55 \angle 55^\circ$$

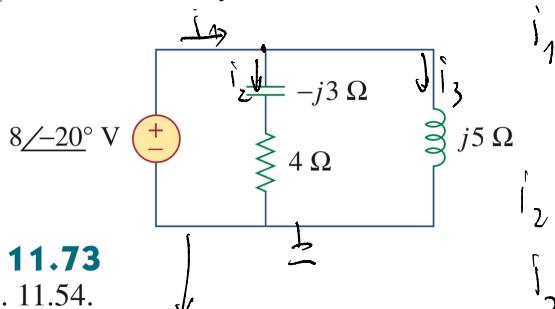- 11.54** For the network in Fig. 11.73, find the complex power absorbed by each element.



$$i_1 = i_2 + i_3$$

$$i_2 = \frac{8\angle-20}{4-j3}$$

$$i_2 = 1.6 \angle 16.87^\circ$$

Figure 11.73

For Prob. 11.54.

Complex Power by the Source

$$S = VI^* \Rightarrow$$


for Complex power it's
in V_{rms}

$$i_3 = \frac{8\angle-20}{j5}$$

$$\Rightarrow 1.6 \angle -110^\circ$$

$$i_1 = i_2 + i_3 \Rightarrow 1.431 \angle -96.565^\circ$$

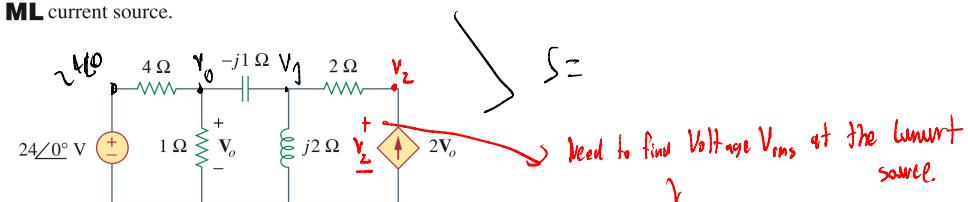- 11.57** For the circuit in Fig. 11.76, find the average, reactive, and complex power delivered by the dependent current source.



Need to find Voltage V_{rms} at the current source.

to find Complex power.

Figure 11.76

For Prob. 11.57.

$$\frac{V_o - 24}{4} + \frac{V_o - V_1}{-j1} + \frac{V_o}{1} = 0$$

$$\frac{V_o}{1} + \frac{V_o - V_1}{-j1} = \frac{24 - V_o}{4}$$

$$2V_o = (S + j4)V_o - j4V_1 \rightarrow (1)$$

At node 1.

$$\frac{V_1 - V_o}{-j1} - 2V_o + \frac{V_1}{j2} = 0$$

$$\frac{V_o - V_1}{-j1} + 2V_o = \frac{V_1}{j2}$$

$$V_1 = (2 - j4)V_o \rightarrow (2)$$

$$V_0 = \frac{-24}{19+j4} ; V_1 = \frac{(-24)(2-j4)}{19+j4}$$

also We know $\rightarrow 2V_0 = \underline{V_2 - V_1}$

$$V_2 - V_1 = 4V_0$$

$$V_2 = 4V_0 + V_1$$

$$V_2 = \frac{(-24)(6-j4)}{19+j4}$$

$$S = V_2 J^* = V_2 (2V_0 J^*)$$

}
Ans

- 11.58** Obtain the complex power delivered to the 10-k Ω resistor in Fig. 11.77 below.

ML

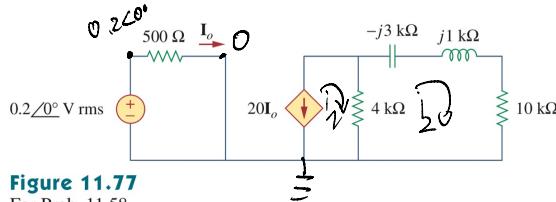


Figure 11.77
For Prob. 11.58.

$$I_o = \frac{0.2}{500} \Rightarrow \frac{1}{2500} A$$

$$I_1 = -20I_o \Rightarrow -\frac{1}{125}$$

$$\text{KVL } i_2 \quad i_2(-2j) + 10i_2 + 4(i_2 - i_1) = 0$$

$$-2j i_2 + 10i_2 + 4i_2 + \frac{4}{125} = 0$$

$$(14-2j)i_2 = \frac{-4}{125}$$

$$i_2 = (2.2627 \times 10^{-3}) \angle -171.87^\circ$$


$$S = I_{rms}^2 Z \Rightarrow \left((2.2627 \times 10^{-3}) \right)^2 \left(10 \times 10^3 \right)$$

$$S = 0.0512 \text{ VA}$$

V

Complex Power delivered to resistor always = watts.

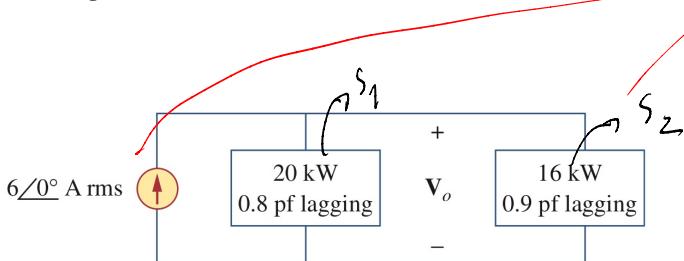- 11.60** For the circuit in Fig. 11.79, find \mathbf{V}_o and the input power factor.



The complex, real, reactive power of the source equal to the sum of the complex, real, reactive power of each individual load.

Figure 11.79

For Prob. 11.60.

Conservation of AC Power

$$S_{\text{Total}} = S_1 + S_2 \rightarrow \text{for } S_1 \rightarrow P = 20 \text{ kW} ; \cos \theta = 0.8$$

$$Q = P \tan \theta \rightarrow \tan \theta = 0.8 \\ \theta = 36.87^\circ$$

$$= 20 \tan 36.87^\circ$$

$$Q = 15$$

$$S_1 = (20 + 15j) \text{ kVA}$$

$$\text{for } S_2 \rightarrow P = 16 \text{ kW} ; \cos \theta = 0.9$$

$$Q = P \tan \theta \rightarrow \tan \theta = 0.9 \\ \theta = 25.87^\circ$$

$$\theta = 25.87^\circ$$

$$Q = 16 \tan 25.87^\circ$$

$$\Rightarrow 7.749$$

$$S_2 = (16 + 7.749j) \text{ kVA}$$

$$S_T = S_1 + S_2 = (20 + 15j) + (16 + 7.749j)$$

$$= 36 + 22.75j$$

$$\downarrow$$
$$= 42.585 \angle 32.29^\circ$$

We know $S = \tilde{V}_{rms} \tilde{I}_{rms}^*$

$$\tilde{V}_o = \frac{S}{\tilde{I}_{rms}^*} = \frac{42.585 \angle 32.29}{b}$$

$$\approx b + 3.79j$$
$$V$$

$$\tilde{V}_o = 7.0975 \angle 32.29$$

$$P_f = \cos \theta \Rightarrow \theta, 84.5^\circ$$

$$S = 42.585 \angle 32.29$$

$$|S| \quad [\Theta_v - \Theta_i]$$

- 11.61** Given the circuit in Fig. 11.80, find \mathbf{I}_o and the overall complex power supplied.

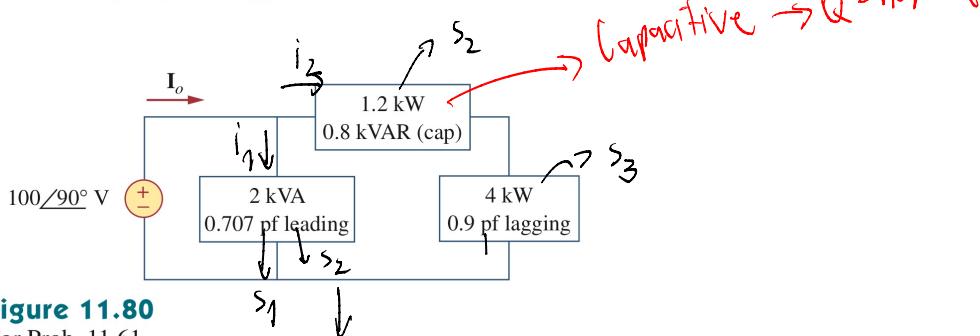


Figure 11.80
For Prob. 11.61.

$$\text{We Know } \mathbf{I}_o = \mathbf{I}_1 + \mathbf{I}_2$$

$$S_2 = (1.2 - 0.8j) \text{ kVA} \quad \times$$

$$S_3 = 4 \text{ kW; } 0.9 \text{ pf lagging}$$

$$\cos \theta = 0.9$$

$$\theta \approx 25.84^\circ$$

$$Q = 4 \tan 25.84^\circ$$

$$Q = 1.937$$

$$S_3 = (4 + 1.937j) \text{ kVA} \quad \times$$

$$S_1 = |S| = 2 \text{ kVA} \rightarrow P_f = 0.707$$

$$P_f = \frac{P}{|S|}$$

$$\cos \theta = 0.707$$

$$\theta = -45^\circ$$

$$P = P_f |S| = 0.707 \times 2$$

$$\Rightarrow 1.414$$

$$Q = P \tan \theta \rightarrow 1.414 \tan (-45^\circ)$$

$$S_1 = 1.414 - 1.414j \text{ kVA}$$

$$S_4 = S_2 + S_3$$

$$\Rightarrow 5.2 + 1.937j$$

$$S_4 = \sqrt{I_{ms}^*}$$

$$I_2^* = \frac{S_4}{\sqrt{V_{rms}}}$$

$$I_2^* = 11.37 - 52j$$

$$I_2 = 11.37 + 52j$$

$$\text{find } I_1 \rightarrow S_1 = V_{\text{rms}} \tilde{I}_{\text{rms}}^*$$

$$\tilde{I}_{\text{rms}} S_1 = \frac{S_1}{V_{\text{rms}}} \Rightarrow \frac{(1.414 - 1.414j) \times 10^3}{100 \angle 90}$$

\downarrow

$$\tilde{I}_1 = -14.142 + 14.142j$$

$$I_0 = I_1 + I_2 \Rightarrow 66.2 \angle 92.4^\circ$$

$$S_0 = V_0 \tilde{I}_0^*$$

$$= (100 \angle 90) (66.2 \angle 92.4)$$

\searrow

$$S_0 = 6.62 \angle -7.4^\circ$$

11.62 For the circuit in Fig. 11.81, find \mathbf{V}_s .

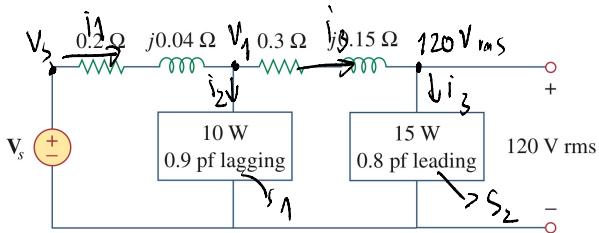


Figure 11.81

For Prob. 11.62.

$$I_1 = I_2 + I_3 \rightarrow S_o = \tilde{V}_s \tilde{I}_1$$

$$\tilde{V}_s = \frac{S_o}{\tilde{I}_1}$$

find \tilde{I}_3 $\rightarrow 15 \text{ W} ; 0.8 \text{ pf leading}$

$$P = 15 \quad \cos \theta = 0.8$$

$$\theta = -36.87^\circ$$

$$Q = 15 \tan(-36.87)$$

$$\Rightarrow -11.25$$

$$S_2 = 15 - 11.25j$$

$$S_2 = \tilde{V}_{IMC} \tilde{I}_3$$

$$\tilde{I}_3 = \frac{S_2}{\tilde{V}_{IMC}} = \frac{15 - 11.25j}{120}$$

$$\tilde{I}_3 \approx 0.156 \angle 36.87^\circ$$

$$\text{find } I_2 \quad \text{also need } V_1 \rightarrow i_3 = \frac{V_1 - 120}{0.3 + 0.15j}$$

$$i_3(0.3 + 0.15j) + 120 = V_1$$

$$V_1 = 120.02 + 0.0469j$$

$$S_1 = \tilde{V}_{ms} \tilde{I}_2^*$$

$$\tilde{I}_2^* = \frac{S_1}{\tilde{V}_{ms}} = \frac{10 + 4.843j}{(120.02 + 0.0469j)}$$

10W; 0.9 Pt lagging

$$\cos \theta = 0.9$$

$$\theta = 25.842$$

$$\alpha = 10 + jn 25.842 = 4.8 + 3$$

$$S_1 = 10 + 4.843j$$

$$\tilde{I}_1 = \tilde{I}_2 + \tilde{I}_3 = 0.2087 + 0.053j$$

Now We Knows $\rightarrow i_1 = \frac{V_s - V_1}{0.2 + 0.04j} \quad i_1(0.2 + 0.04j) + V_1 = V_s$

11.63 Find \mathbf{I}_o in the circuit of Fig. 11.82.

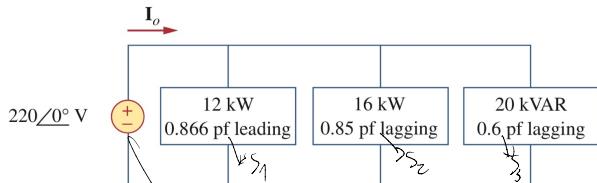


Figure 11.82
For Prob. 11.63.

from $S_1 \rightarrow 12 \text{ kW ; } 0.866 \text{ pf leading}$

$$P = 12 \text{ kW} \rightarrow Q = P \tan \theta \rightarrow \cos \theta = 0.866$$

$$\theta = -30^\circ$$

$$Q = 12 \tan(-30)$$

$$= -6.928$$

$$S_1 = (12 - 6.928j) \text{ kVA} //$$

$$S_2 \rightarrow P = 16 \text{ kW} \quad \cos \theta = 0.85 \\ \theta = 31.788^\circ$$

$$Q = 16 \tan 31.788 \Rightarrow 9.916$$

$$S_2 = (16 + 9.916j) \text{ kVA} //$$

$$S_3 \rightarrow Q = 20 \text{ kVAR} \rightarrow \cos \theta = 0.6$$

$$\cos \theta = 0.6$$

$$\theta = 53.13^\circ$$

$$Q = P \tan \theta \rightarrow P = \frac{Q}{\tan \theta} = \frac{20}{\tan 53.13^\circ} = 15$$

$$S_3 = (15 + 20j) \text{ kVAR}$$

$$S_T = 48 + 22.958j \rightarrow S = \bar{V}_{rms} \bar{I}_o^* \downarrow$$

$$I_o = \frac{S}{V_{rms}}$$

$$\Rightarrow \frac{(t) + 22.448i)}{220}$$

$$I_o = (0.2216 \angle -28.13^\circ) A$$

10.48 Find i_o in the circuit of Fig. 10.93 using superposition.


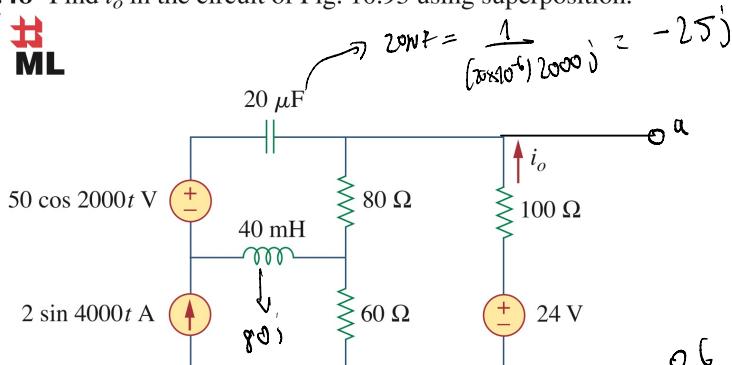


Figure 10.93

Find Thevenin / Norton Equivalent -

first use $W = 2000$

Close $2\sin 4000t$, and $24V$

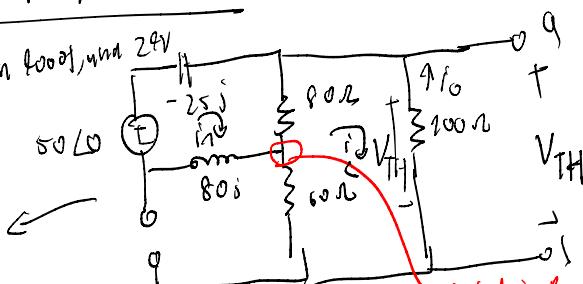

$Z_{eq} \rightarrow$ Close $50 \angle 0$

$$\rightarrow 100 \parallel [(55j \parallel 80) + 60]$$

$$= 41.35 \angle 12.78^\circ$$

$$V_{TH} \rightarrow KVL \rightarrow i_1 \rightarrow -25j i_1 - 50 + 80(i_1 - i_2) + 80j i_1 = 0$$

$$55j i_1 - 50 + 80(i_1 - i_2) = 0$$

$$\cancel{55j i_1} \rightarrow 100i_2 + 60i_2 + 80(i_2 - i_1) = 0$$

$$80(i_2 - i_1) = -160i_2$$

$$80(i_1 - i_2) = 50 - 55j i_1$$

$$80(i_2 - i_1) = -50 + 55j i_1$$

$$-160i_2 = -50 + 55j i_1$$

$$-160i_2 + 50 = 55j i_1$$

$$i_1 = \frac{-160i_2 + 50}{55j}$$

$$80(i_2 - \left(\frac{-160i_2 + 50}{55j} \right)) = -160i_2$$

$$80 \left(i_2 + \left(\frac{160i_2}{55j} - \frac{50}{55j} \right) \right) = -160i_2$$

$$i_2 + \frac{160i_2}{55j} - \frac{50}{55j} = -2i_2$$

$$(3 - \frac{32}{55}j)i_2 = \frac{50}{55j}$$

$$i_2$$

$$V_{TH} = i_2 \times 100 = 15.14 - j15.618 \text{ V}$$

10.48 Find i_o in the circuit of Fig. 10.93 using superposition.



ML


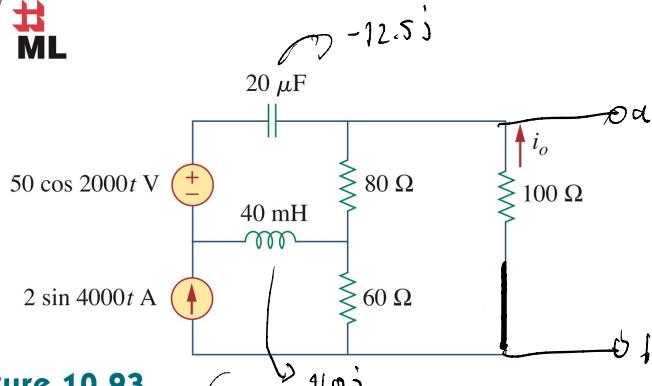


Figure 10.93

for $\omega = 4000$

close $50 \cos 2000t$ and $24V$

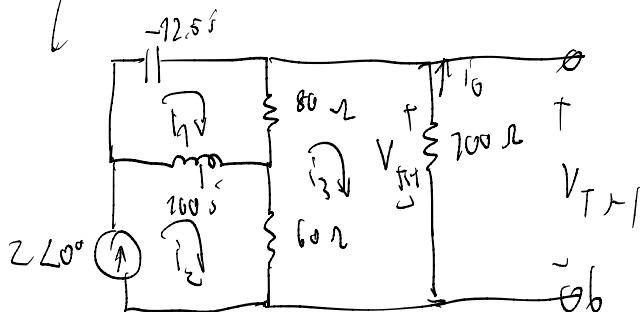


$$Z_{in} \text{ close } 200 \rightarrow 100 \parallel \left[\frac{(167.5)}{80} + j60 \right] \\ 35.12 + j66.62 \Omega$$

$$\underline{\text{Find } V_{T_{(1)}}} \quad \underline{hV L i_1} \rightarrow -12.5j i_1 + 80(i_1 - i_3) + 160j(i_1 - i_2) = 0$$

$$\underline{hV L i_2} \rightarrow i_2 = 2 \angle 0^\circ$$

$$\underline{hV L i_3} \rightarrow 100i_3 + 60(i_3 - i_2) + 80(i_3 - i_1) = 0$$

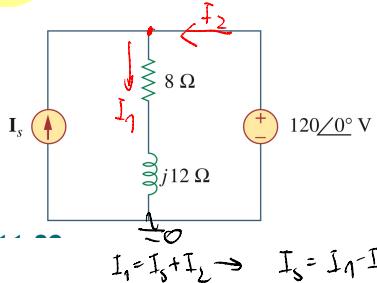- 11.64 Determine I_s in the circuit of Fig. 11.83, if the voltage source supplies 2.5 kW and 0.4 kVAR (leading).



We know $120\angle 0^\circ$ V supplies 2.5 kW and 0.4 kVAR

$$\downarrow$$

$$S = (2.5 - 0.4) \text{ kVA}$$

↓ leading

$$S = V_{\text{in}} \bar{I}_s *$$


$$\bar{I}_s * = \frac{S}{V_{\text{in}}} = \frac{(1500 - 400j)}{120}$$

$$\bar{I}_s = \frac{125}{6} + \frac{20}{3}j$$

$$I_1 = \frac{120 - 0}{8 + j12} \Rightarrow \frac{60}{73} - \frac{40}{73}j$$

$$I_s = I_1 - I_2 \Rightarrow 19.19 \angle -147.61$$

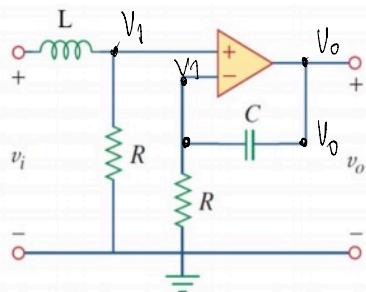Q5. Please draw a **Bode plot** of the transfer function $H(\omega) = V_o/V_i$ [Total 18 points]



$$H(\omega) = \frac{V_o}{V_i}$$

$$\text{KCL at } V_1 \rightarrow \frac{V_i - V_1}{j\omega L} + \frac{V_1}{R} = 0$$

$$\frac{V_1}{R} = \frac{V_i - V_1}{j\omega L}$$

$$\frac{(j\omega L)V_1}{R} + V_1 = V_i$$

$$V_1 \left(\frac{j\omega L}{R} + 1 \right) = V_i \rightarrow (1)$$

KCL at V_1 on other side:

$$\frac{V_1 - V_o}{\frac{1}{j\omega C}} + \frac{V_1}{R} = 0$$

$$j\omega C(V_1 - V_o) + \frac{V_1}{R} = 0$$

$$\frac{V_1}{R} = j\omega C(V_o - V_1)$$

$$\frac{V_1}{R} = j\omega C V_o - j\omega C V_1$$

$$\frac{V_1}{R} + j\omega C V_1 = j\omega C V_o$$

$$V_o = V_1 \left(\frac{1}{j\omega C R} + 1 \right) \rightarrow (2)$$

J

$$H(j\omega) = \frac{V_o}{V_i} \Rightarrow \frac{\frac{1}{j\omega CR} + 1}{\frac{j\omega L}{R} + 1}$$

$$\begin{aligned} H(j\omega s) &= \frac{\left(\frac{1}{j\omega CR} + 1\right)}{\left(\frac{j\omega L}{R} + 1\right)} \times \frac{j\omega CR}{j\omega CR} \\ &= \frac{1 + j\omega R}{j\omega CR \left(\frac{j\omega L}{R} + 1\right)} = \frac{1 + j\omega R}{(j\omega)^2 CL + j\omega CR} \end{aligned}$$

$$\begin{aligned} H(j\omega s) &= \frac{\left(1 + \frac{j\omega}{RC}\right)}{j\omega C \left(\frac{j\omega L + R}{R}\right)} \xrightarrow{\text{Type 3}} \left(\frac{j\omega}{L} + 1\right) \\ &\quad \text{Type 3} \rightarrow (j\omega)^{-1} \xrightarrow{\text{Type 3} \rightarrow \text{Pole}} \end{aligned}$$

for Type 1 $\rightarrow \frac{1}{RC} \rightarrow 20 \log_{10} \left| \frac{1}{RC} \right|$

for $\frac{1}{RC} > 0 \rightarrow \phi = 0$

for Type 2 $(j\omega)^{-1} \rightarrow \text{slope} \Rightarrow -20 \log_{10}(j\omega)$

$$\phi = -90^\circ$$

for Type 3 zeros $\rightarrow Z_1 = \frac{1}{RC}$ $H(j\omega) \begin{cases} 0 \rightarrow \omega \leq \frac{1}{RC} \\ 20 \rightarrow \omega \geq \frac{1}{RC} \end{cases}$

$$\phi \rightarrow \begin{cases} 0 & \omega \leq 0.1 \frac{1}{RC} \\ 45 + 45 \log_{10} \left(\frac{\omega}{\frac{1}{RC}} \right) & 0.1 \frac{1}{RC} \leq \omega \leq \frac{10}{RC} \end{cases}$$


10


$$w \geq \frac{10}{R_0}$$

for type I zeros $Z_{\gamma} = \frac{P}{L}$

$$H_{\text{out}} \rightarrow \begin{cases} 0 & w \leq \frac{R}{L} \\ -20 & w \geq \frac{R}{L} \end{cases}$$

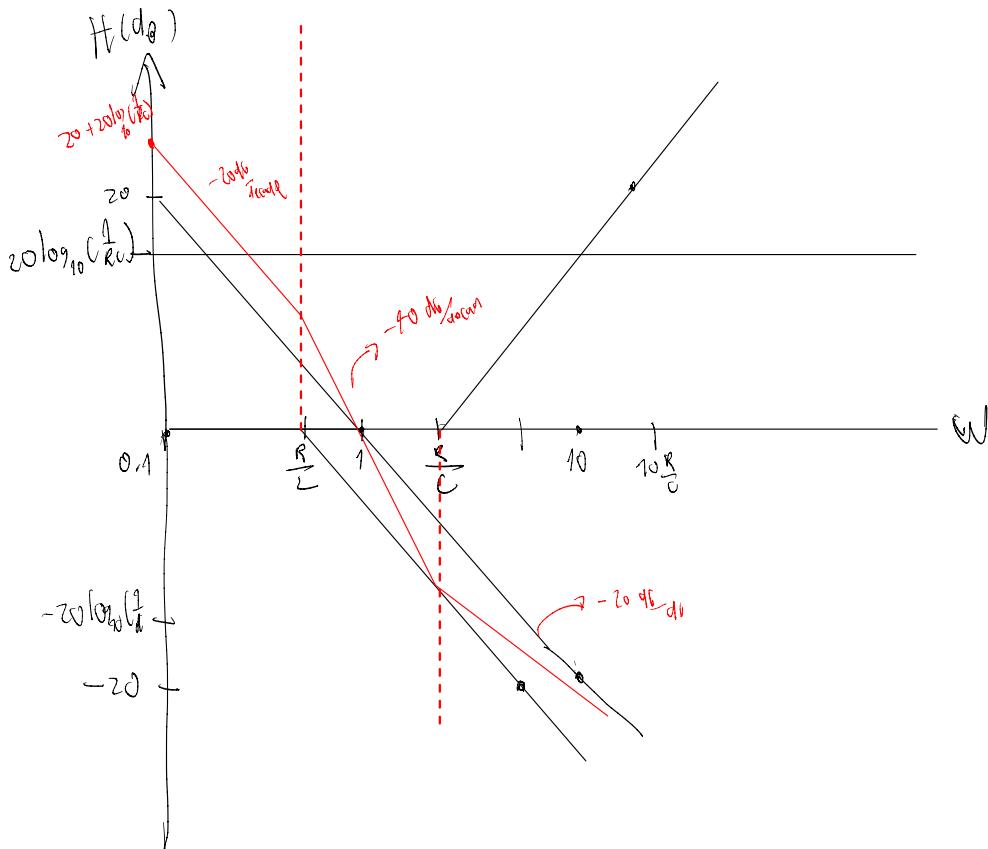
$$\phi \rightarrow \begin{cases} 0 & w \leq 0.1 \frac{R}{L} \\ -45 & 0.1 \frac{R}{L} \leq w \leq 10 \frac{R}{L} \\ -90 & w \geq 10 \frac{R}{L} \end{cases}$$



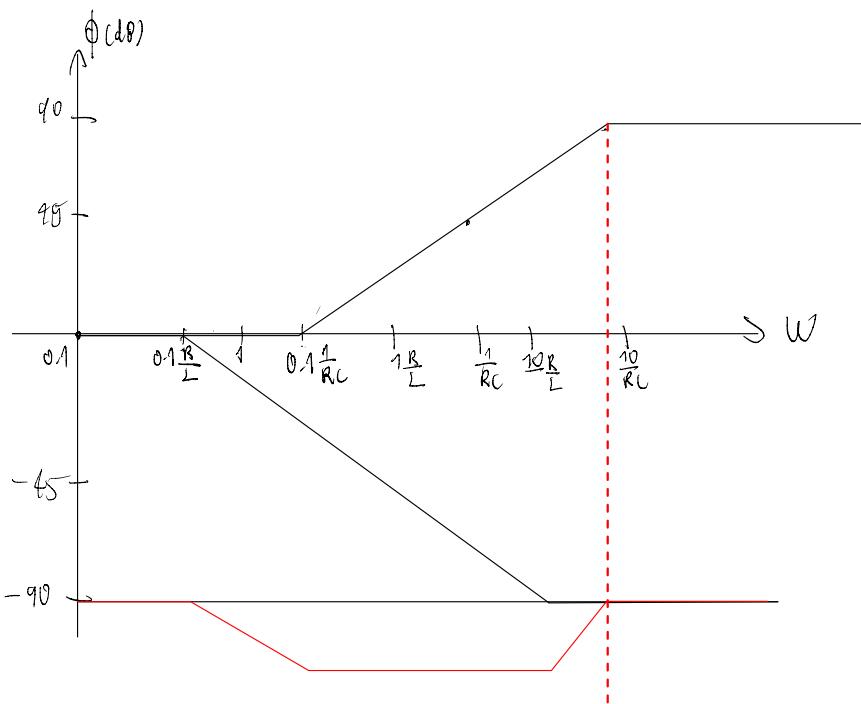

$$V_L = 100 \angle 45^\circ \left(\frac{j1}{1+3j} \right)$$
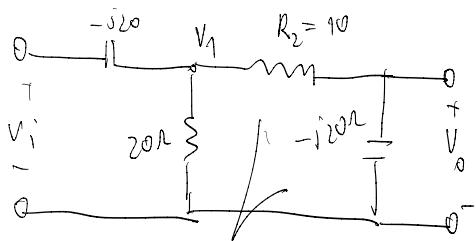
$$\therefore V_L = 50.596 \angle 63.43^\circ$$



$$Z = 20 \parallel 10 - 20j = \frac{140}{73} - \frac{80}{73}j$$

$$V_1 = V_i \left(\frac{\left(\frac{140}{73} - \frac{80}{73}j \right)}{\left(\frac{140}{73} - \frac{80}{73}j \right) - 20j} \right)$$

$$V_1 = \frac{\left(\frac{140}{73} - \frac{80}{73}j \right)}{\left(\frac{140}{73} - \frac{80}{73}j \right)} V_i$$

$$V_o = V_1 \left(\frac{-j40}{10 - 20j} \right) = \left(\frac{4}{5} - \frac{2}{5}j \right) V_1$$

$$V_o = \left(\frac{2\sqrt{5}}{3} \angle -26.57^\circ \right) V_1$$

$$V_1 =$$

$$|s|=6 \quad ; \quad f=0.750 \rightarrow 41.4096$$

$$P_f = \frac{P}{|s|} \rightarrow 0.750(6) = 4.5 \text{ kW}$$


$$S_1 = 4.5 +$$

$$\frac{(= 4500 (\tan(41.4096) - \tan(11.4783)))}{(25 \times 60)(240)^2}$$


$$k_i = 0.980 \rightarrow 11.4783$$

↓
Leading component of Capacitance

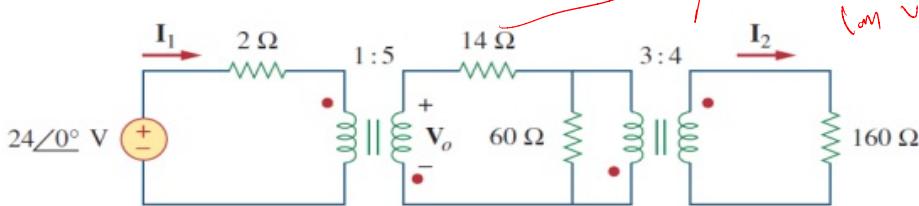3.[8%] For the circuit below, find I_1 , I_2 and V_o .



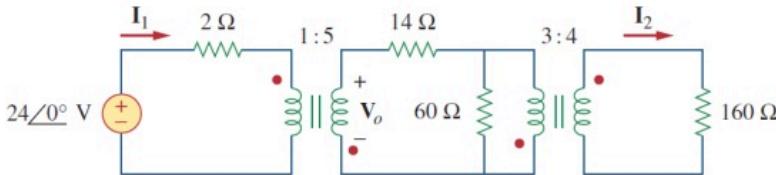
3.[8%] For the circuit below, find I_1 , I_2 and V_o .



Solution:

We reflect the 160-ohm load to the middle circuit.
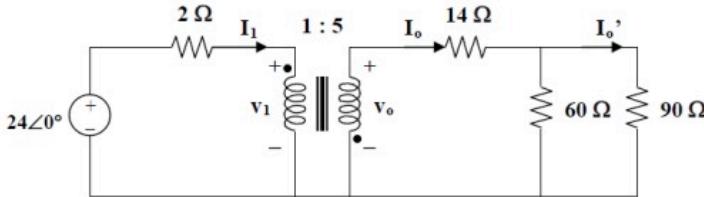
$$Z_R = Z_L/n^2 = 160/(4/3)^2 = 90 \text{ ohms, where } n = 4/3$$



$$14 + 60||90 = 14 + 36 = 50 \text{ ohms}$$

We reflect this to the primary side.

$$Z_{R'} = Z_L/(n')^2 = 50/5^2 = 2 \text{ ohms when } n' = 5$$

$$I_1 = 24/(2+2) = 6 \text{ A}$$


$$24 = 2I_1 + v_1 \text{ or } v_1 = 24 - 2I_1 = 12 \text{ V}$$

$$v_o = -nv_1 = -60 \text{ V}, I_o = -I_1/n_1 = -6/5 = -1.2$$

$$I_o' = [60/(60+90)]I_o = -0.48 \text{ A}$$

$$I_2 = -I_o'/n = 0.48/(4/3) = 360 \text{ mA}$$

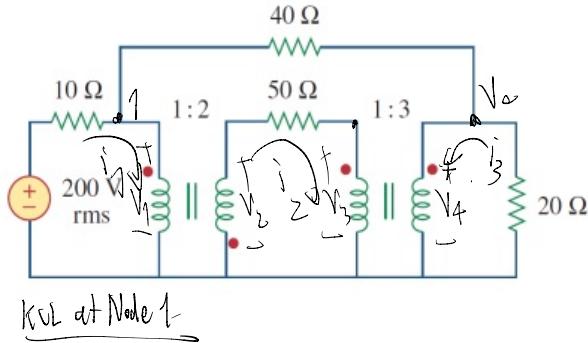4.[10%] Calculate the average power dissipated by the 20Ω resistor in the circuit below.



$$P_2 = \frac{V_{rms}^2}{R}$$

$$P = \frac{V_4^2}{20}$$

$$\frac{V_1 - 200}{10} + I_1 + \frac{V_1 - V_4}{40} = 0$$

$$\frac{200 - V_1}{10} = \frac{V_1 - V_4}{40} + I_1 \rightarrow (1)$$

$$200 = 1.25 V_1 - 0.25 V_4 + 10 I_1 \rightarrow (2)$$

KCL at Node 2

$$\frac{V_4 - V_1}{40} + I_3 + \frac{V_4}{20} = 0$$

$$\frac{V_1 - V_4}{40} = \frac{V_4}{20} + I_3$$

V

$$V_1 = 3V_4 + 40I_3 \rightarrow (2)$$

diff at the terminals $\rightarrow \frac{V_2}{V_1} = -2 \rightarrow V_2 = -2V_1$

$$\therefore \frac{I_1}{I_2} = -2 \rightarrow I_1 = -2I_2$$

$$\text{KVL at the main loop.} \rightarrow 50I_2 + V_3 - V_2 = 0$$

✓

$$V_3 = V_2 - 50I_2 \rightarrow (3)$$

At the Second Terminal.

$$\frac{V_4}{V_3} = 3 \rightarrow V_3 = \frac{1}{3}V_4$$

$$\frac{I_2}{I_3} = -3$$

$$\frac{I_2}{I_3} = -3 I_3$$

$$\frac{1}{3}V_4 = V_2 - 50I_2$$

$$V_4 = 3V_2 - 150(-2I_3)$$

We have seven equations and seven unknowns. Combining (1) and (2) leads to

$$200 = 3.5V_4 + 10I_1 + 50I_3$$

$$V_2 = -2V_1$$

But from (4) and (7), $I_1 = -2I_2 = -2(-3I_3) = 6I_3$. Hence

$$200 = 3.5V_4 + 110I_3$$

$$V_4 = -6V_1 + 450I_3 \quad (8)$$

From (5), (6), (3), and (7),

$$V_4 = 3(V_2 - 50I_2) = 3V_2 - 150I_2 = -6V_1 + 450I_3$$

Substituting for V_1 in (2) gives

$$V_4 = -6(3V_4 + 40I_3) + 450I_3 \longrightarrow I_3 = \frac{19}{210}V_4 \quad (9)$$


Substituting (9) into (8) yields

$$200 = 13.452V_4 \longrightarrow V_4 = 14.87$$

$$P = \frac{V^2}{20} = \underline{\underline{11.05 \text{ W}}}$$

- 9.48 Find the Norton equivalent with respect to terminals a,b in the circuit of Fig. P9.48.

Figure P9.48

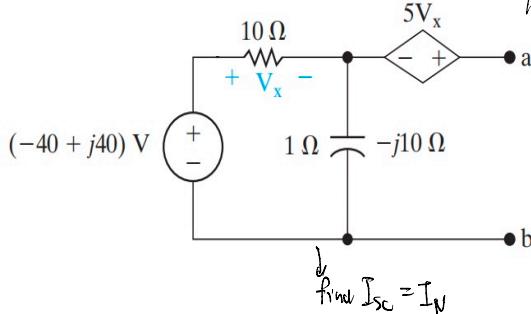


$$Z_N = Z_{TH}$$

$$Z_{TH} < \frac{V_{TH}}{I_{SC}}$$

$$I = \frac{-5V_x - (-V_{OC})}{-59\Omega}$$

$$-j10I = -5V_x + V_{OC}$$

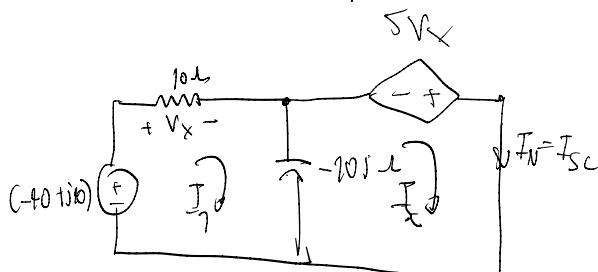

$$V_x - 10j(V_x - I_{SC}) = -40 + j40 \rightarrow (1)$$

$$V_x - 10jI_1 + 10jI_Sc = -40 + j40$$

KVL at Mesh 2

$$-5V_x = 10j(I_{SC} - I_1)$$

$$V_x = -2j(7_{SC} - I_1) \rightarrow (2)$$

$$\text{Also } V_x = 10I_1$$

$$\text{Solve give } I_N = I_{SC} = 6 + j4 A$$

Sketch bode Plot. \rightarrow

$$G(s) \rightarrow \frac{s}{(s+2)^2(s+1)}$$

\swarrow Type 2 \rightarrow Zeros
 $\frac{jw}{\sum}$

$$(1 + \frac{jw}{2})^2 (1 + jw)$$

$$\approx \frac{\frac{1}{4}(jw)}{(1 + \frac{jw}{2})^2 (jw + 1)}$$